

Department of ECE, Bennett University

EECE105L: Fundamentals of Electrical and Electronics Engineering

Tutorial Sheet-3

1. For the circuits shown in fig. 1 through 4, find the equivalent resistance R_T between nodes A and B. If the value for any resistor is not provided, assume $1\text{ k}\Omega$ resistance.

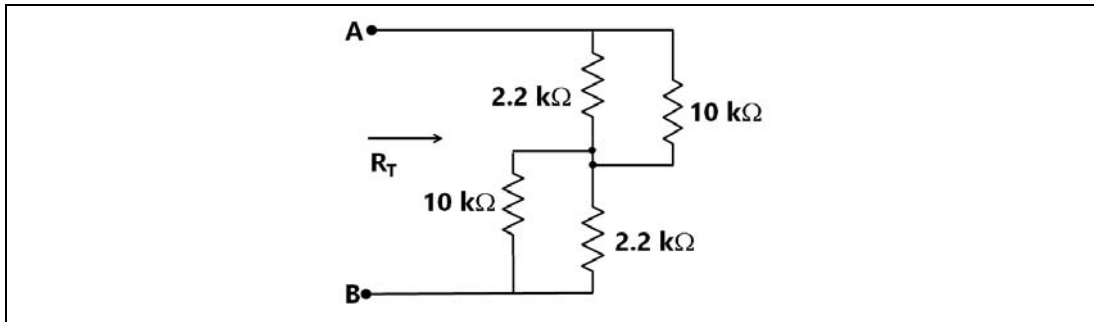


Fig. 1

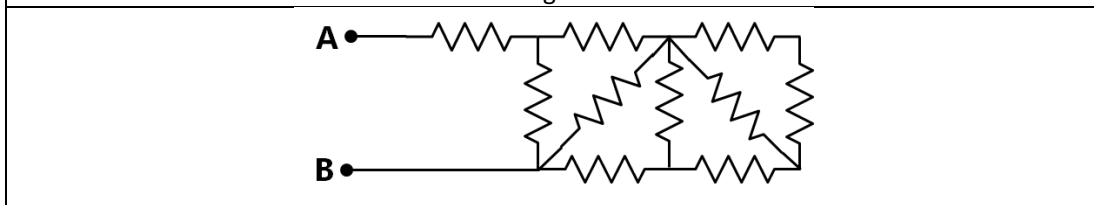


Fig. 2

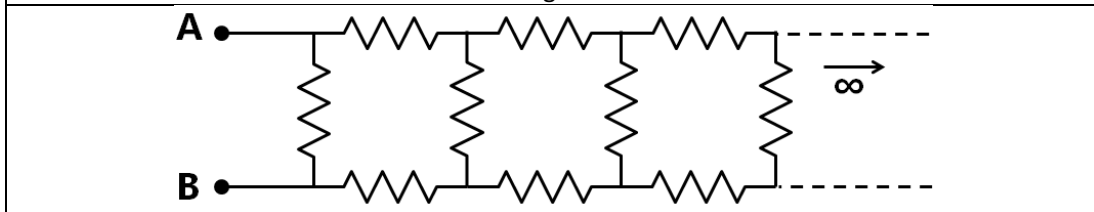


Fig. 3

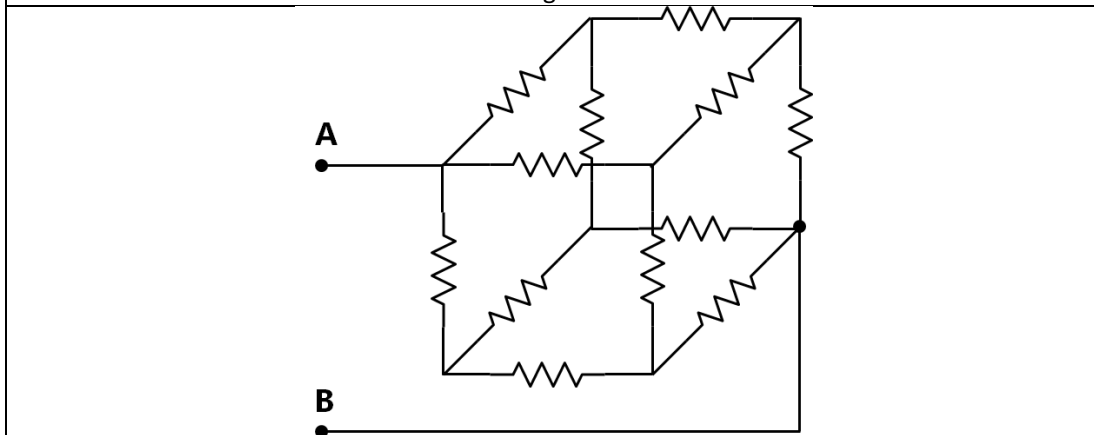


Fig. 4

2. For the circuit shown in fig. 5 through 8, find the equivalent resistance between nodes A and B. Then evaluate current through each resistor and voltage drop across each resistor.

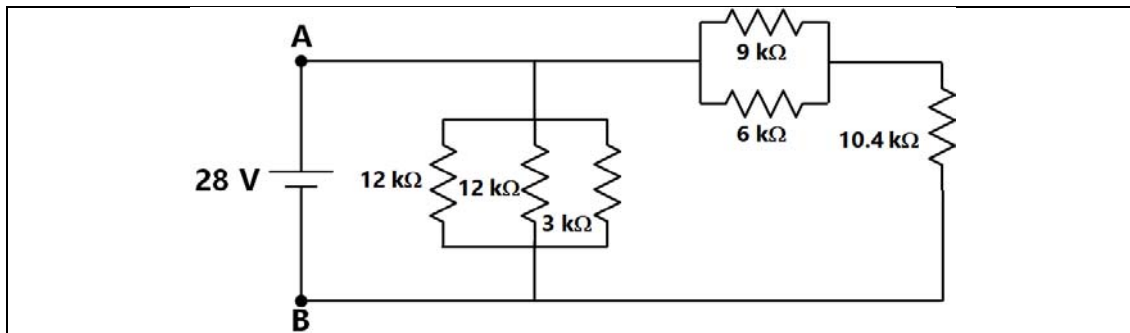


Fig. 5

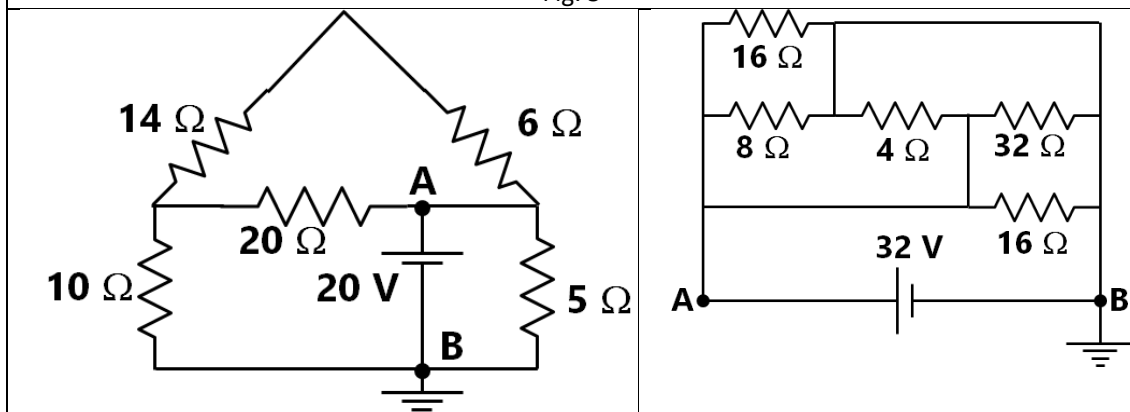


Fig. 6

Fig. 7

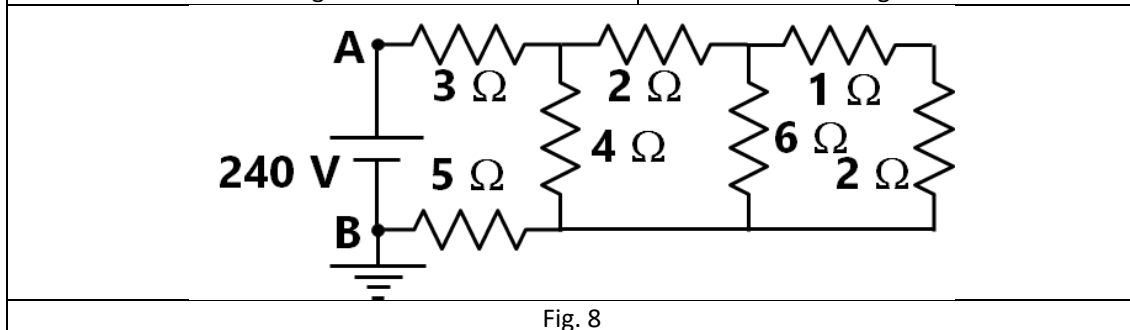


Fig. 8

3. For the circuit shown in fig. 9 and fig. 10, determine current through the resistors, voltage across the resistors and their power rating.

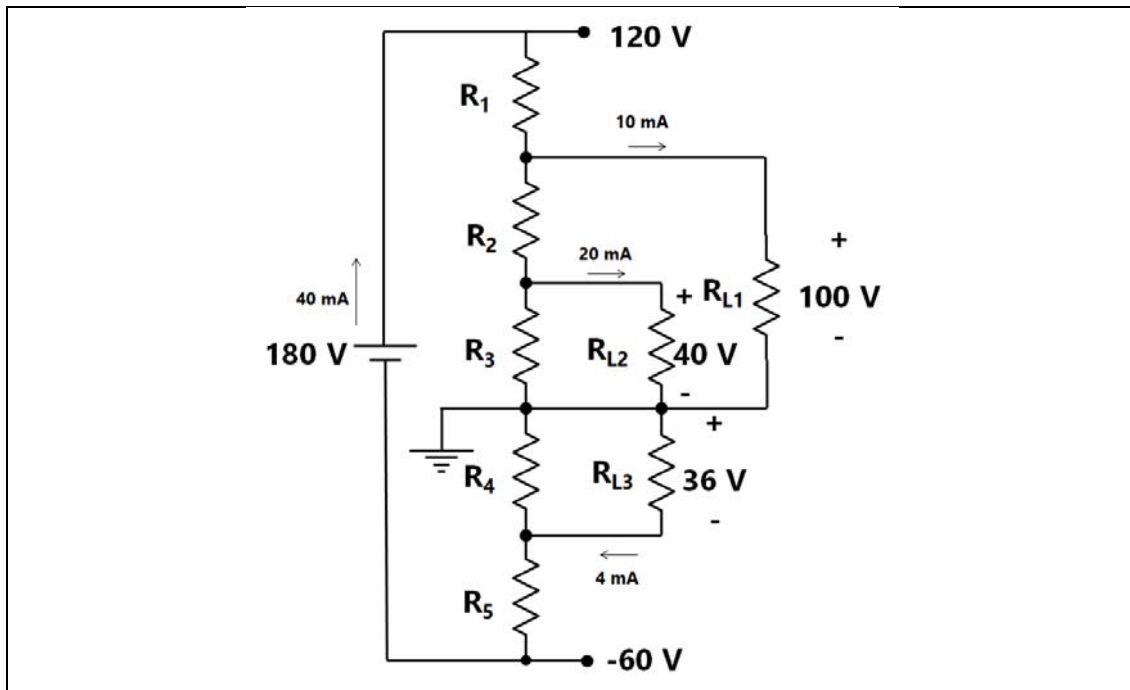


Fig. 9

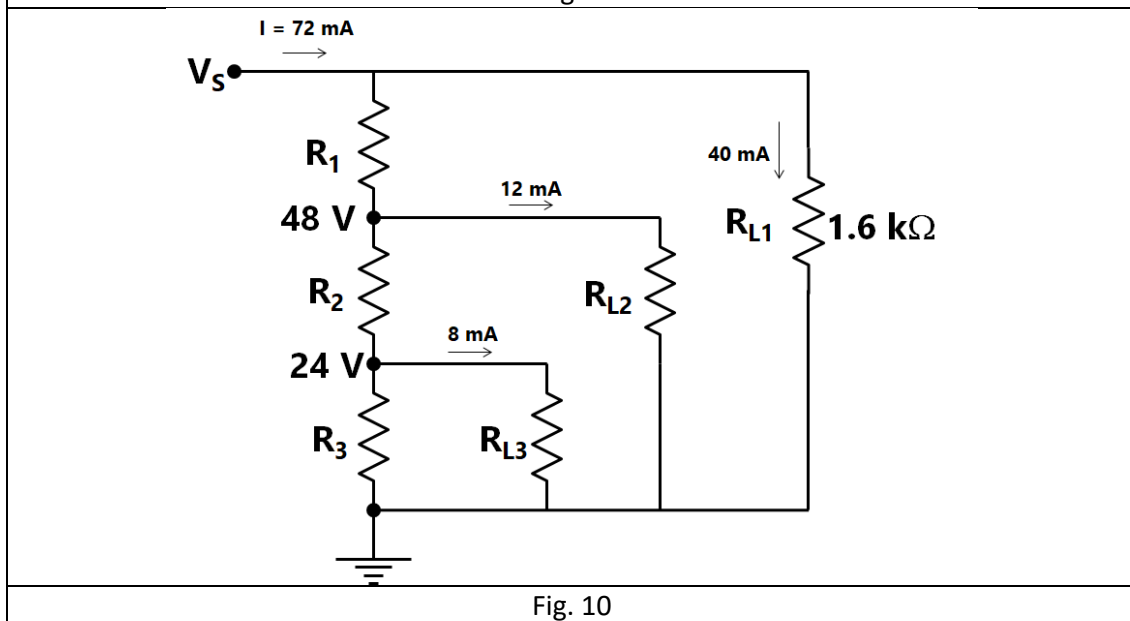


Fig. 10

----- END OF QUESTIONS -----