




BENNETT
UNIVERSITY
A TIMES GROUP INITIATIVE

Series and Parallel Connections


Rama Komaragiri

Direction of Current Flow: Voltage Source

- If the wires is an ideal conductor (having no opposition to current flow), then the potential difference across the resistor R (V_R) is equal to the supply voltage (V)
- By convention, the direction of conventional current flow and electron current flow are opposite
- Following the conventional current flow, $I = \frac{V}{R} = \frac{V_R}{R}$
- a rise in the potential across the battery (- to +)
- a drop in the potential across the resistor (+ to -)

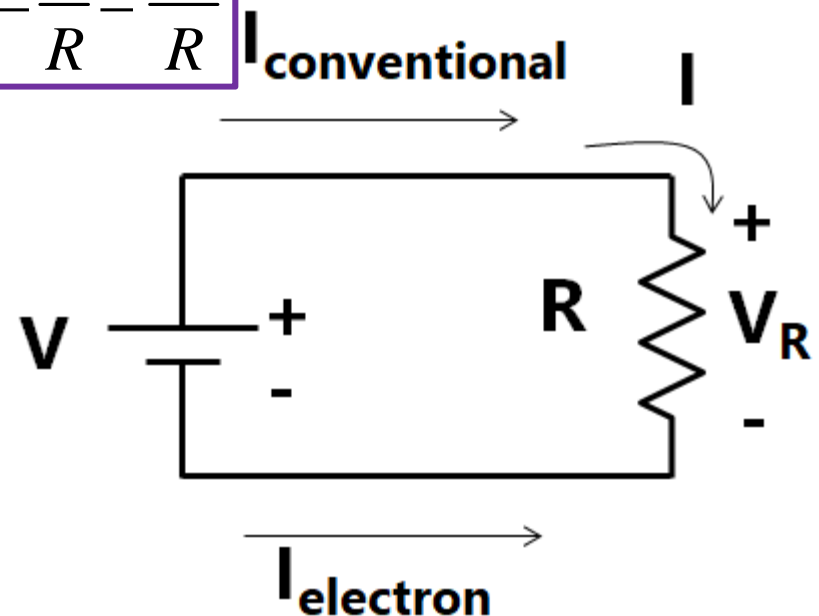


Series Connections

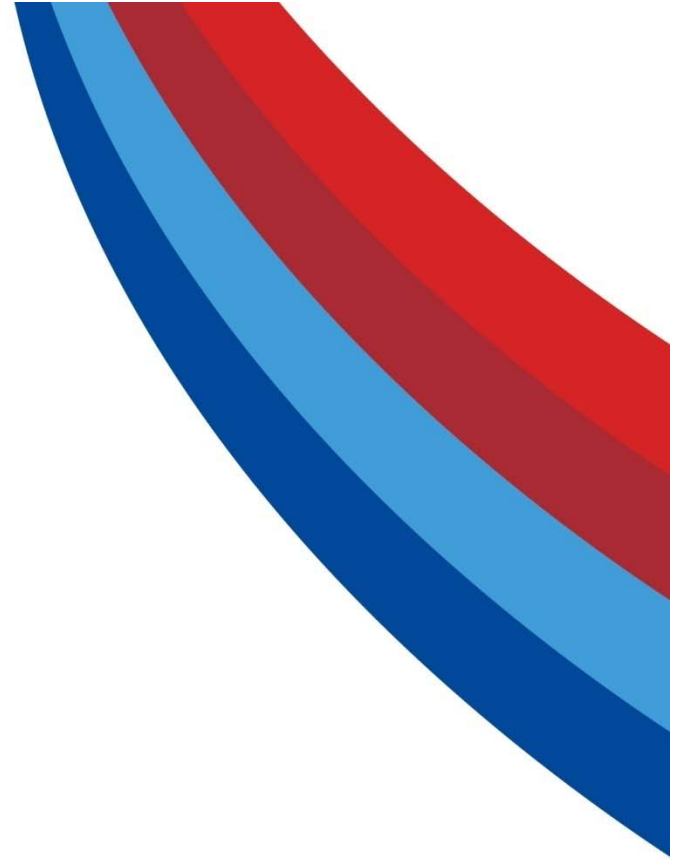




Series Connections

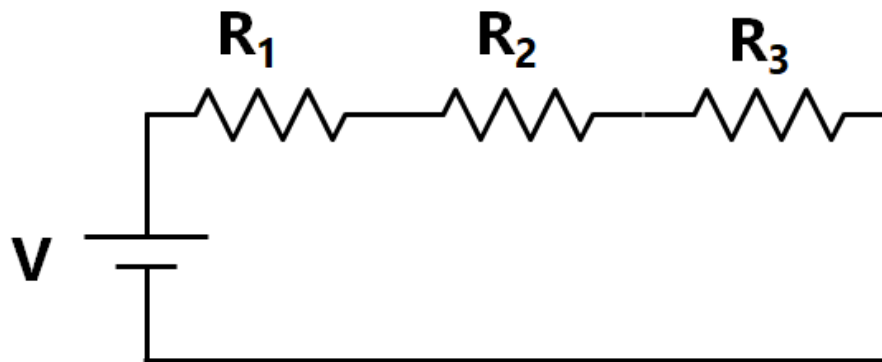- Circuit is an arrangement of components (or circuit elements) that results in a continuous flow of charge, or current, through the configuration
- Series Configuration: The current is same in the every point in the circuit




Resistors in Connected in Series

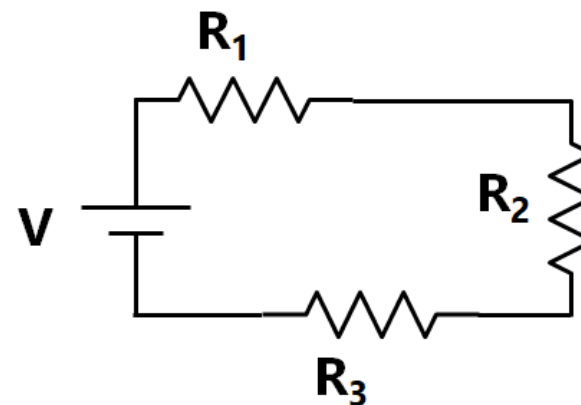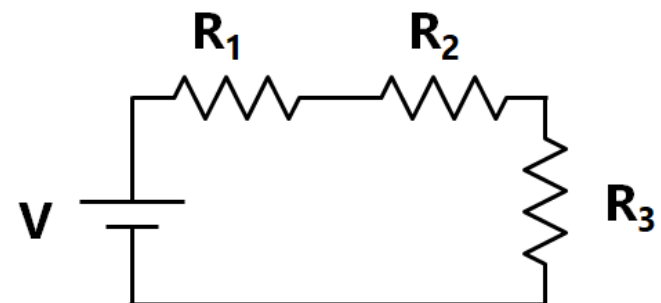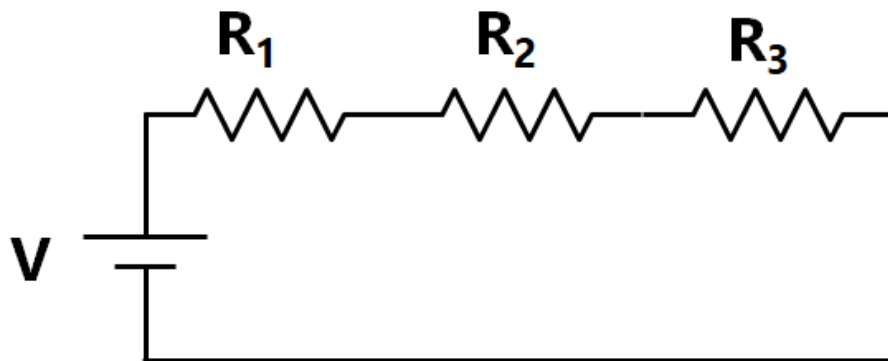- Series Configuration: The current is same in the every point in the circuit
 - In a circuit, if two elements are in series, the current must be same
 - If the currents are same in two adjoining circuit branches, the elements may or may not be in series



Direction of Current in a Resistor

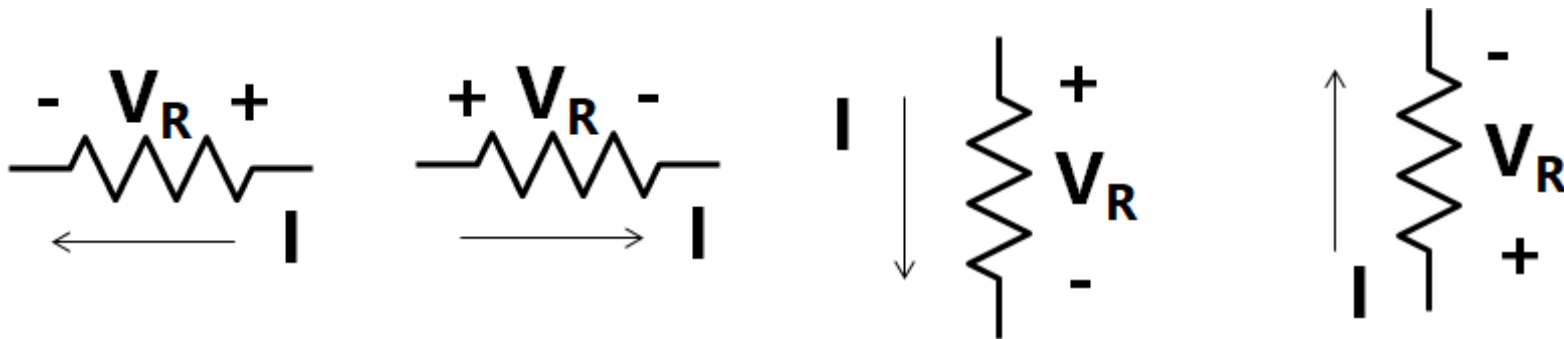
- The polarity of the voltage across a resistor is determined by the direction of current
- Current entering a resistor creates a voltage drop with polarity as shown



- **The sign of current flow in a resistor when current flows from positive potential to negative potential is negative**

Resistors in Connected in Series

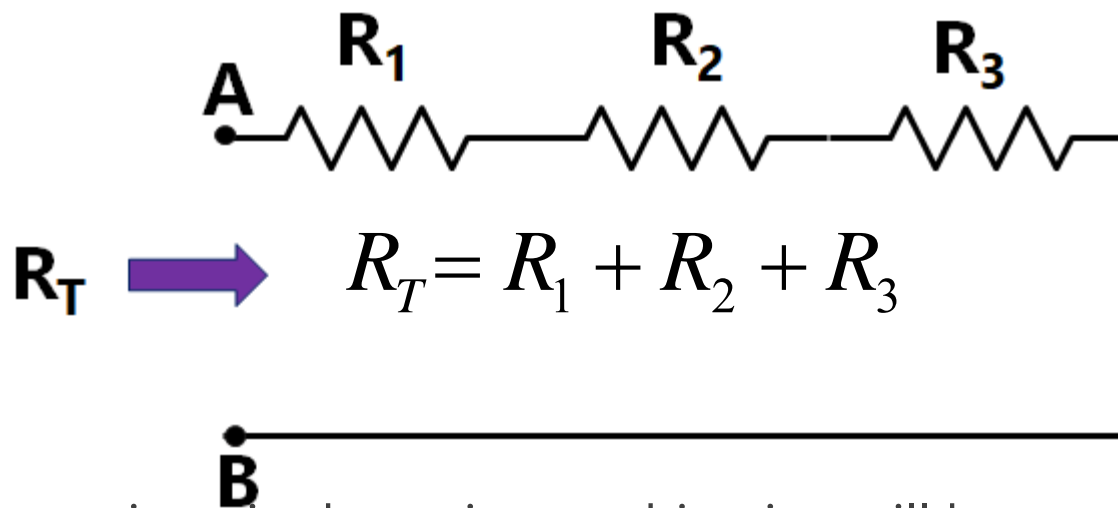- The total resistance of a series configuration is the sum of the individual resistances as seen between the terminals "A" and "B"





- The largest resistor in the series combination will have most impact on the total resistance
- More resistors in series combination, the greater the resistance, no matter what the value of the resistor is

Resistors in Connected in Series


- Let $R_1 = 1 \text{ k}\Omega$, $R_2 = 5 \text{ k}\Omega$, $R_3 = 1.5 \text{ k}\Omega$
- The total resistance $R_T = 7.5 \text{ k}\Omega$.
- Let $V = 15 \text{ V}$
- Current I through the circuit is
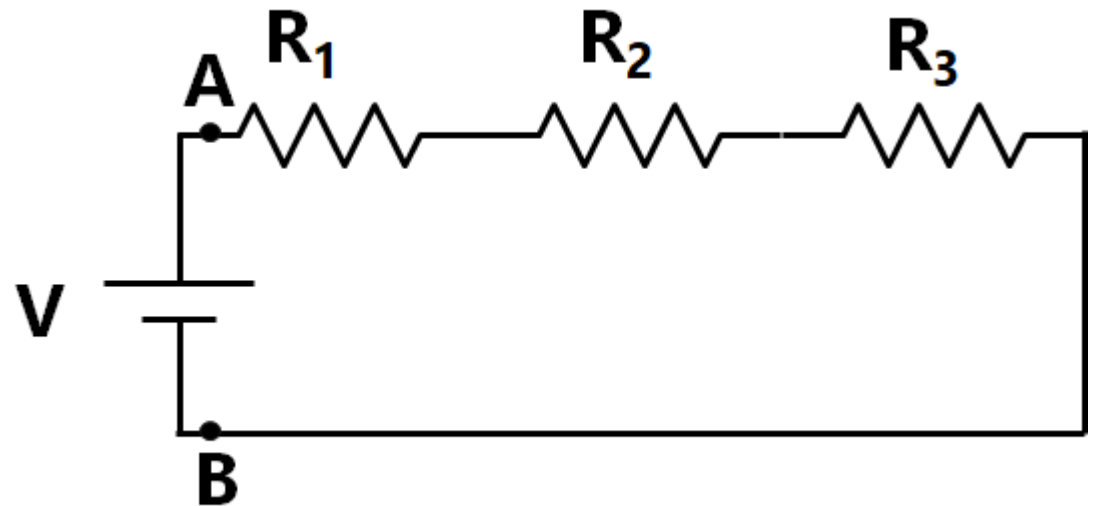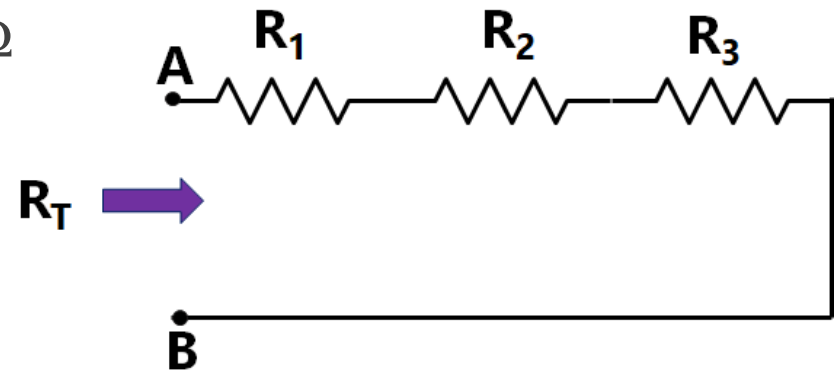
$$I = \frac{V}{R_T} = \frac{15\text{V}}{7.5\text{k}\Omega} = 2\text{mA}$$




Voltage Sources Connected in Series

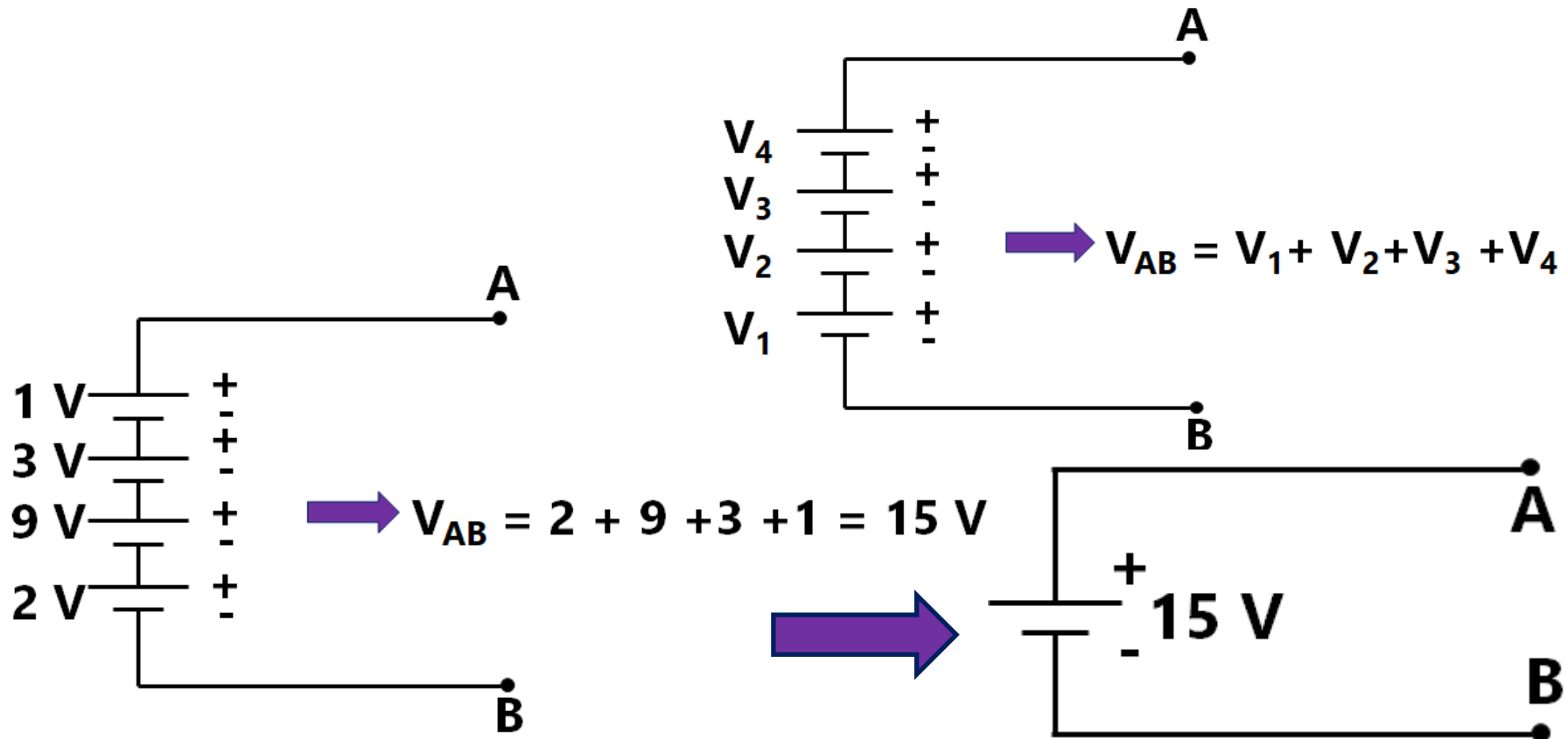- The net voltage is obtained by summing up the voltages with same polarity and subtracting voltages with opposite polarity




Voltage Sources Connected in Series

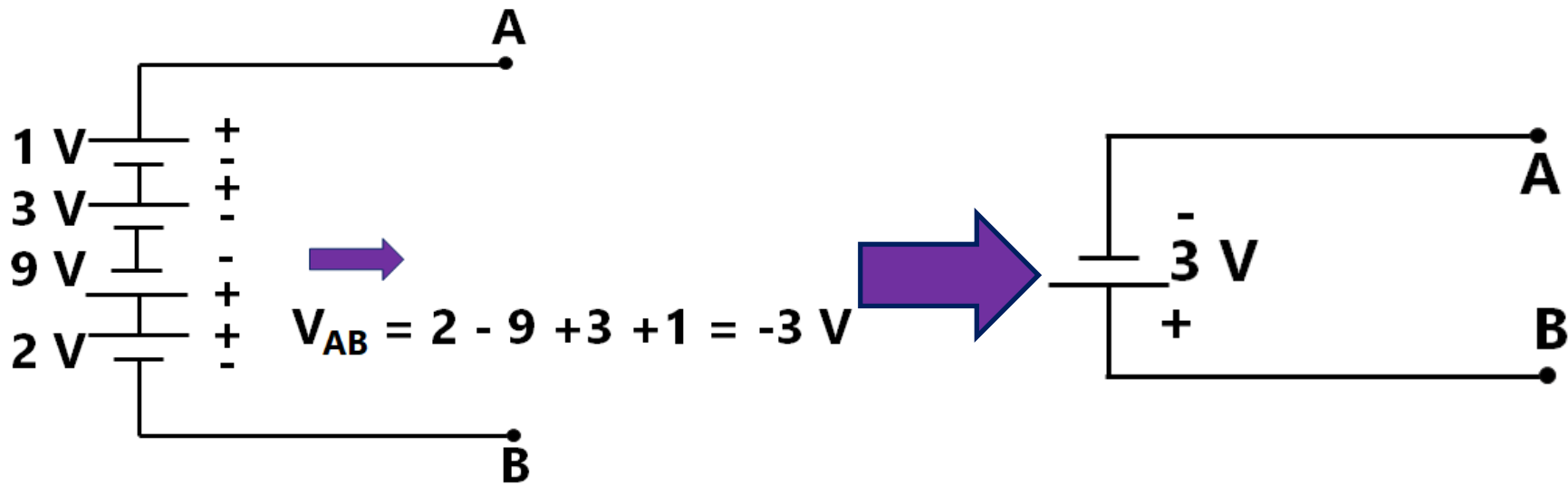

Kirchhoff's Voltage Law

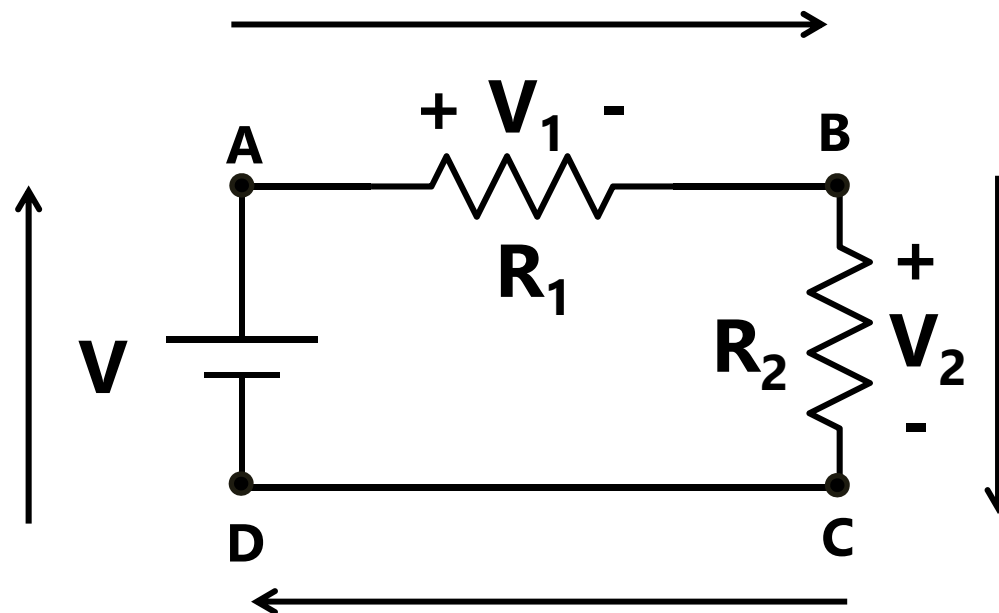- A definition of closed path is required by starting at a point and ending at the same point thus forming a closed loop
- **Kirchhoff's Voltage Law (KVL):** The algebraic sum of the potential raises and drops around a closed path (closed loop) is zero




Kirchhoff's Voltage Law

- Writing out the voltages in sequence by noting the sign convention,
 - V : with positive sign
 - V_1, V_2 : with negative sign
- By applying KVL,
 - Loop: "A" → "B" → "C" → "D" → "A"

$$+V - V_1 - V_2 = 0$$



$$V = V_1 + V_2$$

$$\sum_{raises} V = \sum_{drops} V$$

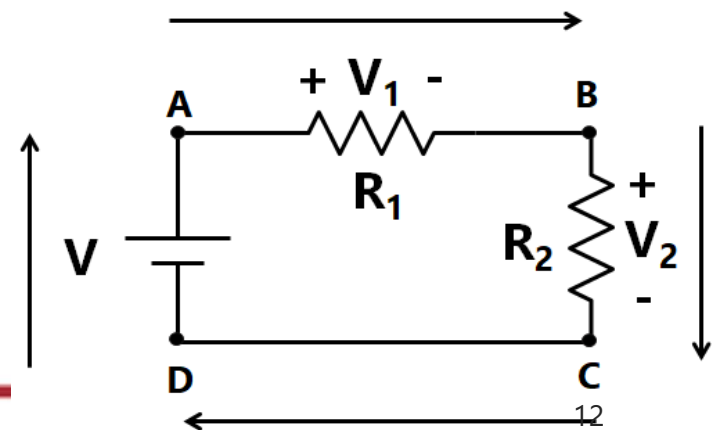

Resistances Connected in Series-Voltage Divider Rule

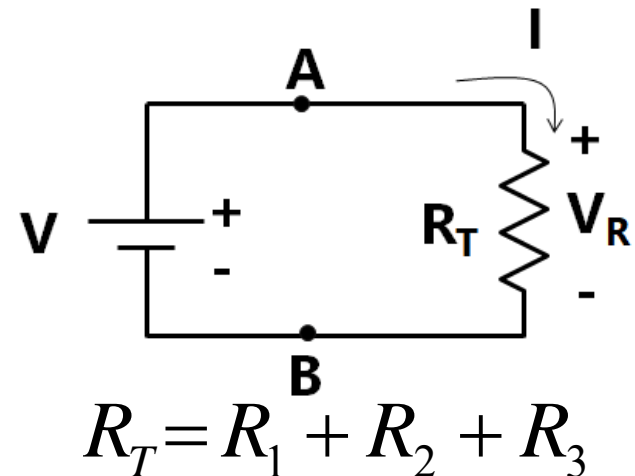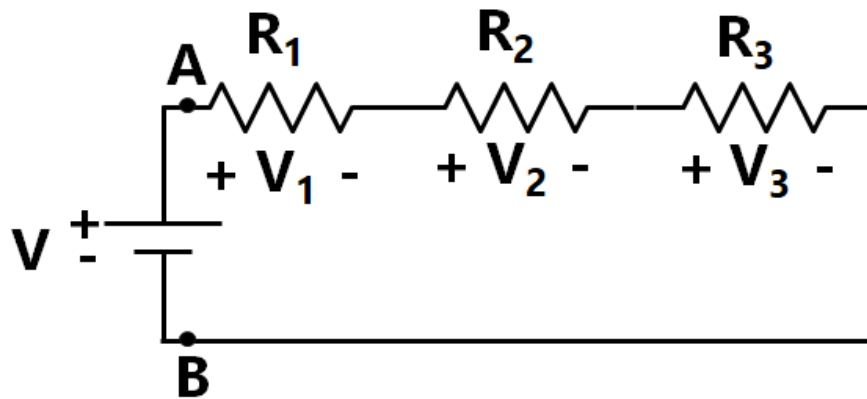- To calculate the voltage drop across the each resistance in a series circuit



- Current through the circuit I is given by

$$I = \frac{V}{R_T} = \frac{V_R}{R_T}$$

Resistances Connected in Series-Voltage Divider Rule


- Voltage drop V_1 across resistor R_1 is given by $V_1 = IR_1$.
- Similarly, $V_2 = IR_2$, $V_3 = IR_3$
- $IR_1 + IR_2 + IR_3 = IR_T = V$
- Thus, voltage drop across R_1 is given by

$$V_1 = IR_1 = \frac{V}{R_T} R_1 = \frac{R_1}{R_T} V$$

- Similarly,

$$V_2 = IR_2 = \frac{V}{R_T} R_2 = \frac{R_2}{R_T} V \quad V_3 = IR_3 = \frac{V}{R_T} R_3 = \frac{R_3}{R_T} V$$

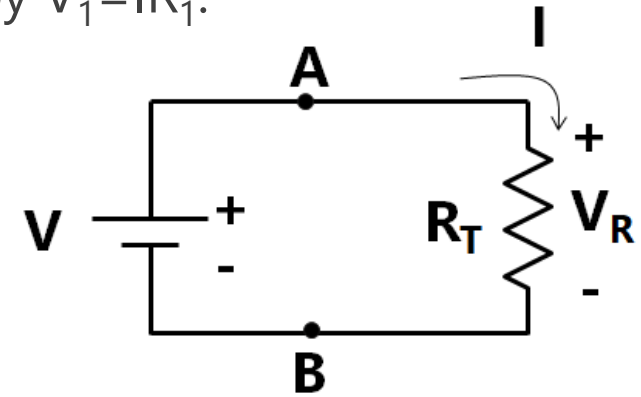- Thus, $V = IR_1 + IR_2 + IR_3 = \left(\frac{R_1}{R_T} + \frac{R_2}{R_T} + \frac{R_3}{R_T} \right) V$




$$R_T = R_1 + R_2 + R_3$$


The voltage drop is maximum across the largest resistor in the series combination

Resistances Connected in Series

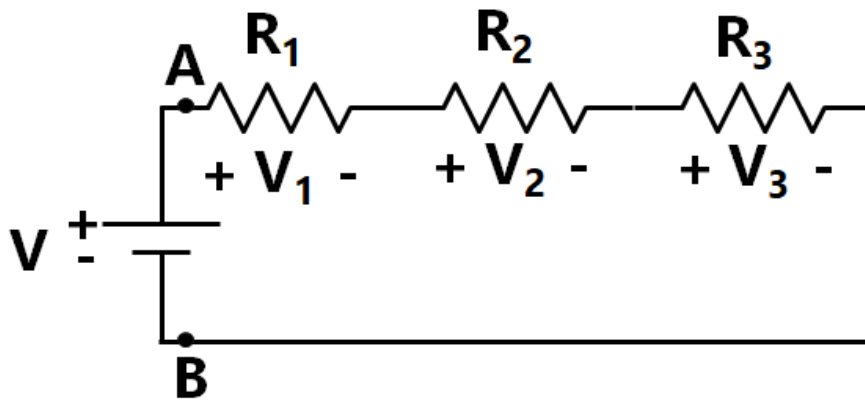- To calculate the voltage drop across the each resistance in a series circuit


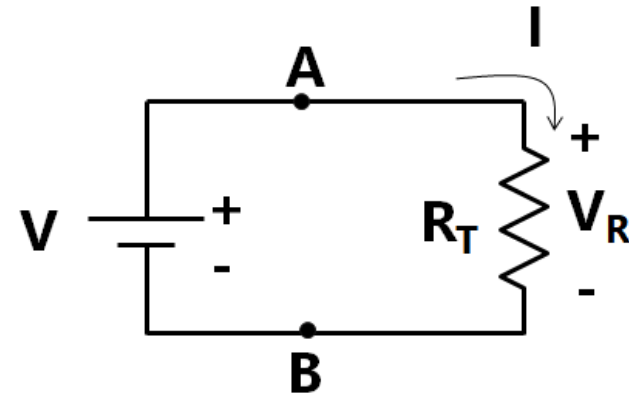
$$R_1 = 1 \text{ k}\Omega, R_2 = 5 \text{ k}\Omega, R_3 = 1.5 \text{ k}\Omega$$




$$I = \frac{V}{R_T} = \frac{15V}{7.5k\Omega} = 2mA$$

$$V_1 = IR_1 = 2V, V_2 = IR_2 = 10V, V_3 = IR_3 = 3V$$

$$R_2 (5k\Omega) > R_3 (1.5k\Omega) > R_1 (1k\Omega)$$

$$V_2 (10V) > V_3 (3V) > V_1 (2V) \quad V_R = V_1 + V_2 + V_3 = 2 + 10 + 3 = 15V = V$$


Parallel Connections

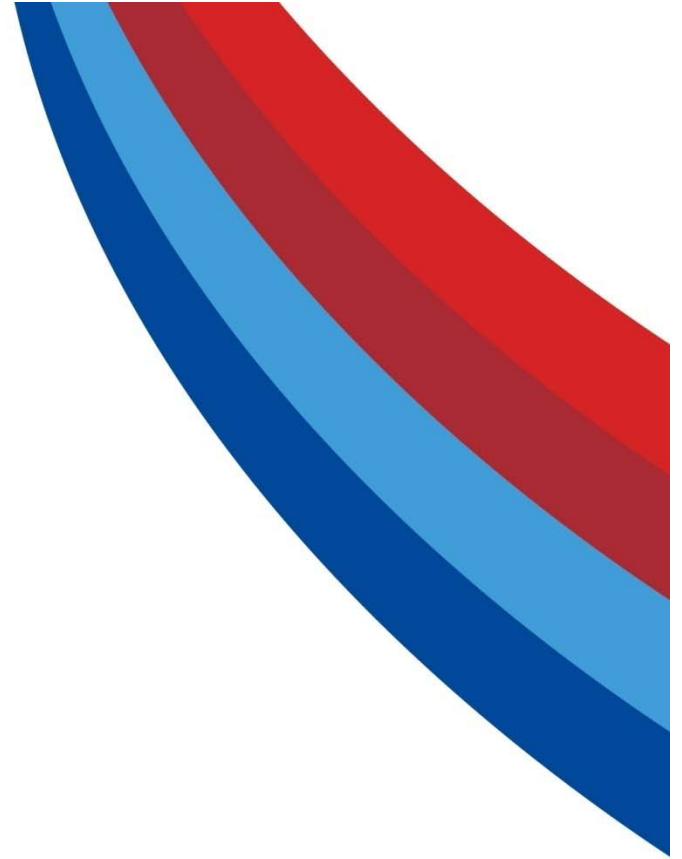

Parallel Connections


- Two elements or circuits or branches are in **parallel** if they have two **points in common**
- The total current before branching is sum of currents in the individual branches

$$I = I_1 + I_2$$

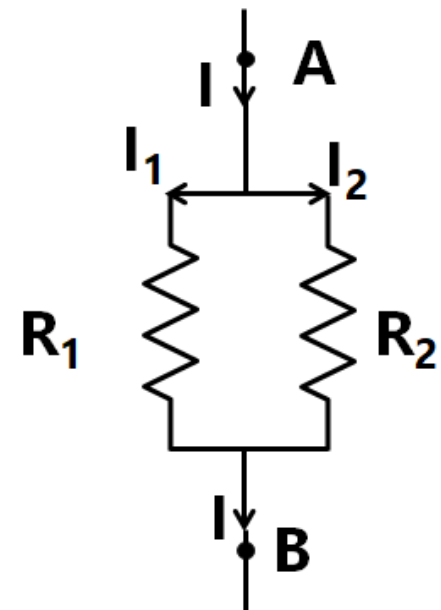

Parallel Connections

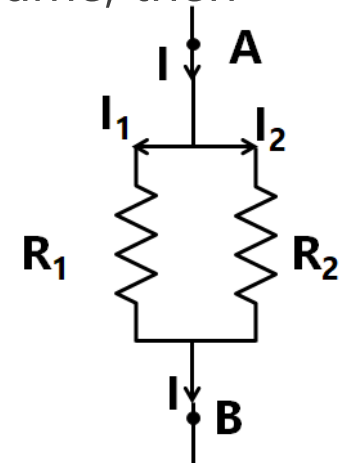- Two elements or circuits or branches are in **parallel** if they have two **points in common**
- Voltage across parallel elements is always same
- If two elements are in parallel the voltage across them must be same.
- If the voltage across two neighbouring elements is the same, then the two elements may not be in parallel



Equivalent Resistance of a Parallel Combination

- Let I be the total current and V_{AB} be the voltage between points **A** and **B** and R_T be the equivalent resistance between points **A** and **B**

- The total current I is given
$$I = \frac{V_{AB}}{R_T}$$


- The total current $I = I_1 + I_2 + I_3$

- Current through resistance R_1 is given by

$$I_1 = \frac{V_{AB}}{R_1}$$

- Similarly,
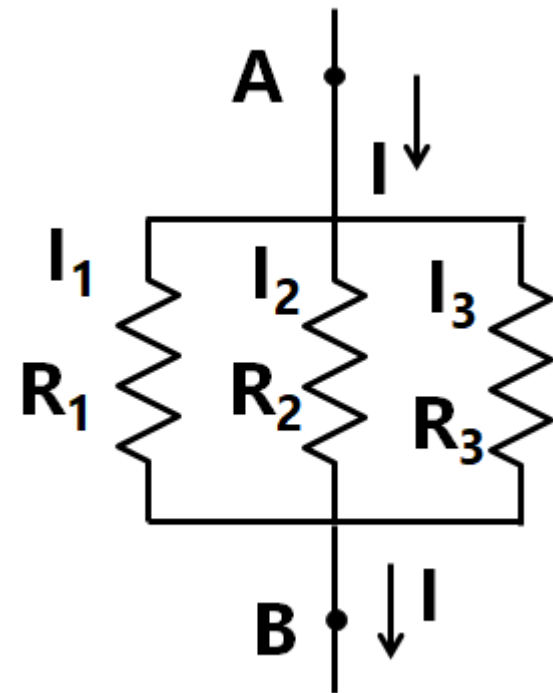
$$I_2 = \frac{V_{AB}}{R_2} \quad I_3 = \frac{V_{AB}}{R_3}$$




Equivalent Resistance of a Parallel Combination

➤ Thus

$$I = \frac{V_{AB}}{R_T} = I_1 + I_2 + I_3 = \frac{V_{AB}}{R_1} + \frac{V_{AB}}{R_2} + \frac{V_{AB}}{R_3}$$

$$\boxed{\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}}$$

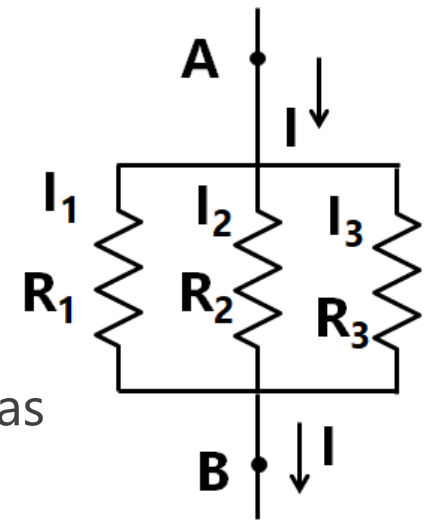➤ The large the value of resistance is, less the effect it has




Current Division

- Current I_1 through resistance R_1 is given by

$$I_1 = \frac{V_{AB}}{R_1}$$

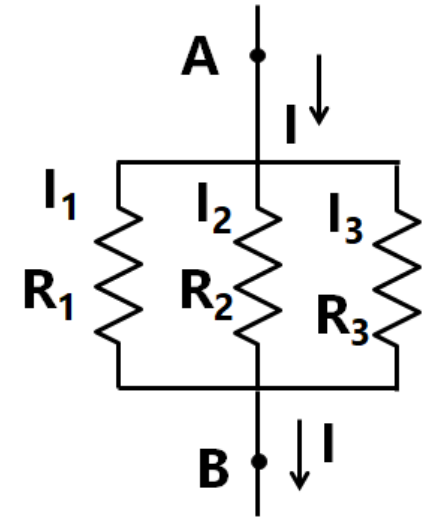- Substituting $I = \frac{V_{AB}}{R_T} \Rightarrow I_1 = \frac{IR_T}{R_1}$



$$\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \Rightarrow R_T = \frac{R_1 R_2 R_3}{R_2 R_3 + R_3 R_1 + R_1 R_2}$$


- Thus,
$$I_1 = \frac{R_2 R_3}{R_2 R_3 + R_3 R_1 + R_1 R_2} I$$

Current Division

$$I_1 = \frac{R_2 R_3}{R_2 R_3 + R_3 R_1 + R_1 R_2} I$$

$$I_2 = \frac{R_3 R_1}{R_2 R_3 + R_3 R_1 + R_1 R_2} I$$
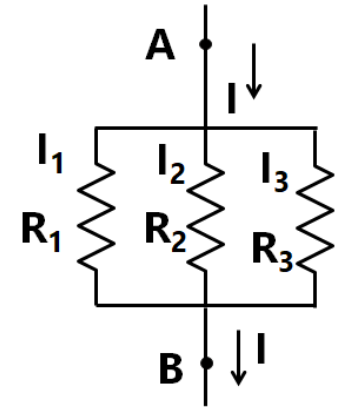
$$I_3 = \frac{R_1 R_2}{R_2 R_3 + R_3 R_1 + R_1 R_2} I$$



- The branch with largest resistance in a parallel combination has maximum current

Kirchhoff's Current Law

- The algebraic sum of currents entering and leaving a junction or region of a network is zero
- Let I_i be the currents that enter in to a junction and let I_o be currents leaving a junction. Then **KCL** states

$$\Sigma I_i = \Sigma I_o$$

- I_1 , I_2 and I_5 are entering junction or node "A"
- I_3 and I_4 are leaving junction or node "A"
- Thus, as per KCL, $I_1 + I_2 + I_5 = I_3 + I_4$

