

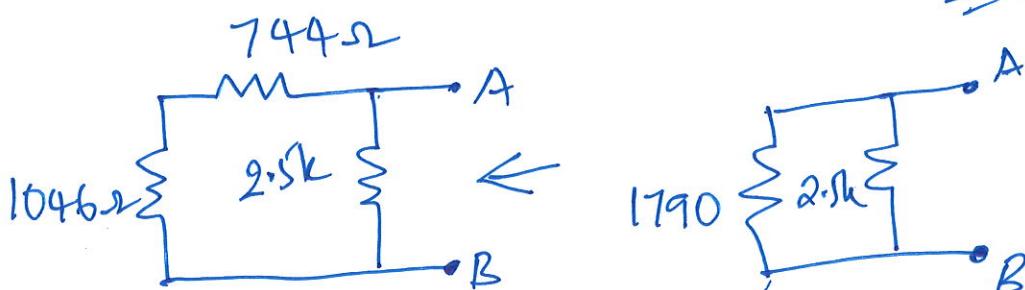
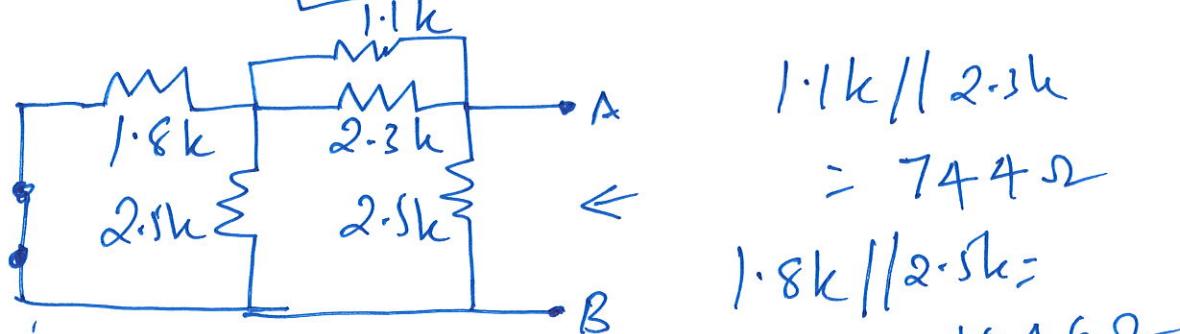
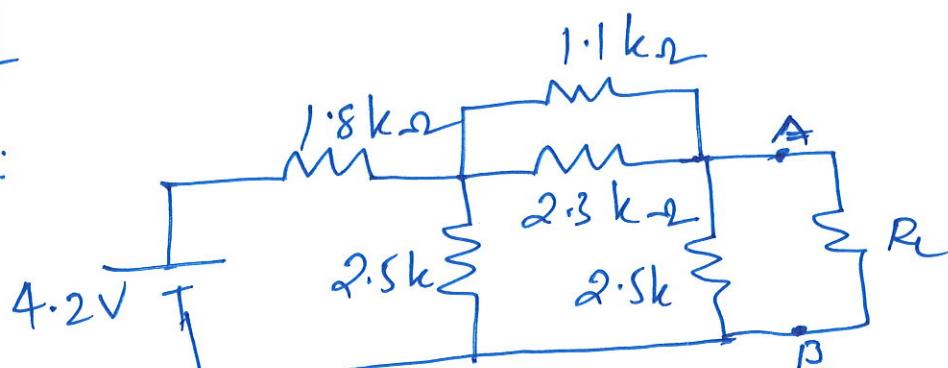


142SOLUTIONSFig. 1 R_{TH} :



$$R_{AB} = 1043\Omega = R_{TH}$$

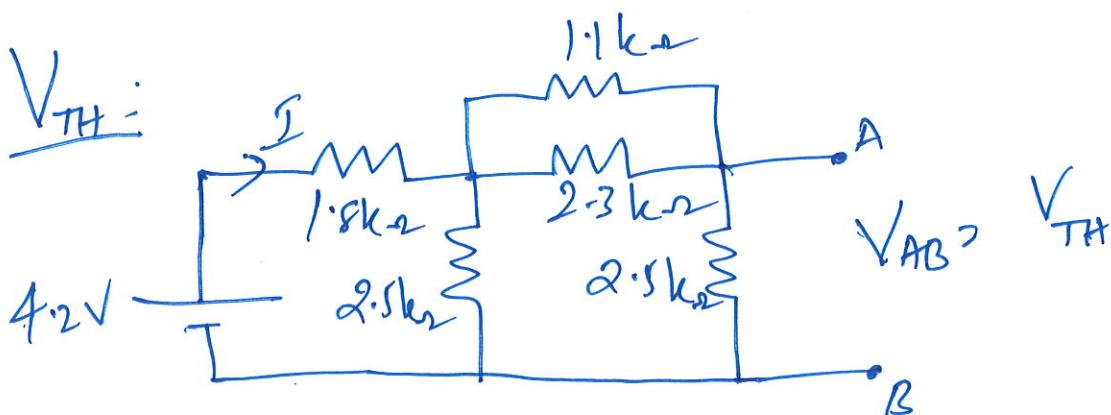

(2)

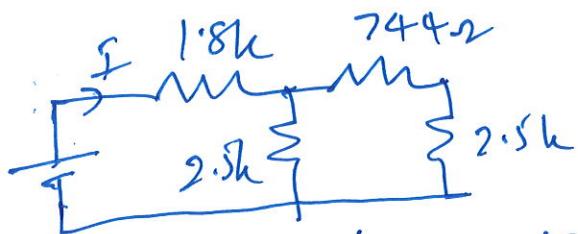

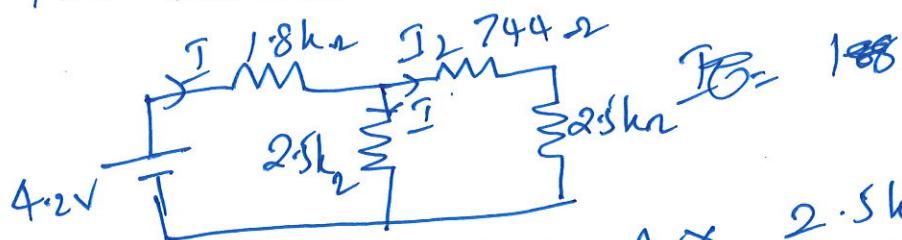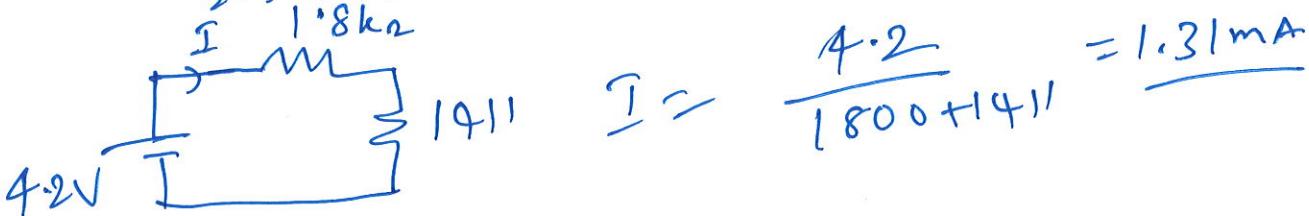
$$2.5k \parallel (7442 + 2.5k) = 1411\text{--}$$



$$I_2 = 1.31 \text{ mA} \times \frac{2.5k}{2.5k + 7442 + 2.5k}$$


$$= 0.57 \text{ mA}$$

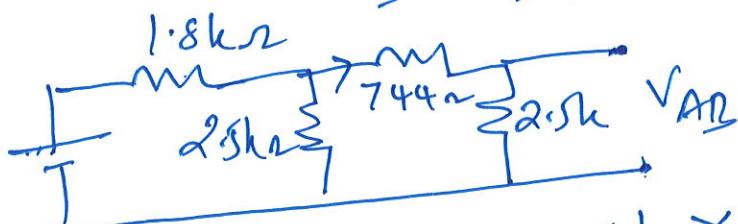

$$V_{2.5k\text{--}} = V_{AB} = 2.5k \times 0.57 \text{ mA} = 1.425 \text{ V}$$

$$V_{TH} = V_{AB} = 1.425 \text{ V}$$

$$R_{TH} = 1.043 \text{ k}\Omega$$

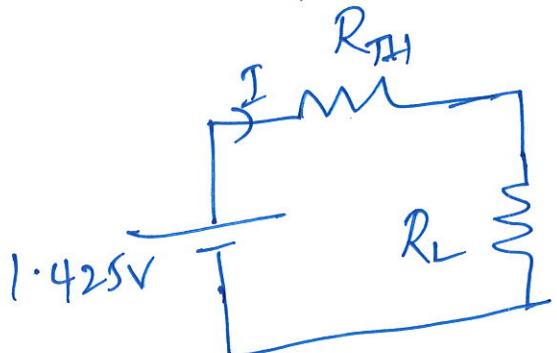

Maximum power is transferred

when $R_L = R_{TH}$.

$$\text{Thus, } R_L = 1.043 \text{ k}\Omega$$




$$I_L = \frac{1.425}{R_L + R_{TH}} = 0.683 \text{ mA}$$

$$V_L = 0.7125 \text{ V} \quad P_L = V_L I_L = 0.49 \text{ mW}$$

(3)


NORTON THEOREM

$$R_{TH} = R_N = 1043\ \Omega$$

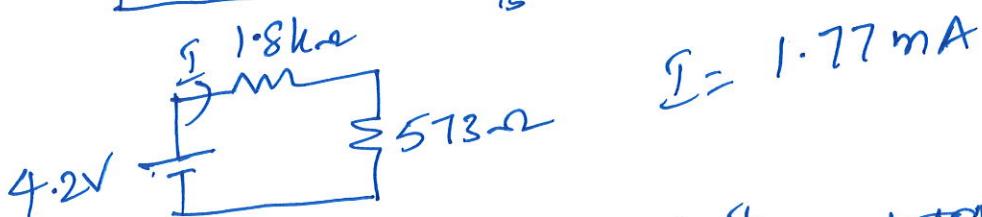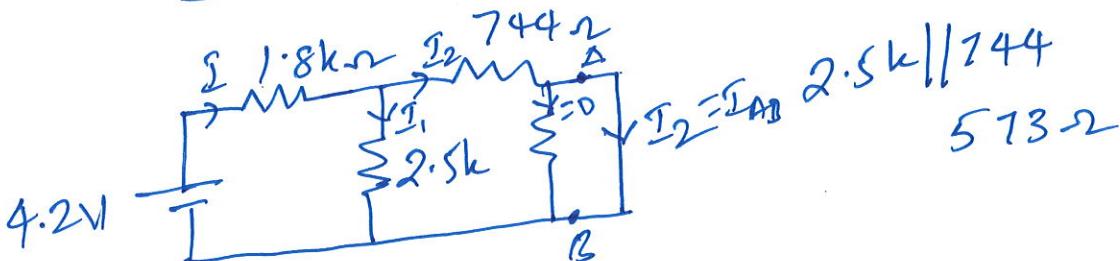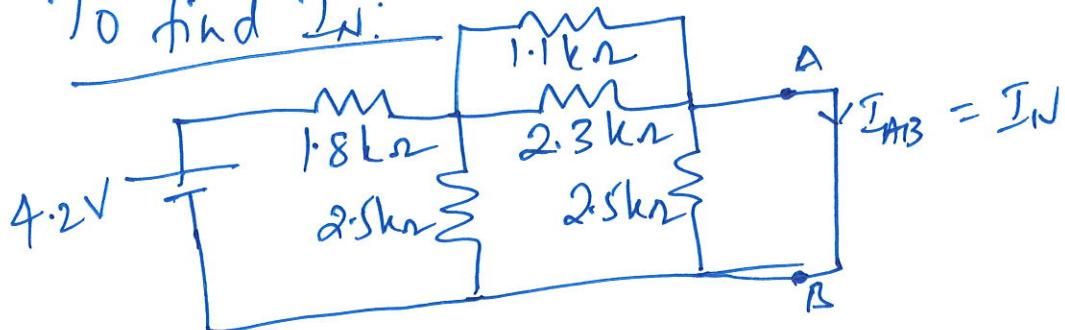To find I_{IN} :

$$I_{AB} = I_2 = \frac{1.77 \times 2.5k}{2500 + 744} = 1.36 \text{ mA}$$
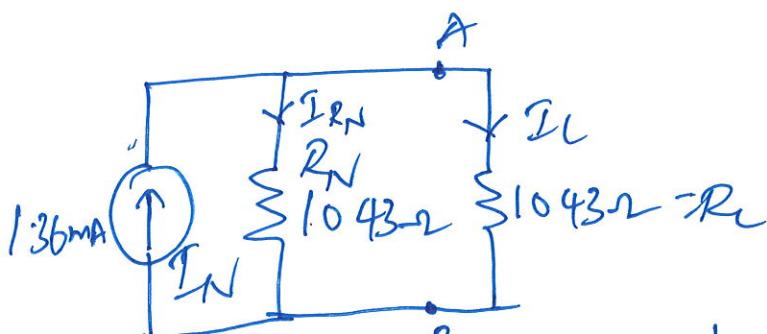
$$I_1 = \frac{1.77 \times 744}{2500 + 744} = 0.4059 \text{ mA} \approx 0.41 \text{ mA}$$






for maximum power transfer $R_L = R_N$

$$I_L = \frac{1.36 \text{ mA} \times R_L}{R_L + 1043\ \Omega} = 0.68 \text{ mA}$$


$$V_L = 0.71 \text{ V} \quad P_L = I_L V_L = 0.48 \text{ mW}$$

(4)

Fig. 2

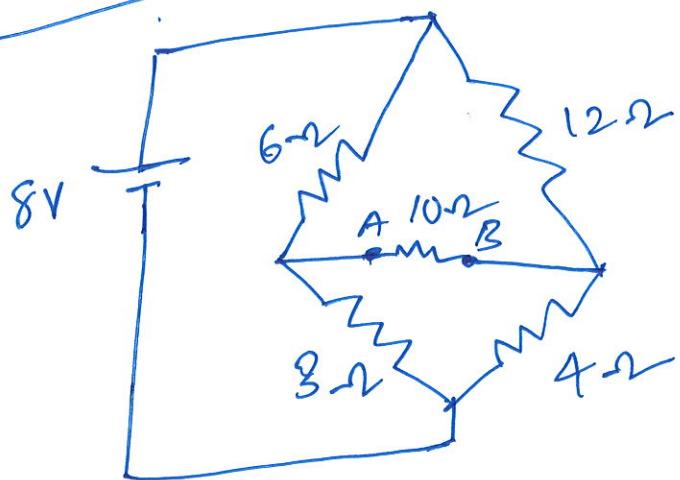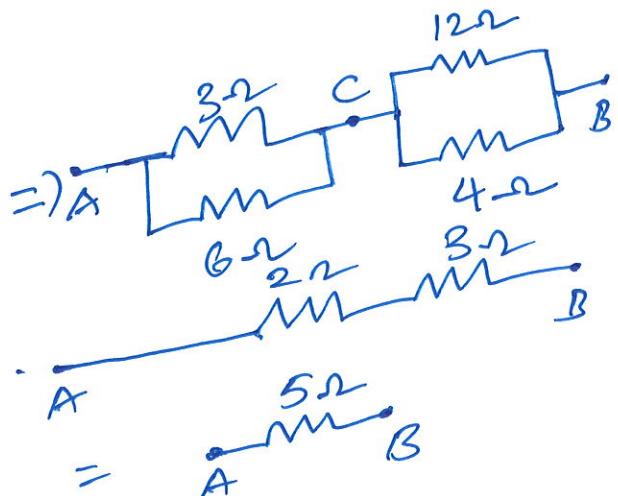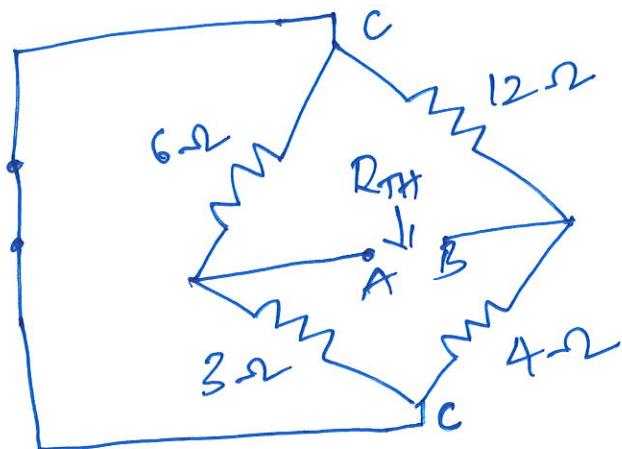
Thevenin's EquivalentTo find R_{TH} .

$$R_{AB} = R_{TH} = 5\Omega$$

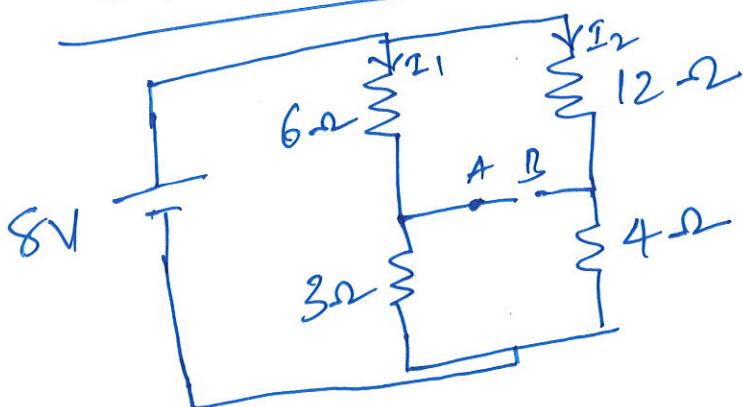To find V_{TH} 

$$I_1 = \frac{8}{6+3} = \frac{8}{9} A$$

$$I_2 = \frac{8}{12+4} = 0.5 A$$

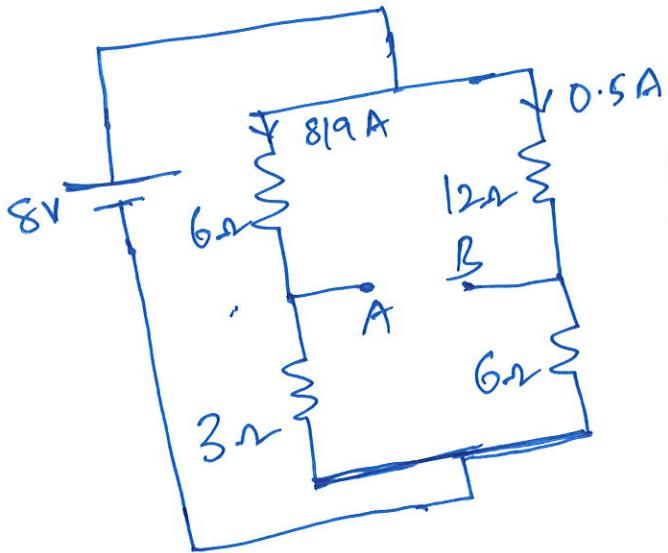


$$\left. \begin{array}{l} \text{Voltage across } 6\Omega = 5.33V \\ \text{Voltage across } 3\Omega = 2.67V \end{array} \right\}$$

$$\left. \begin{array}{l} \text{Voltage across } 12\Omega = 6V \\ \text{Voltage across } 6\Omega = 2V \end{array} \right\}$$

Let the bottom 3Ω and 6Ω are connected to ground. Then $V_A = 2 \frac{67}{87}V$ $V_B = 2V$

$$V_{AB} = 2.7 - 2 = \underline{0.67V}$$

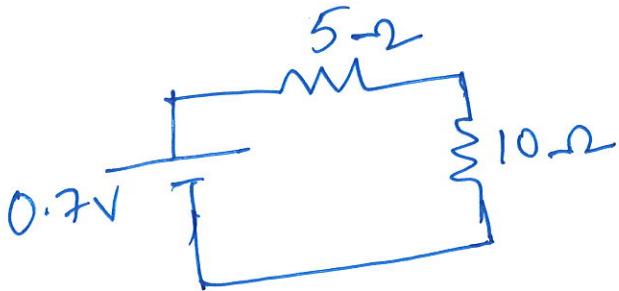


$$I_V = \frac{0.67}{15} = 44.7mA$$

$$V_L = 0.447V$$


$$P_L = V_L I_V = 20mW$$

Norton Equivalent

$$R_N = R_{TH} = 5\Omega$$

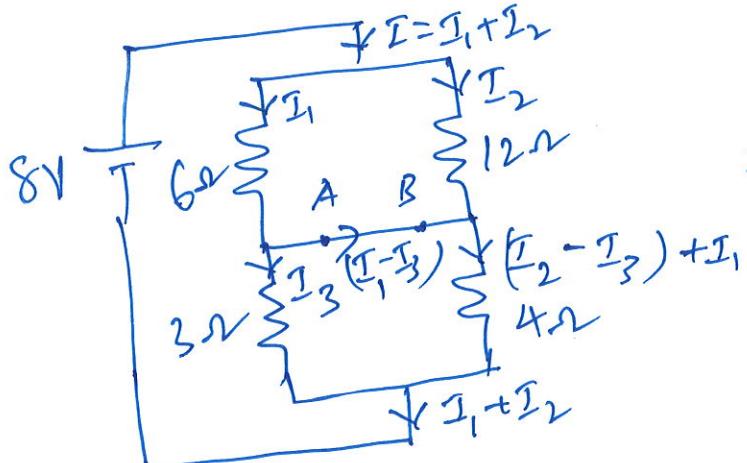

$$I_3 = \frac{2.4}{3\Omega} = 0.8A$$

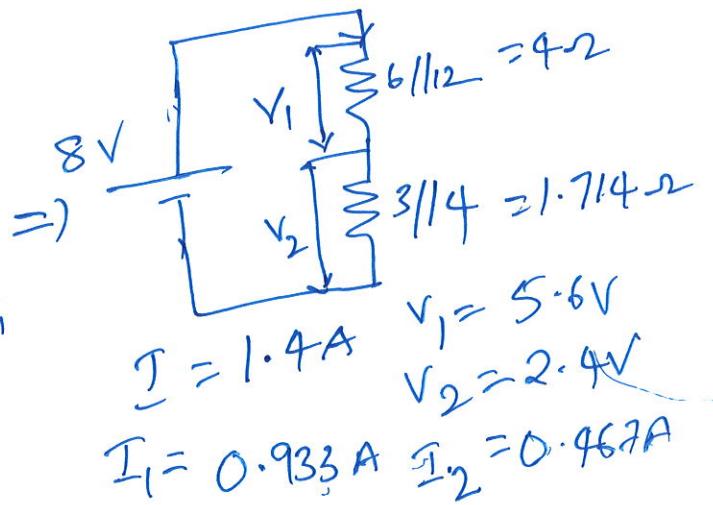

$$\begin{aligned} I &= 1.4A & V_1 &= 5.6V \\ I_1 &= 0.933A & V_2 &= 2.4V \\ I_2 &= 0.467A \end{aligned}$$

$$I_{AB} = I_1 - I_3 = 0.933 - 0.8 = \underline{\underline{0.133A}} \quad (6)$$

$$I_N = I_{AB} = 0.133A$$



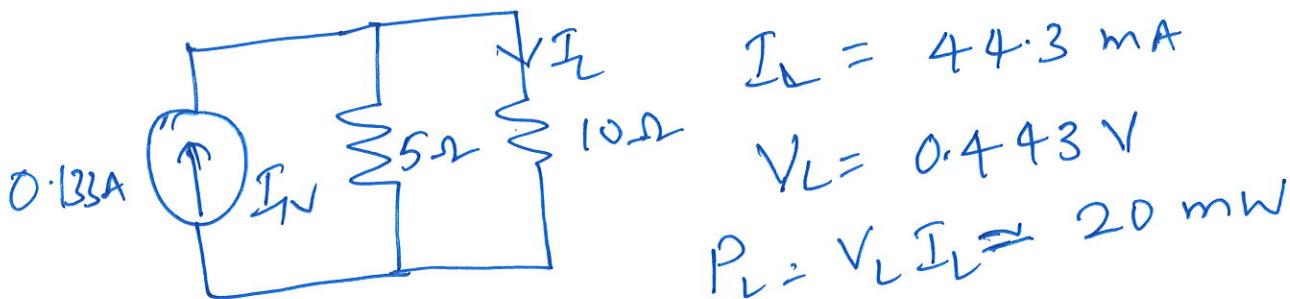


Fig. 3

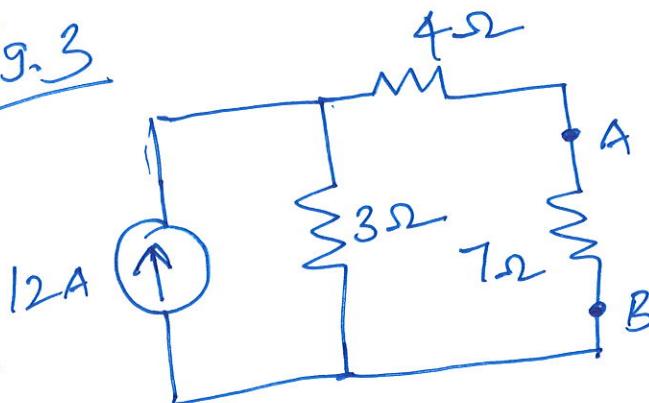

Thevenin's Equivalent:


To find R_{TH} :

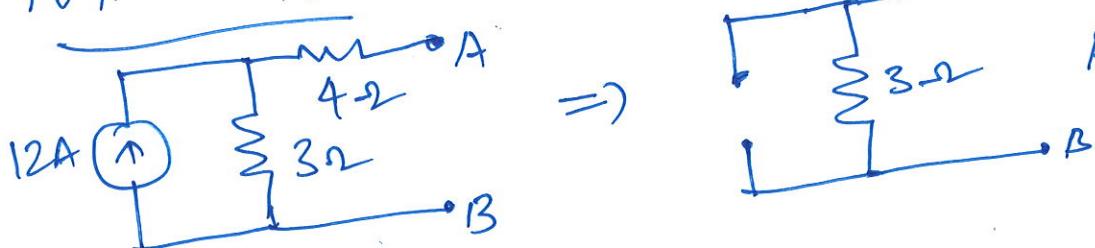

$$R_{TH} = R_{AB} = 7\Omega$$


$$R_{AB} = 7\Omega$$

To find V_{TH}

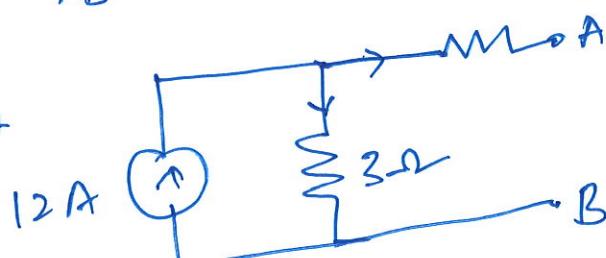

$$V_{AB} = V_{3\Omega} = 12 \times 3 = 36 \text{ V} = V_{TH}$$

(7)

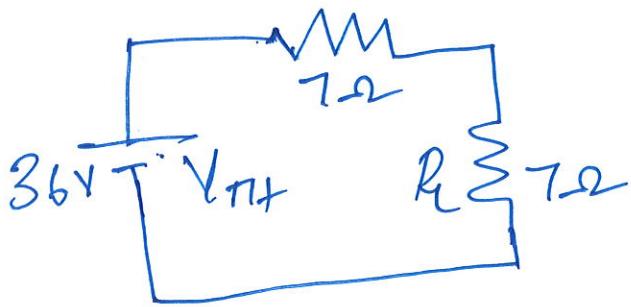

$$V_L = 18V$$


$$I_L = 2.57A$$

$$P_L = V_L I_L = \underline{46.286 W}$$

NORTON'S EQUIVALENT


$$R_N = R_{TH} = 7\Omega$$

To find I_N :

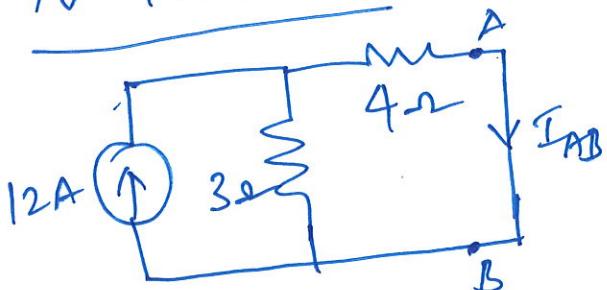

$$I_{4\Omega} = \frac{12 \times 3}{3+4} = 5.14A$$
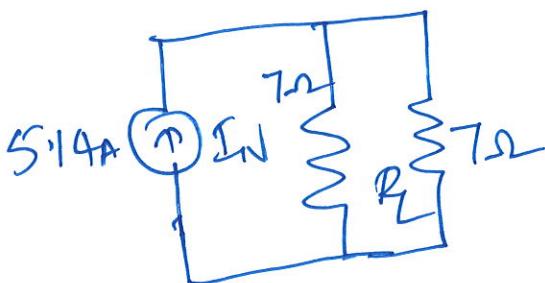
$$I_N = I_{4\Omega} = \underline{5.14A}$$




$$I_L = \frac{5.14 \times 7}{7+7} = 2.57A$$

$$V_L = 2.57 \times 7 = 18V$$





$$P_L = V_L \cdot I_L = \underline{46.286 W}$$

Fig. 4

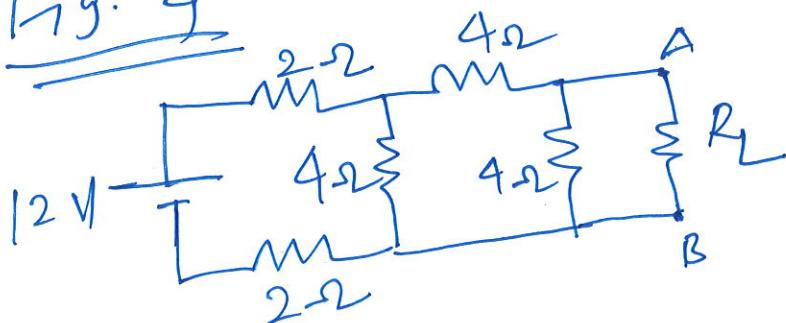


(8)

THEVINVININ'S EQUIVALENT

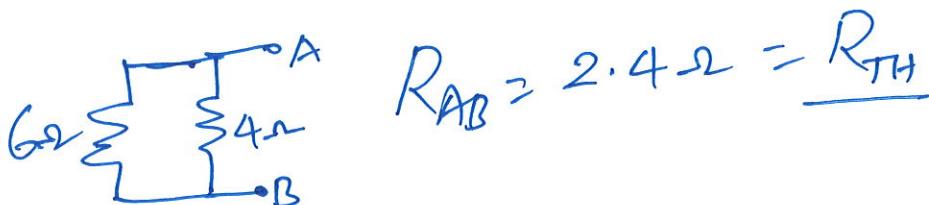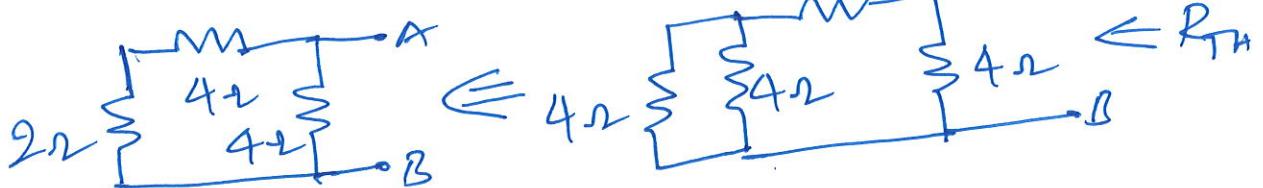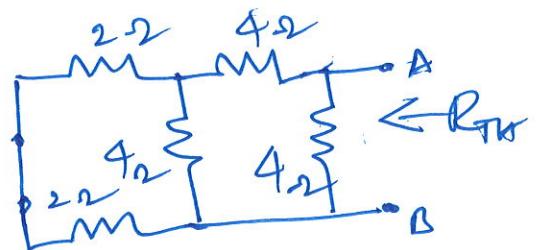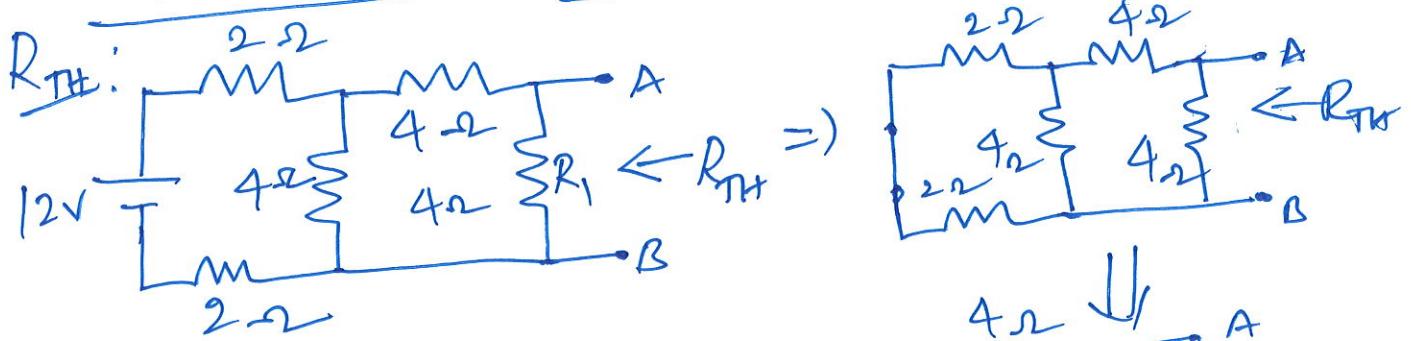


To find V_{TH} :

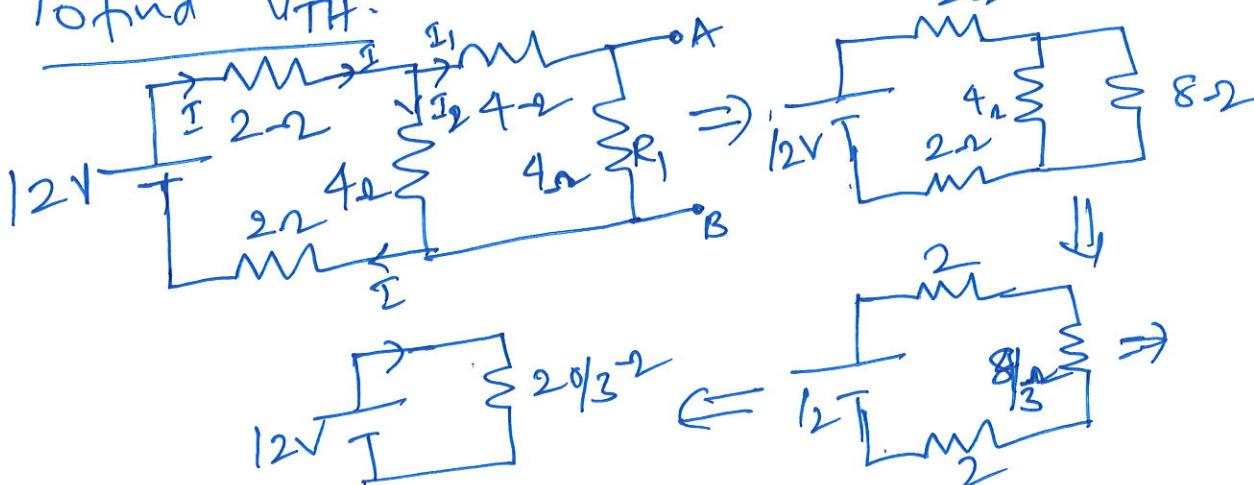

$$I = \frac{12}{20/3} = \frac{9}{5} = 1.8A$$

$$I_2 = \frac{1.8 \times 4}{4+8} = 0.6A \quad V_{4\Omega} = 0.6 \times 4 = 2.4V$$

$$V_{R_1} = V_{AB} = 2.4V = V_{TH}$$

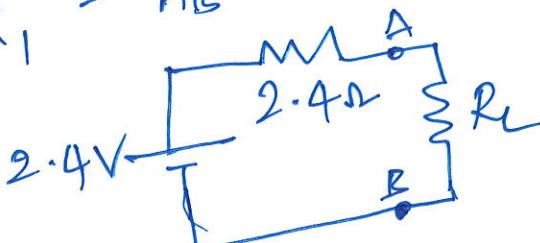

for maximum power transfer

(9)

$$R_L = R_{TH} = 2.4\Omega$$

$$V_L = \frac{2.4V}{2.4+2.4} = 1.2V$$



$$I_L = \frac{V_L}{R_L} = \frac{1.2}{2.4} = 0.5A$$

$$P_L = V_L I_L = 0.6W$$

Norton Equivalent


$$R_N = R_{TH} = 2.4\Omega$$

To find I_N :

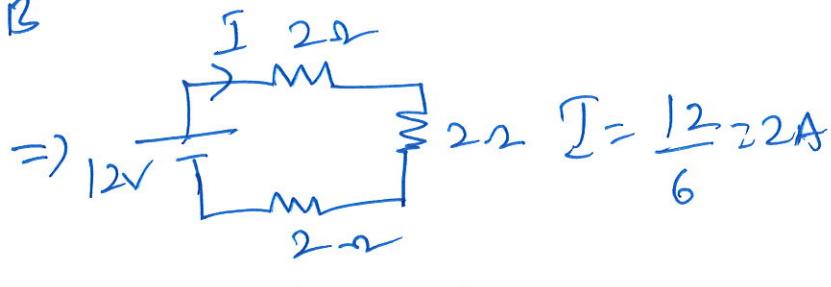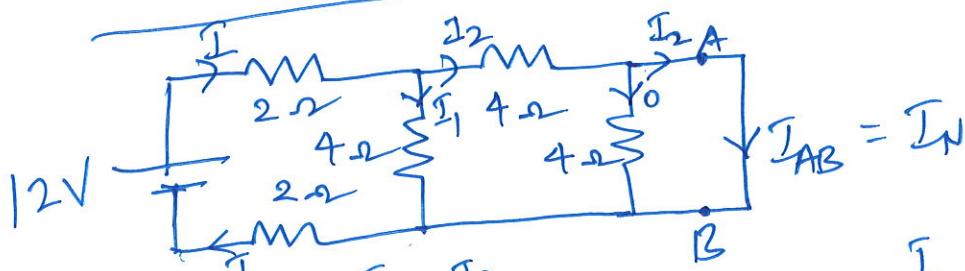

$$I_2 = \frac{2 \times 4}{4+4} = 1A$$

$$I_2 = I_{AB} = I_N = 1A$$

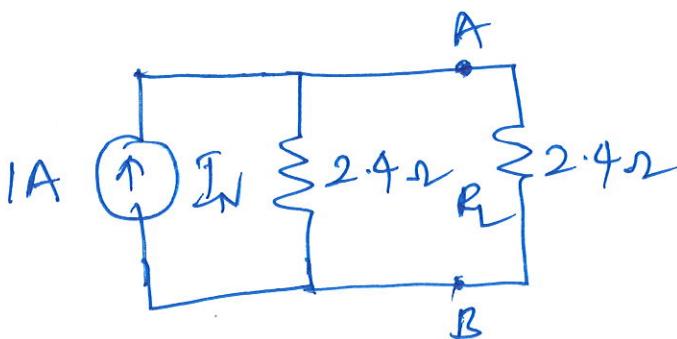

for Maximum power transfer,

$$R_L = R_S = 2.4\Omega$$


$$I_L = \frac{1 \cdot 2.4}{2.4 + 2.4} = \underline{\underline{0.5 \text{ A}}}$$

(10)

$$V_L = I_L R_L = 0.5 \times 2.4 = \underline{\underline{1.2 \text{ V}}}$$



$$P_L = V_L I_L = \underline{\underline{0.6 \text{ W}}}$$

Fig. 5

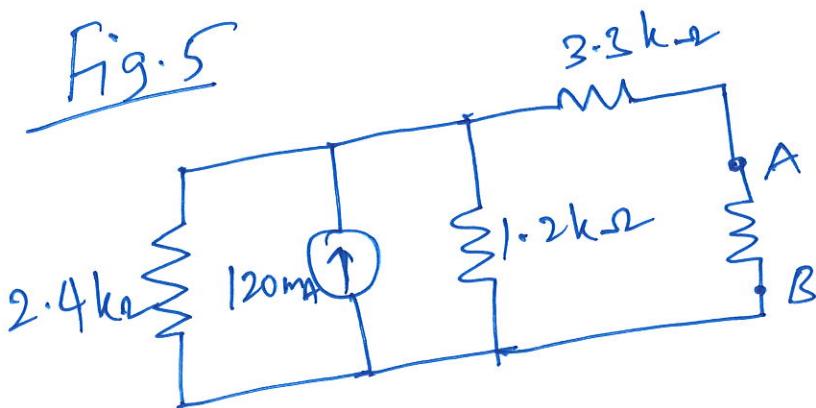

TAEYININ'S EQUIVALENT


To find R_{TH} :

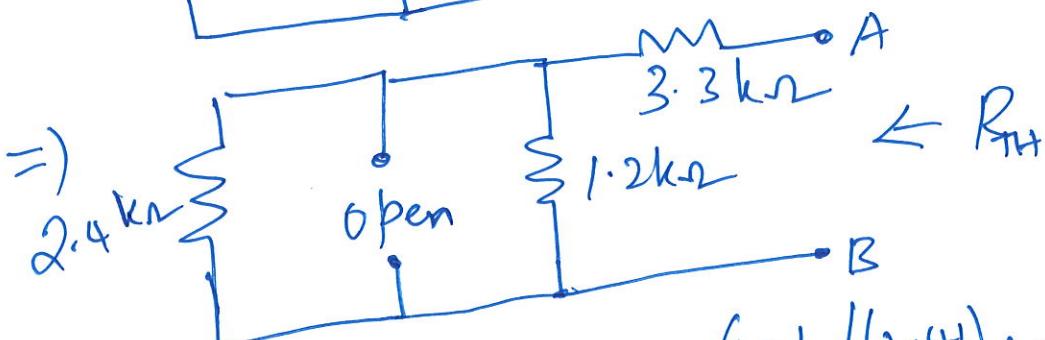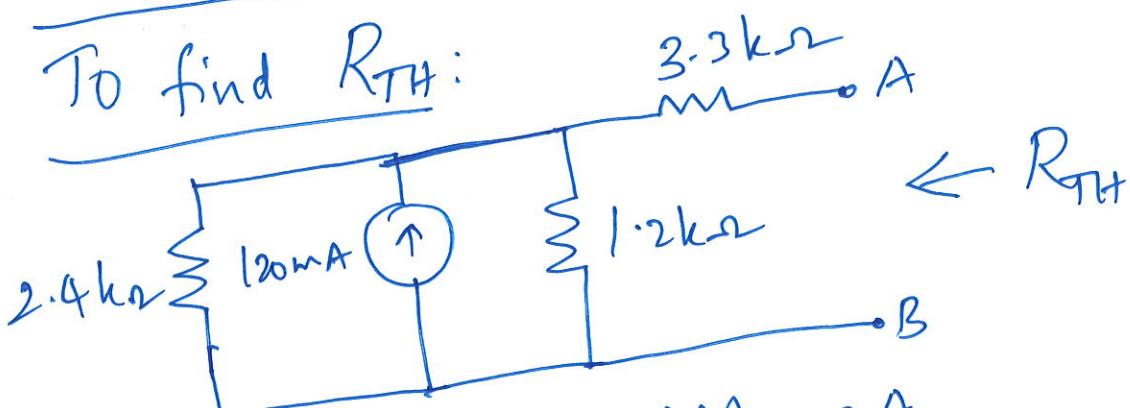

$$R_{AB} = 3.3\text{k}\Omega + \frac{(1.2\text{k})(2.4\text{k})}{1.2\text{k} + 2.4\text{k}} = 3.3\text{k}\Omega + 0.8\text{k}\Omega = 4.1\text{k}\Omega$$

$$R_{TH} = R_{AB} = 4.1\text{k}\Omega$$

(11)

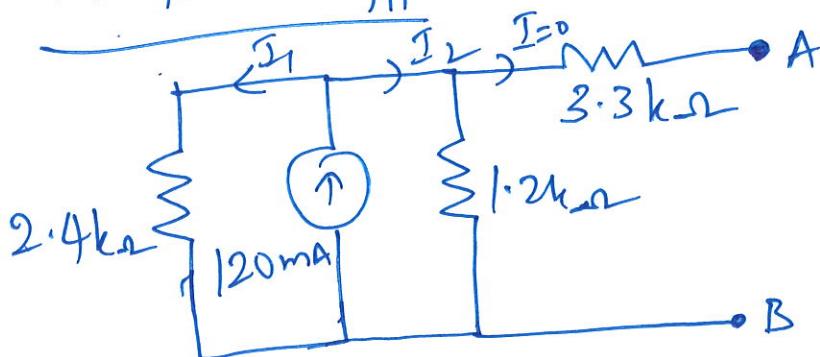
To find V_{TH} 

$$V_{AB} = V_{TH}$$

$$I_2 = \frac{120 \text{ mA} \times 2.4 \text{ k}\Omega}{(2.4 \text{ k} + 1.2 \text{ k})\Omega} = 80 \text{ mA}$$

$$V_{AB} = V_{1.2 \text{ k}\Omega} = 80 \text{ mA} \times 1.2 \text{ k}\Omega = \underline{96 \text{ V}}$$
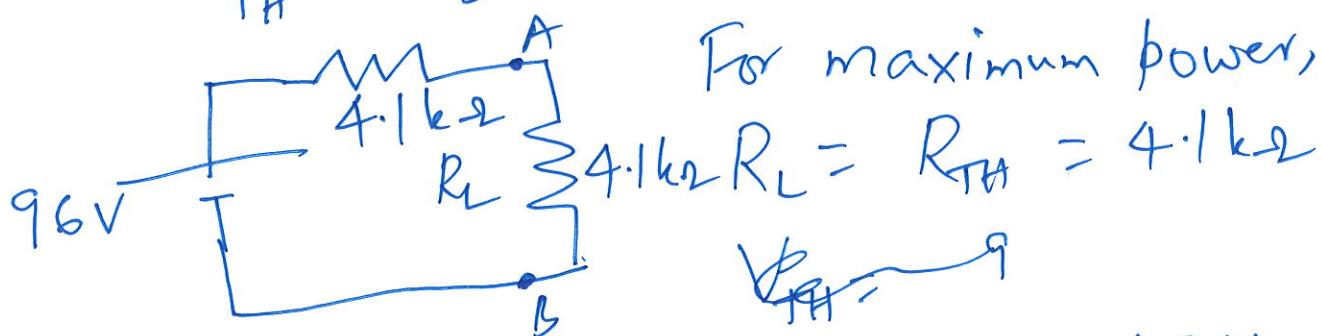
$$V_{TH} = V_{AB} = \underline{96 \text{ V}}$$



For maximum power,

$$4.1 \text{ k}\Omega R_L = R_{TH} = 4.1 \text{ k}\Omega$$

$$V_L = \frac{96 \times 4.1 \text{ k}\Omega}{4.1 \text{ k}\Omega + 4.1 \text{ k}\Omega} = 48 \text{ V}$$


$$I_L = \frac{V_L}{R_L} = 11.707 \text{ mA}$$

$$P_L = V_L I_L = \underline{0.56 \text{ W}}$$

NORTON'S EQUIVALENT

$$R_N = R_{TH} = 4.1 \text{ k}\Omega$$

(12)

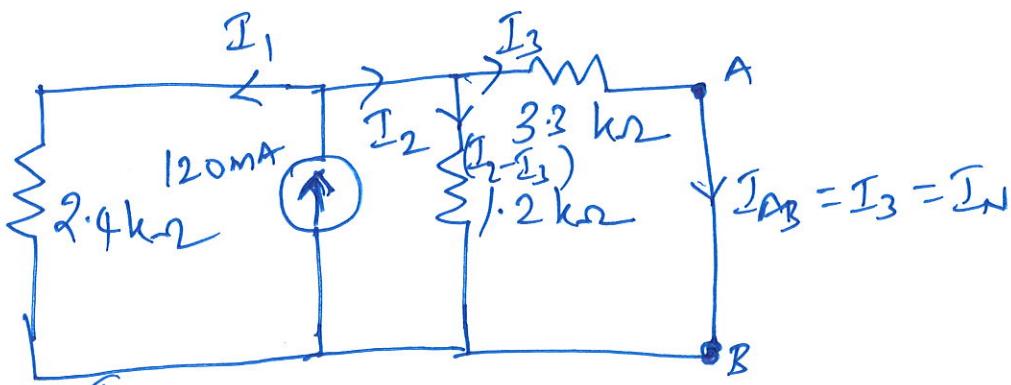


To find
 $I_2 : (3.3k \parallel 1.2k) = 0.88k\Omega$

$$I_2 = \frac{120mA \times 2.4k\Omega}{2.4k\Omega + 0.88k\Omega} = 87.8mA$$

$$I_3 = \frac{87.8 \times 1.2k}{1.2k + 3.3k} = 23.41mA = I_N$$
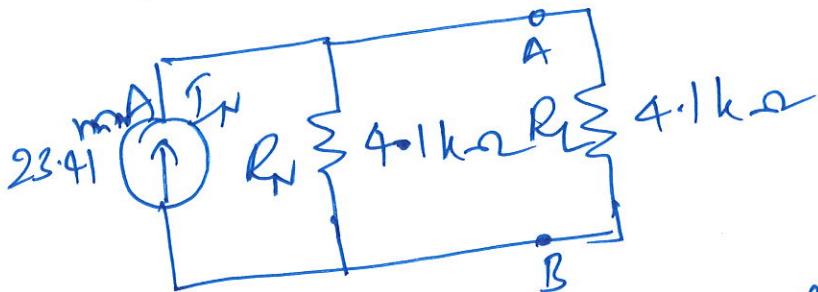
$$I_N = I_3 = I_{AB} = \underline{23.41mA}$$



Maximum power is transferred when $R_L = R_N = 4.1k\Omega$


$$I_L = \frac{23.41mA \times 4.1k\Omega}{4.1k\Omega + 4.1k\Omega} = 11.707mA$$

$$V_L = I_L R_L = 48V$$

$$P_L = V_L I_L = 48 \times 11.707mA = \underline{0.56mW}$$




Fig. 6

(B)

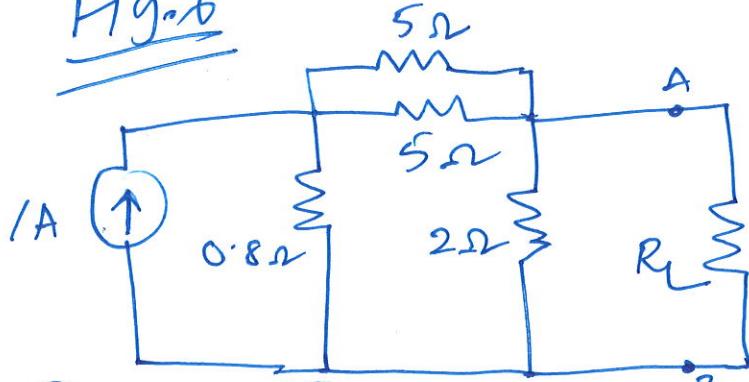

THEVENIN'S EQUIVALENT:



R_{TH} :

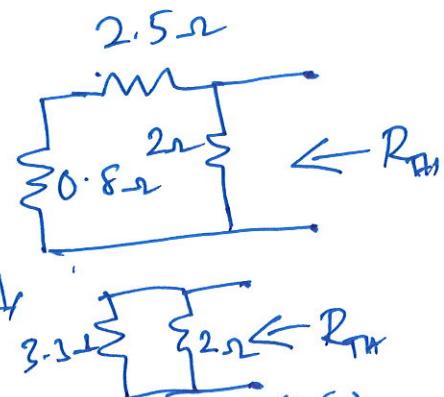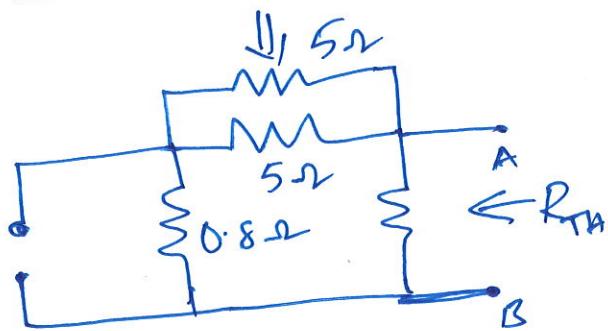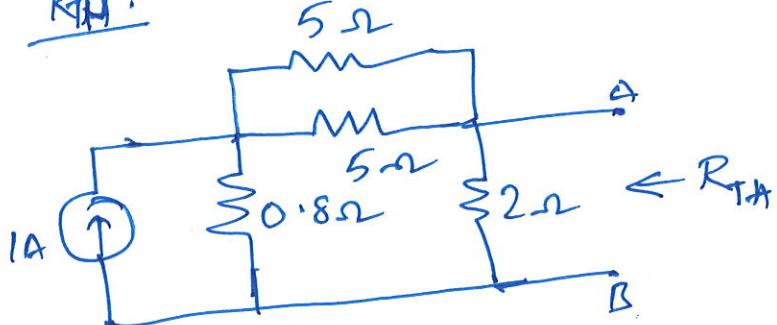

$$R_{TH} = 3.3 \parallel 2 = 1.245 \Omega$$


$$(1 \Omega) \Rightarrow (5 \parallel 5)$$

V_{TH} :

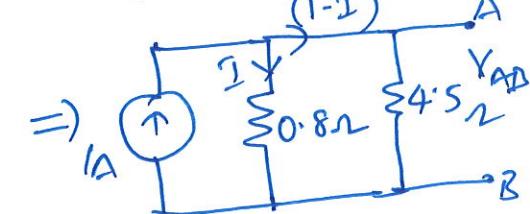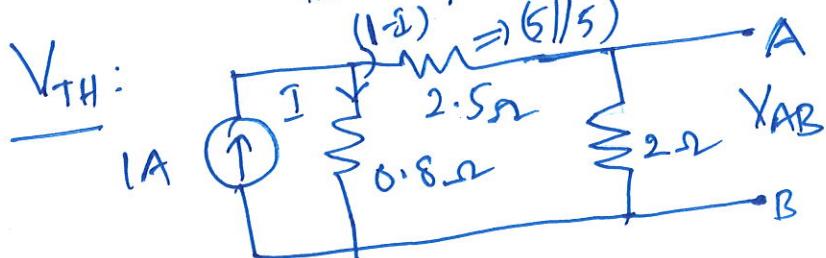

$$I = \frac{1 \times 0.8}{0.8 + 4.5} = 0.151 A$$
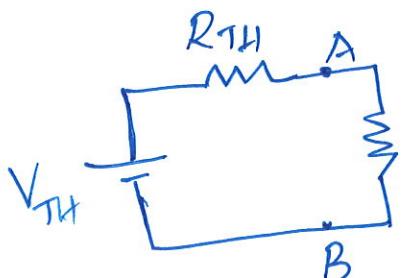
$$V_{2\Omega} = 0.151 \times 2 = \underline{0.302 V} = V_{AB} = V_{TH}$$



$$R_{TH} = 1.245 \Omega \quad I_L = 0.121 A$$

$$V_{TH} = 0.302 V \quad P_L = 18.31 mW$$

($V_L \cdot I_L$)


for maximum power transfer

$$R_L = R_{TH} = 1.245 \Omega$$

(14)

Norton Equivalent


$$R_N = R_{TH} = 1.245 \Omega$$

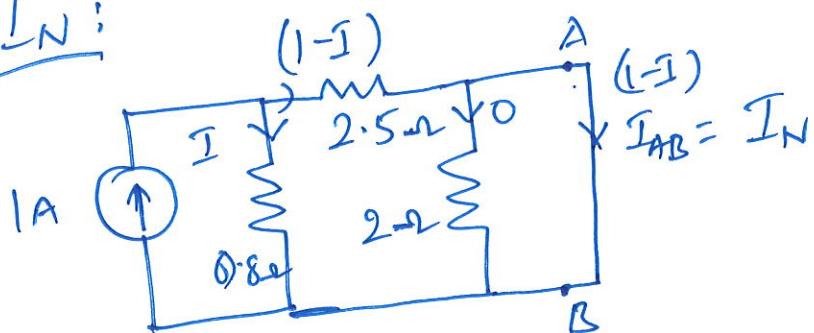 I_N :

$$I_{AB} = 1 - \frac{2.5}{3.3} \times 1 = 0.2424 \text{ A}$$

- i) Current division between 0.8Ω and 2.5Ω
ii) No I through 2Ω

Norton Equivalent:

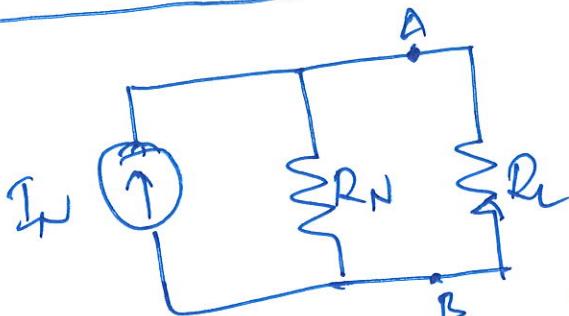

$$I_N = 0.2424 \text{ A}$$

$$R_N = 1.245 \Omega$$

$R_L = R_N$ (for maximum power transfer)

$$I_L = \frac{0.2424 \times 1.245}{1.245 + 1.245}$$

$$= 0.121 \text{ A}$$

$$V_L = I_L R_L = 0.151 \text{ V}$$

$$P_L = V_L I_L = 18.3 \text{ mW}$$