




BENNETT
UNIVERSITY
A TIMES GROUP INITIATIVE

Filter Circuits

EECE105L

Dr. Rama Komaragiri

Filters

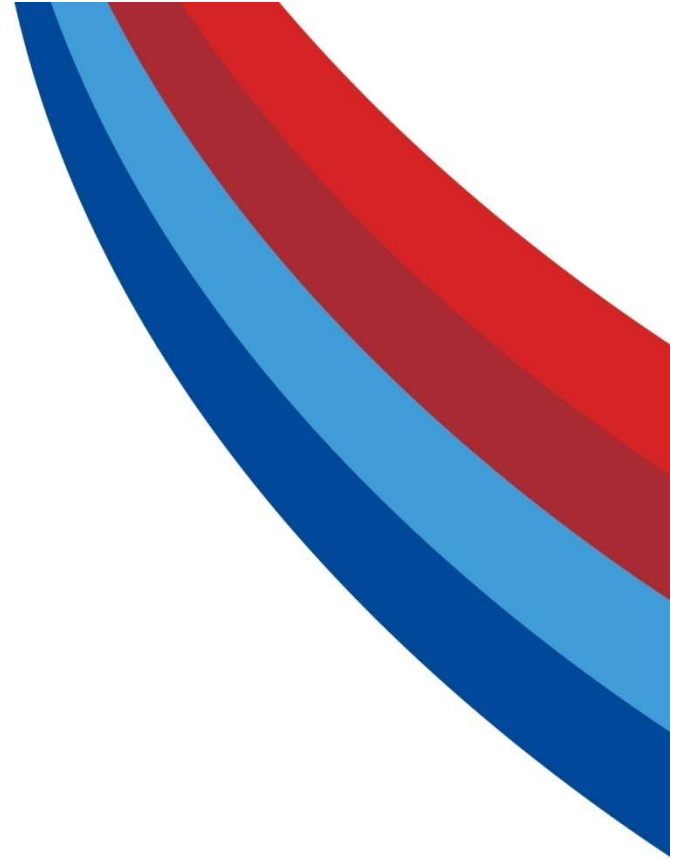

Need of Filters

- Circuits that perform signal processing functions are *filters*
- Filters are specifically used to
 - remove unwanted frequency components from the signal
 - to enhance wanted ones
 - or both.
- Filters are essential building blocks in many systems,
 - Example: used in communication and instrumentation systems
- A common need for filter circuits is in high-performance stereo systems, where certain ranges of audio frequencies need to be amplified or suppressed for best sound quality and power efficiency


What a Filter Does?



- Filter is an electrical network that modifies the amplitude and phase characteristics of a signal with respect to frequency
- A filter will not add any extra frequency component or delete any frequency component.
- A filter changes the relative amplitudes of various frequency components and their phase relationships.
- In electronic systems, filters are useful in emphasizing signals in certain frequency ranges and reject signals in other frequency ranges.
- A filter has a gain which is dependent on signal frequency.

What a Filter Does?

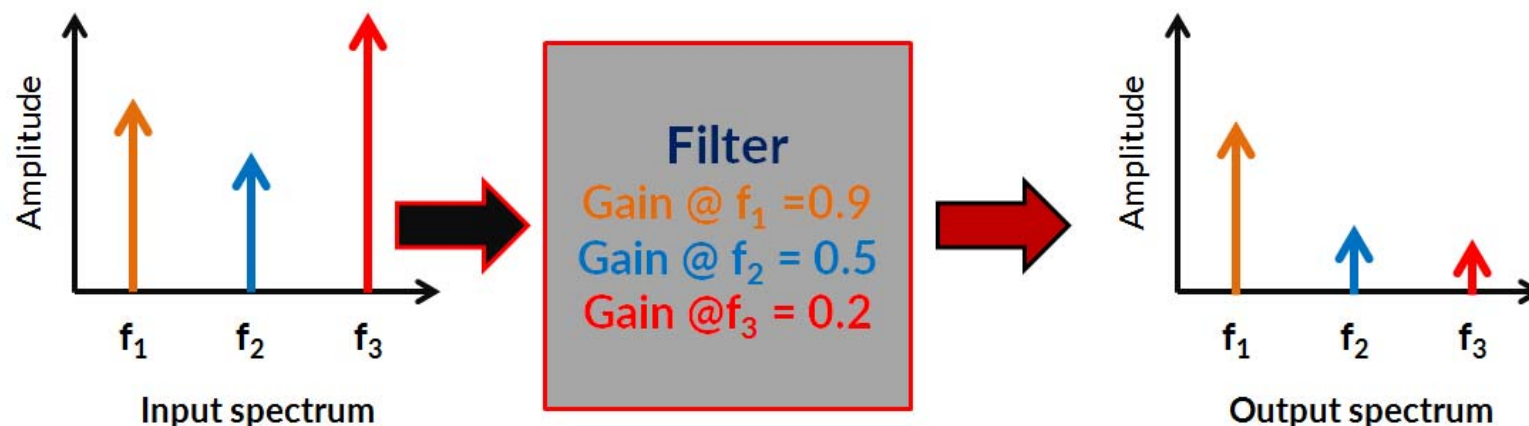- Consider a signal with frequency f_1 is contaminated with unwanted signals at f_2 and f_3
- Consider when the signal is passed through a circuit that has very low gain at f_2 and f_3 when compared to f_1
- While the useful signal component (f_1) remains, the undesired signal components (f_2 and f_3) are removed



What a Filter Does?

- Relative to signal at frequency f_1 , once the signals at frequencies f_2 and f_3 are sufficiently attenuated, the performance of the filter is considered to be satisfactory
- Different types of filters
 - **Low-pass filter:** low frequencies are passed, high frequencies are attenuated.
 - **High-pass filter:** high frequencies are passed, low frequencies are attenuated.
 - **Band-pass filter:** only frequencies in a frequency band are passed.
 - **Band-stop filter or band-reject filter:** only frequencies in a frequency band are attenuated.
 - **Notch filter:** rejects just one specific frequency - an extreme band-stop filter.
 - **Comb filter:** has multiple regularly spaced narrow pass-bands giving the band-form the appearance of a comb.
 - **All-pass filter:** all frequencies are passed, but the phase of the output is modified.

Study of Filter


- Filter is characterized by two important observations
 - Transfer Function or Transfer Characteristics: A mathematical function describing the output response of a filter system to the input or stimulus
 - Transfer function in filters is studied as a frequency response
 - Phase response: How the phase of filter changes with frequency
- The order of the filter is decided by the order of the differential equation that need to be solved.
 - 1st order differential equation- 1st order filter
 - 2nd order differential equation- 2nd order filter
- Important properties of filter
 - 3 dB Frequency or cut-off frequency

Filter - Important Characteristics

- Transfer function ($H(\omega)$): is a mathematical representation of a filter which describes the relation between input and output.
- Cut-off Frequency (f_c) or 3-dB frequency: The frequency at which the transfer function becomes half.
- Transfer Characteristics: A plot between $H(\omega)$ Vs. ω .
- Phasor diagrams: Plots the phase of gain at different frequencies.

RC Filters


RC Low Pass Filter

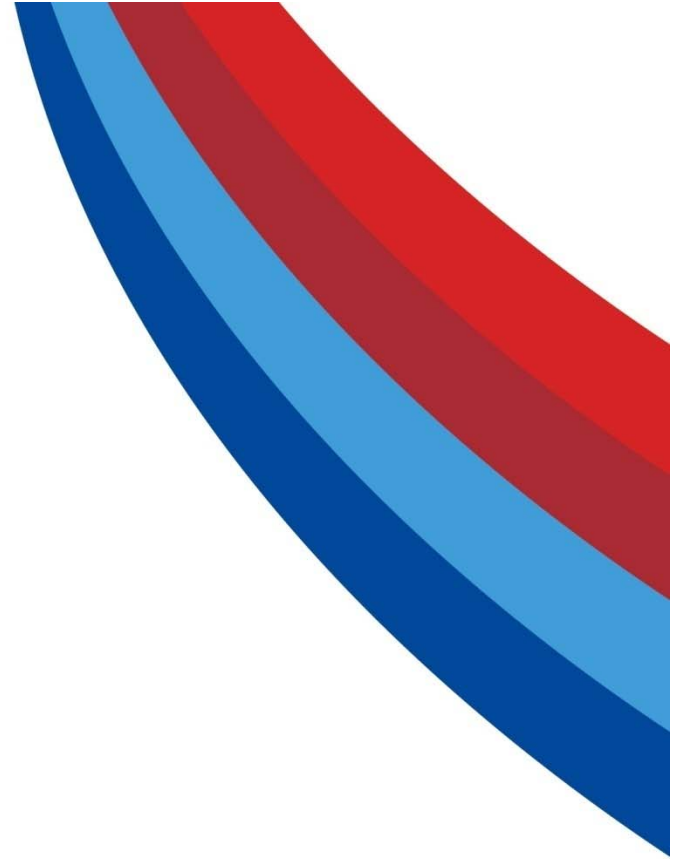

RC Low Pass Filter – Transfer Function ($H(\omega)$)

- Low pass filter passes low frequency signals and attenuates high frequency signals
- Consider an input signal v_{in} . **Output** v_{out} is taken across **capacitor**.
- Transfer function **$H(\omega)$** :
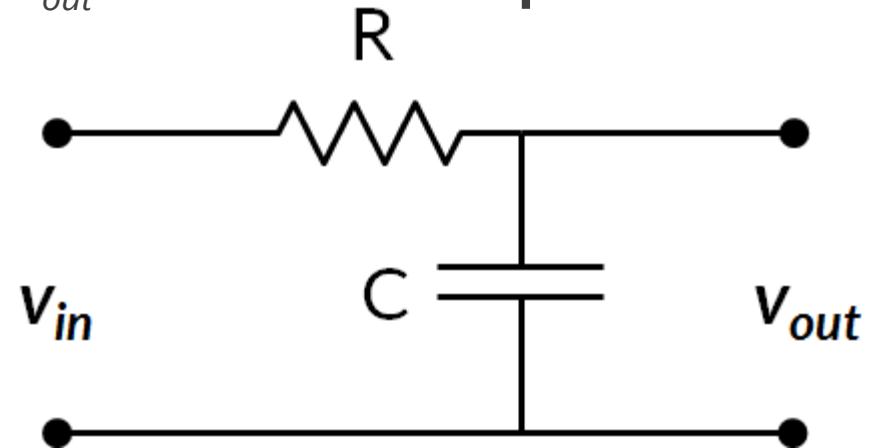
$$H(\omega) = \frac{V_{out}}{V_{in}} = \frac{V_C}{V_R + V_C}$$



$$H(\omega) = \frac{V_C}{V_R + V_C} = \frac{\frac{1}{j\omega C}}{R + \frac{1}{j\omega C}} = \frac{1}{1 + j\omega RC}$$



RC Low Pass Filter – Transfer Function ($H(\omega)$)

➤ Transfer function $\mathbf{H(\omega)}$:

$$H(\omega) = \frac{V_C}{V_R + V_C} = \frac{\frac{1}{j\omega C}}{R + \frac{1}{j\omega C}} = \frac{1}{1 + j\omega RC}$$

$$H(\omega) = \frac{1}{1 + j\omega RC}$$

$$|H(\omega)| = \frac{1}{\sqrt{1 + (\omega RC)^2}}$$

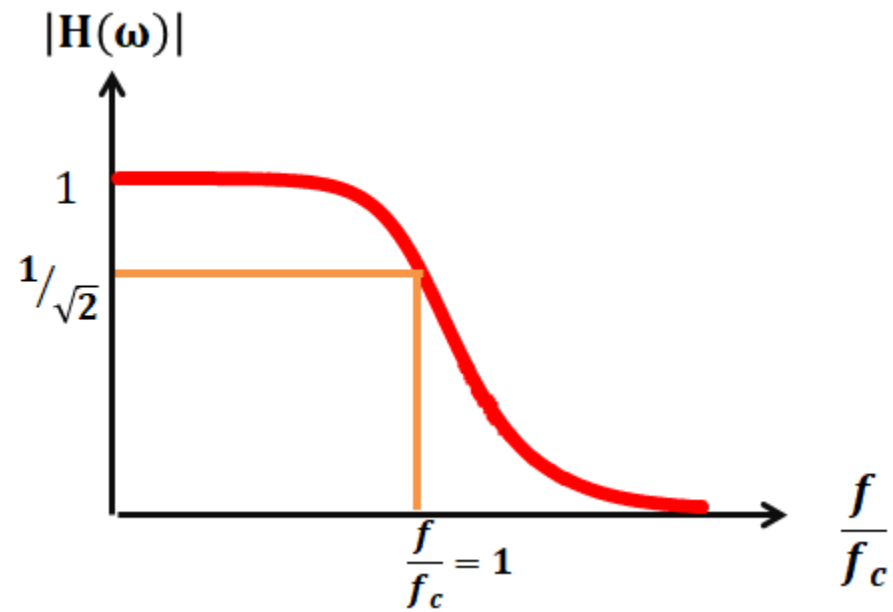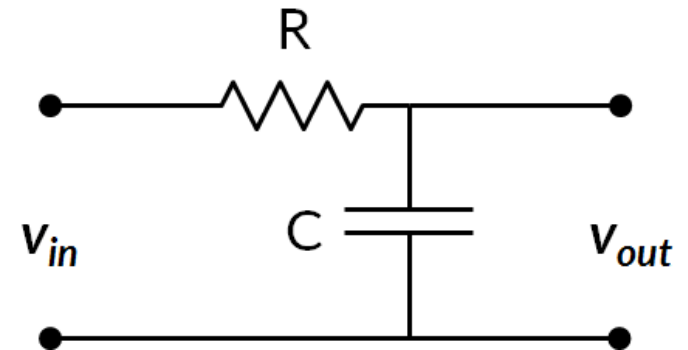

RC Low Pass Filter – Cut-off Frequency (f_c)

- Cut-off Frequency (f_c) or 3-dB frequency is the frequency at which transfer function is $1/2$.

$$|H(\omega)| = \frac{1}{\sqrt{1 + (\omega RC)^2}} = \frac{1}{\sqrt{2}} \Rightarrow \omega_c = \frac{1}{RC}$$

$$f_c = \frac{1}{2\pi RC}$$

$$|H(\omega)| = \frac{1}{\sqrt{1 + \left(\frac{\omega}{\omega_c}\right)^2}} = \frac{1}{\sqrt{1 + \left(\frac{f}{f_c}\right)^2}}$$

- For example, if $R = 160 \, \Omega$, $C = 1 \, \mu\text{F}$, then cut-off frequency (f_c) of a low pass filter is 1 kHz.

RC Low Pass Filter – Phase Angle (ϕ)


➤ Rewriting the Transfer function,

$$H(\omega) = \frac{1}{1 + j\omega RC} = \frac{1 - j\omega RC}{1 + (\omega RC)^2} = |H(\omega)| \angle \phi$$

➤ Phase angle (ϕ)


$$\phi = \tan^{-1} \left(\frac{-\omega RC}{1} \right) = -\tan^{-1}(\omega RC)$$
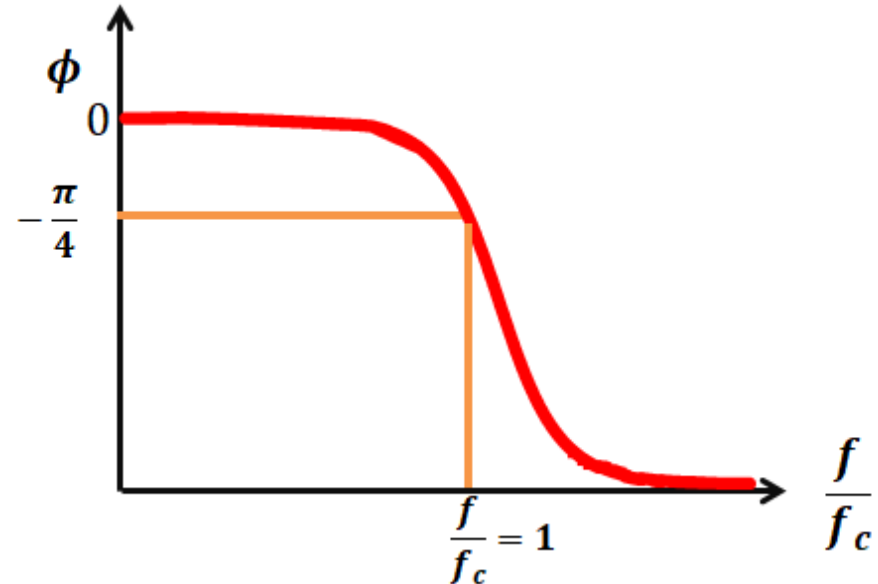
$$\phi = -\tan^{-1} \left(\frac{\omega}{\omega_c} \right) = -\tan^{-1} \left(\frac{f}{f_c} \right)$$



RC Filters

RC High Pass Filter

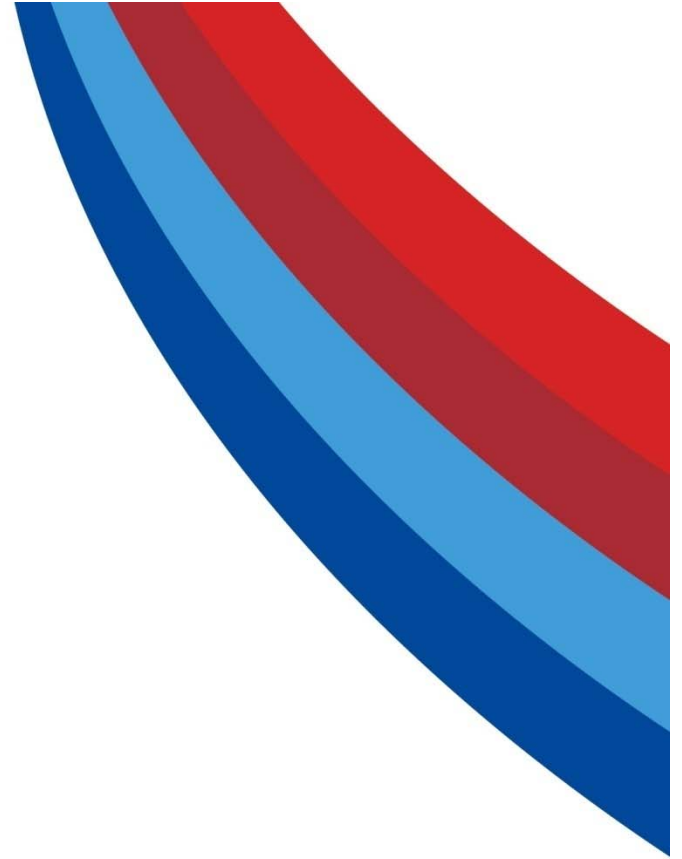


RC High Pass Filter – Transfer Function ($H(\omega)$)

- High pass filter passes high frequency signals and attenuates low frequency signals
- Consider an input signal v_{in} . **Output** v_{out} is taken across **resistor**.
- Transfer function $H(\omega)$:

$$H(\omega) = \frac{V_{out}}{V_{in}} = \frac{V_R}{V_R + V_C}$$

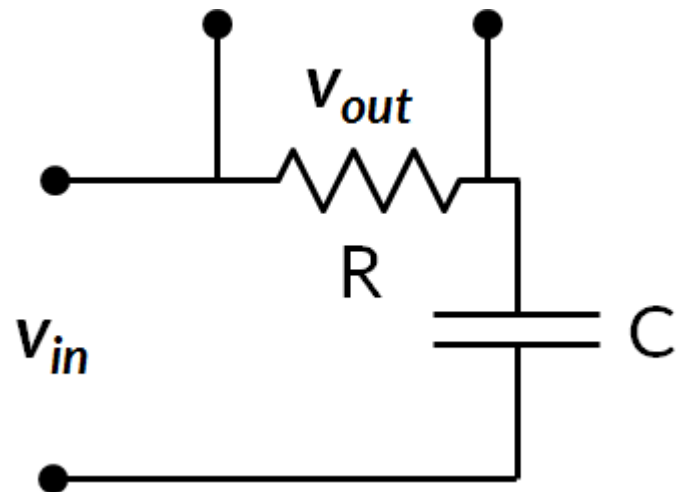
$$H(\omega) = \frac{V_R}{V_R + V_C} = \frac{R}{R + \frac{1}{j\omega C}} = \frac{j\omega RC}{1 + j\omega RC}$$




RC High Pass Filter - Transfer Function ($H(\omega)$)

➤ Transfer function $\mathbf{H}(\omega)$:
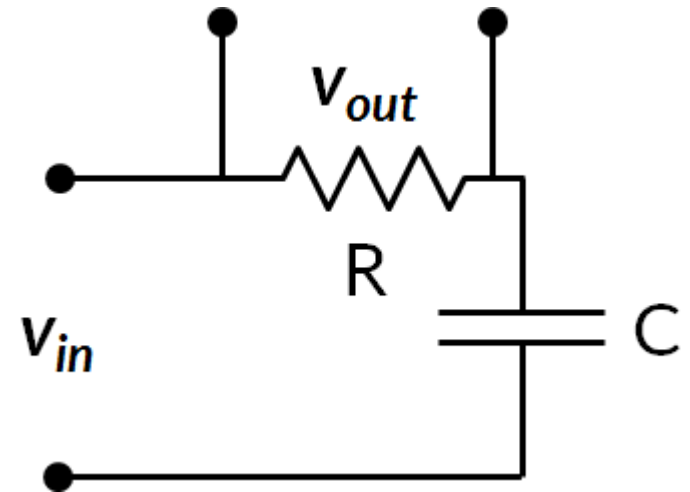
$$H(\omega) = \frac{V_R}{V_R + V_C} = \frac{R}{R + \frac{1}{j\omega C}} = \frac{j\omega RC}{1 + j\omega RC}$$



$$|H(\omega)| = \frac{\omega RC}{\sqrt{1 + (\omega RC)^2}}$$

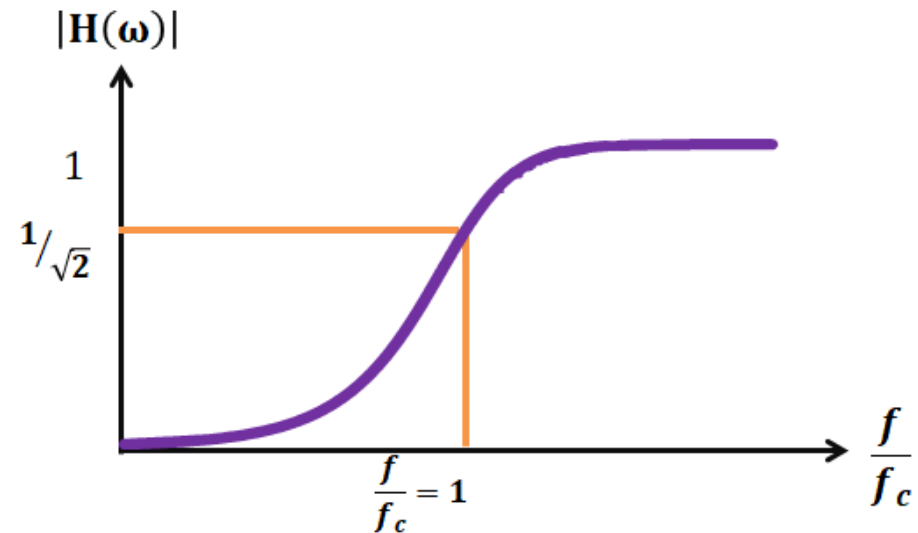

RC High Pass Filter – Cut-off Frequency (f_c)

- Cut-off Frequency (f_c) or 3-dB frequency is the frequency at which transfer function is $1/\sqrt{2}$.

$$|H(\omega)| = \frac{\omega RC}{\sqrt{1 + (\omega RC)^2}} = \frac{1}{\sqrt{2}} \Rightarrow \omega_c = \frac{1}{RC}$$

$$f_c = \frac{1}{2\pi RC}$$

$$|H(\omega)| = \frac{1}{\sqrt{1 + \left(\frac{\omega_c}{\omega}\right)^2}} = \frac{1}{\sqrt{1 + \left(\frac{f_c}{f}\right)^2}}$$

- For example, if $R = 160 \, \Omega$, $C = 1 \, \mu\text{F}$, then cut-off frequency (f_c) of a high-pass filter is 1 kHz.

RC High Pass Filter – Phase Angle (ϕ)


➤ Re-writing transfer function

$$H(\omega) = \frac{j\omega RC}{1 + j\omega RC} \frac{1 - j\omega RC}{1 - j\omega RC} = \frac{(\omega RC)^2 + j\omega RC}{1 + (\omega RC)^2} = |H(\omega)| \angle \phi$$

➤ Phase angle (ϕ)


$$\begin{aligned}\phi &= \tan^{-1} \left(\frac{\omega RC}{(\omega RC)^2} \right) = \tan^{-1} \left(\frac{1}{\omega RC} \right) \\ &= \tan^{-1} \left(\frac{\omega_c}{\omega} \right) = \tan^{-1} \left(\frac{f_c}{f} \right)\end{aligned}$$
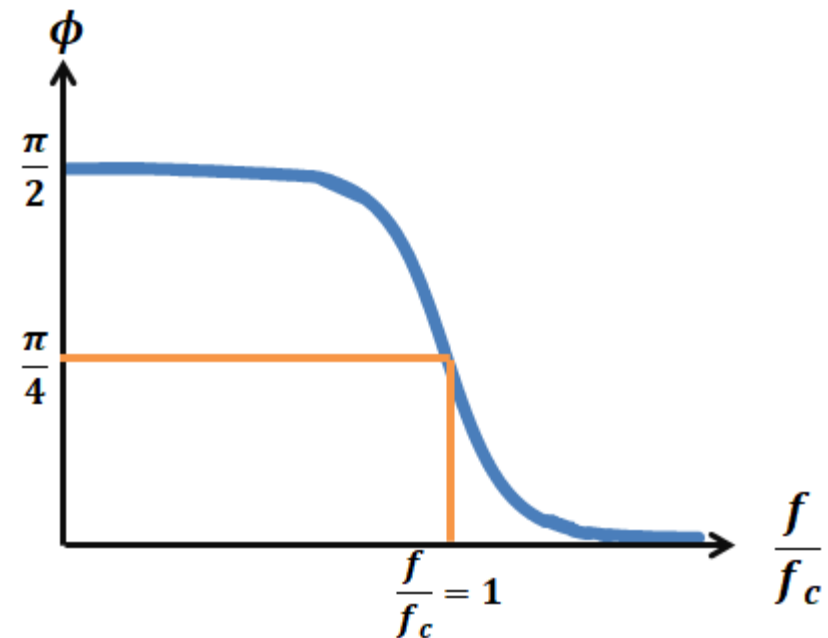
$$\phi = \tan^{-1} \left(\frac{f_c}{f} \right) = \frac{\pi}{2} - \tan^{-1} \left(\frac{f}{f_c} \right)$$



RL Filters


RL Low Pass Filter

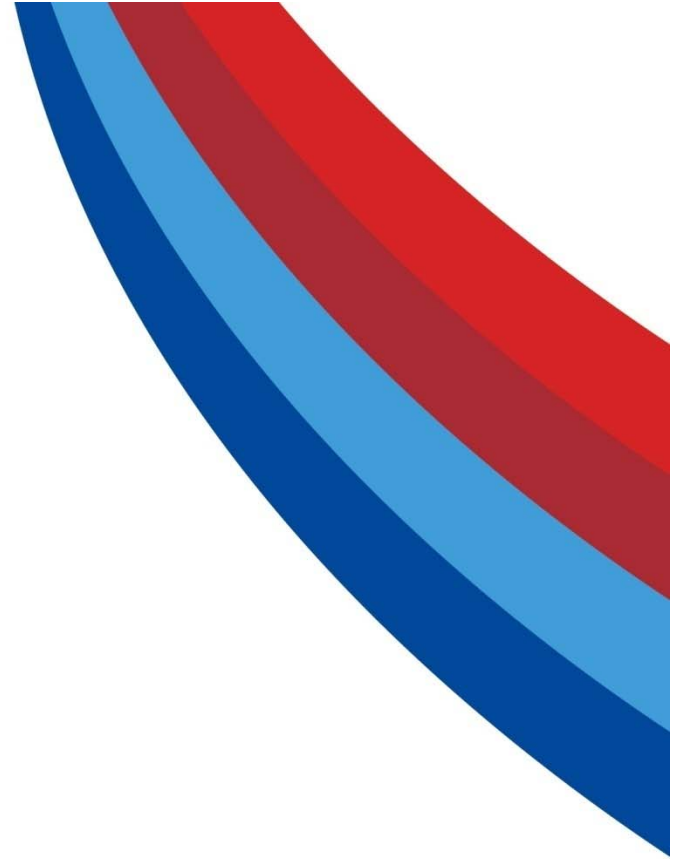

RL Low Pass Filter – Transfer Function ($H(\omega)$)


➤ Transfer function
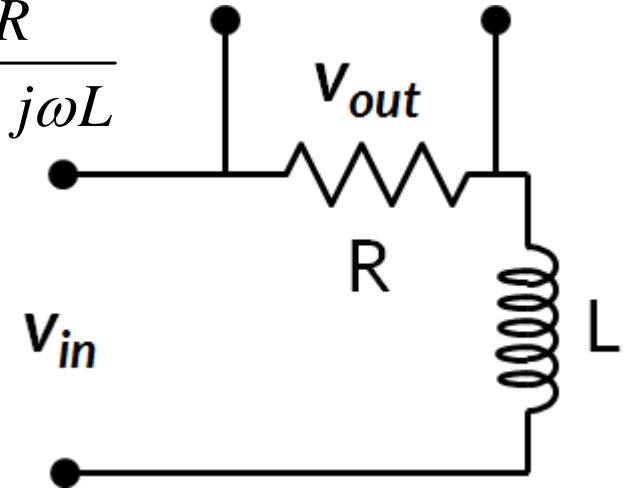
$$H(\omega) = \frac{V_{out}}{V_{in}} = \frac{V_R}{V_R + V_L} = \frac{R}{R + j\omega L}$$



$$|H(\omega)| = \frac{1}{\sqrt{1 + \left(\frac{\omega L}{R}\right)^2}}$$
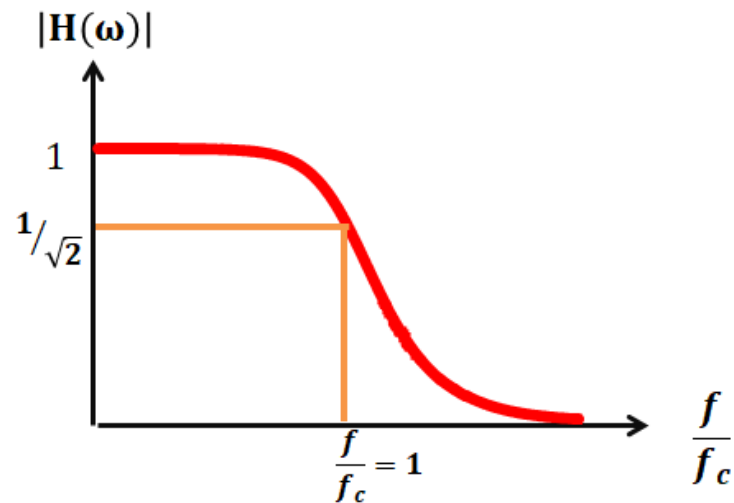
$$H(\omega) = \frac{1}{1 + \frac{j\omega L}{R}}$$



RL Low Pass Filter – Cut-off Frequency (f_c)

- Cut-off frequency (f_c)


$$|H(\omega)| = \frac{1}{\sqrt{1 + \left(\frac{\omega L}{R}\right)^2}} = \frac{1}{\sqrt{2}} \Rightarrow \omega_c = \frac{R}{L}$$

$$f_c = \frac{R}{2\pi L}$$

RL Low Pass Filter – Phase Angle (ϕ)


➤ Transfer function is

$$H(\omega) = \frac{1}{1 + \frac{j\omega L}{R}} = \frac{1 - \frac{j\omega L}{R}}{1 + \left(\frac{\omega L}{R}\right)^2} = |H(\omega)| \angle \phi$$

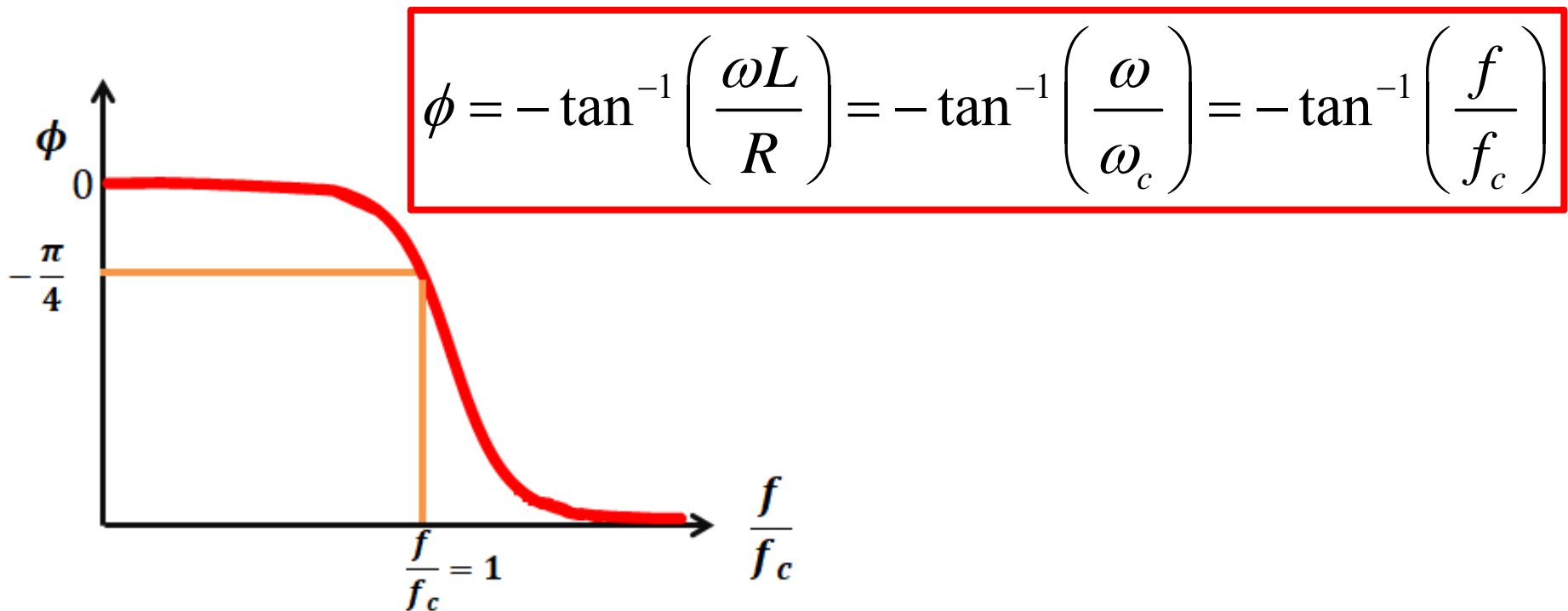

RL Filters

RL High Pass Filter

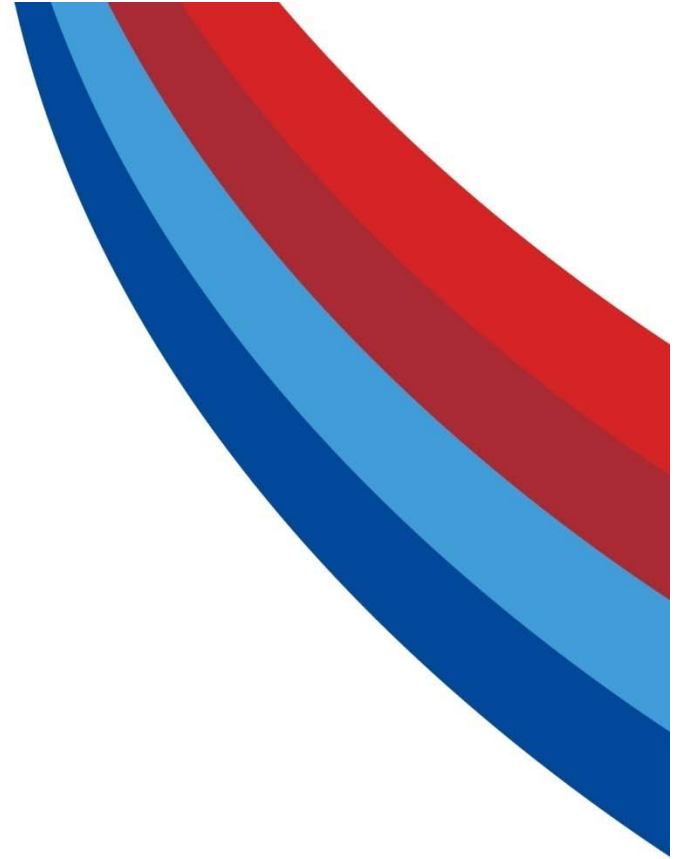



RL High Pass Filter – Transfer Function ($H(\omega)$)

➤ Transfer function

$$H(\omega) = \frac{V_{out}}{V_{in}} = \frac{V_L}{V_R + V_L} = \frac{j\omega L}{R + j\omega L}$$

$$H(\omega) = \frac{1}{1 + \frac{R}{j\omega L}}$$

$$|H(\omega)| = \frac{1}{\sqrt{1 + \left(\frac{R}{\omega L}\right)^2}}$$

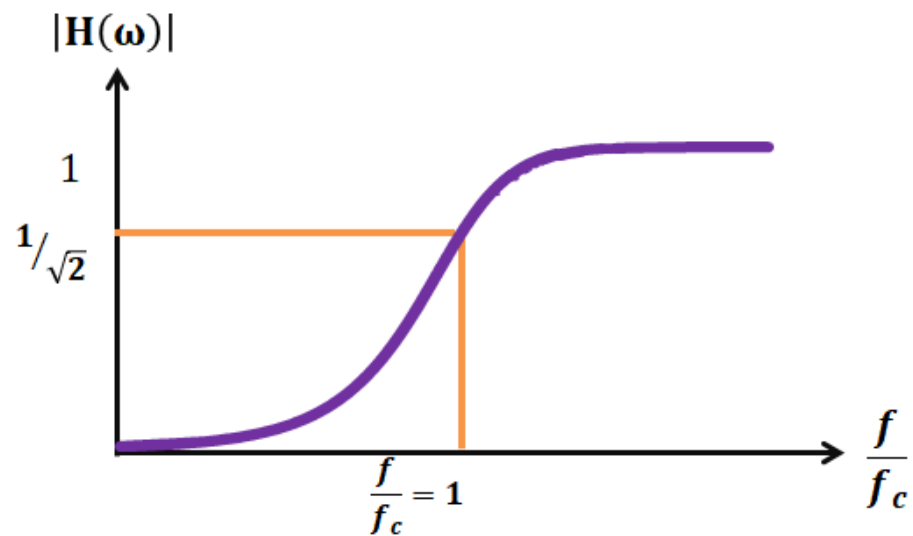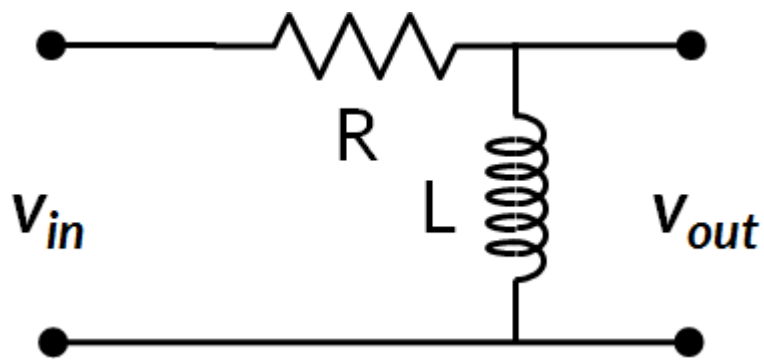

RL High Pass Filter – Cut-off Frequency (f_c)

- Cut-off frequency (f_c)

$$|H(\omega)| = \frac{1}{\sqrt{1 + \left(\frac{R}{\omega L}\right)^2}} = \frac{1}{\sqrt{2}} \Rightarrow \omega_c = \frac{R}{L}$$

$$f_c = \frac{R}{2\pi L}$$

RL High Pass Filter – Phase Angle (ϕ)

➤ Transfer function is

$$H(\omega) = \frac{1}{1 + \frac{R}{j\omega L}} = \frac{1 - \frac{R}{j\omega L}}{1 + \left(\frac{R}{\omega L}\right)^2} = |H(\omega)| \angle \phi$$

$$\phi = \tan^{-1}\left(\frac{R}{\omega L}\right) = \tan^{-1}\left(\frac{\omega_c}{\omega}\right) = \tan^{-1}\left(\frac{f_c}{f}\right) = \frac{\pi}{2} - \tan^{-1}\left(\frac{f}{f_c}\right)$$

