
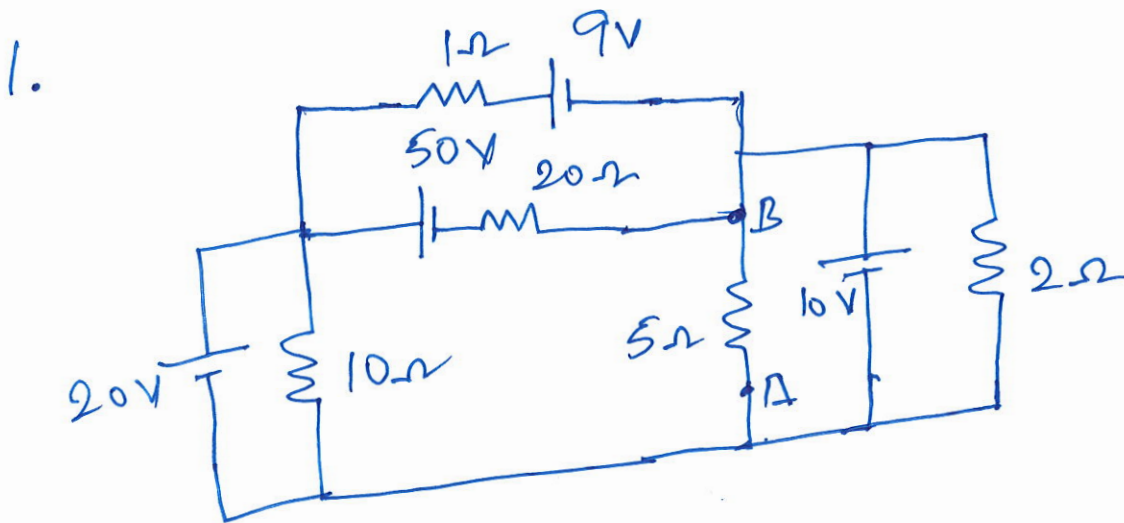


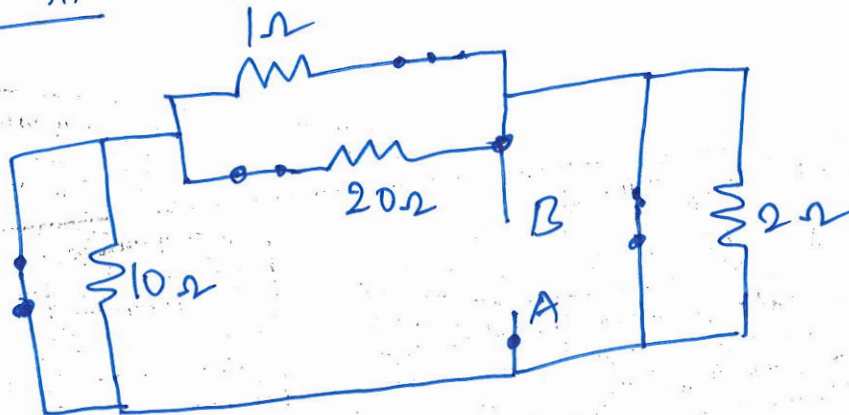
EEEL105L SOLUTIONS TO MIDTERM EXAMINATION ①



To find R_{TH} :




\Rightarrow

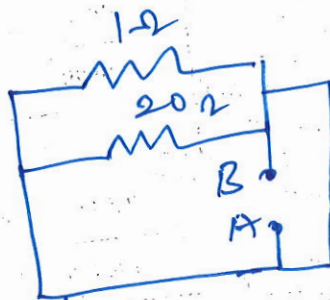


$\Rightarrow R_{AB} = 0 = \underline{\underline{R_{TH}}}$

V_{TH}

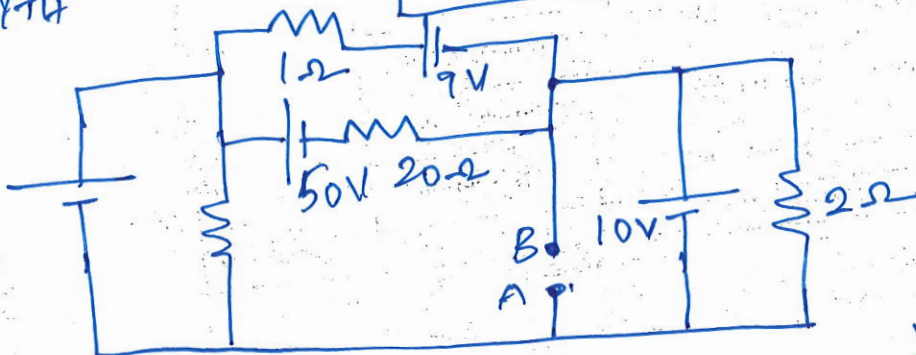

As 10V supply is in parallel, $V_{AB} = 10V$
 So $V_{TH} = \underline{10V}$


②

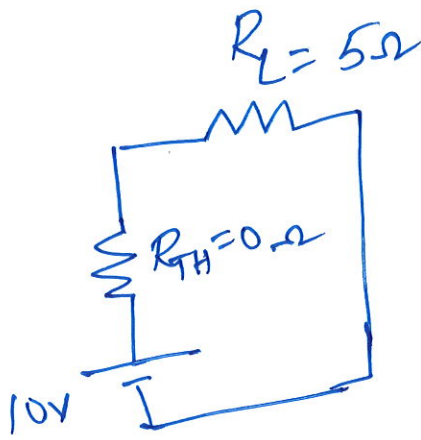


$$I_L = \frac{V_L}{R_L} = \frac{10}{5} = 2A$$

$$P_L = V_L \cdot I_L = 10 \cdot 2 = \underline{\underline{20W}}$$


2.

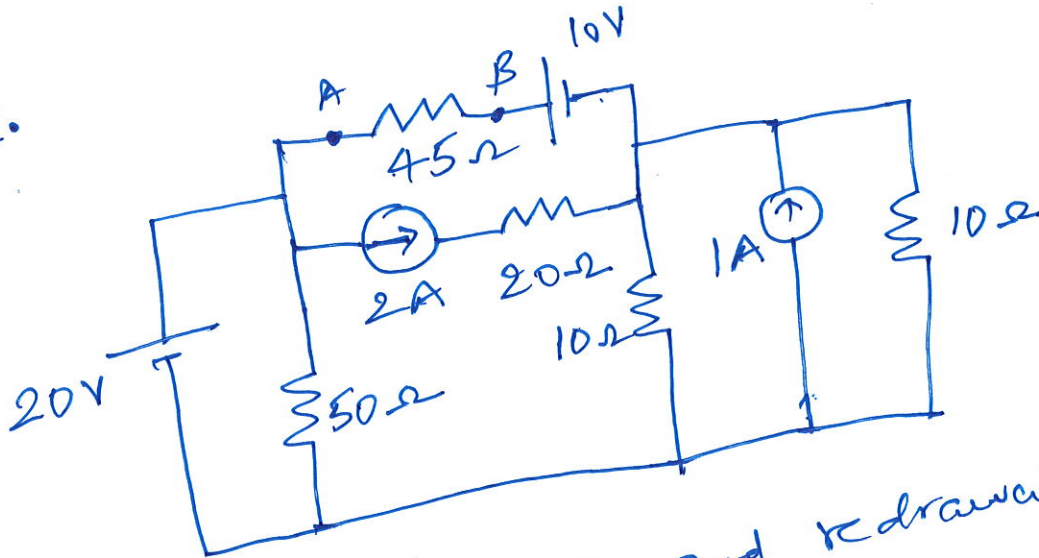

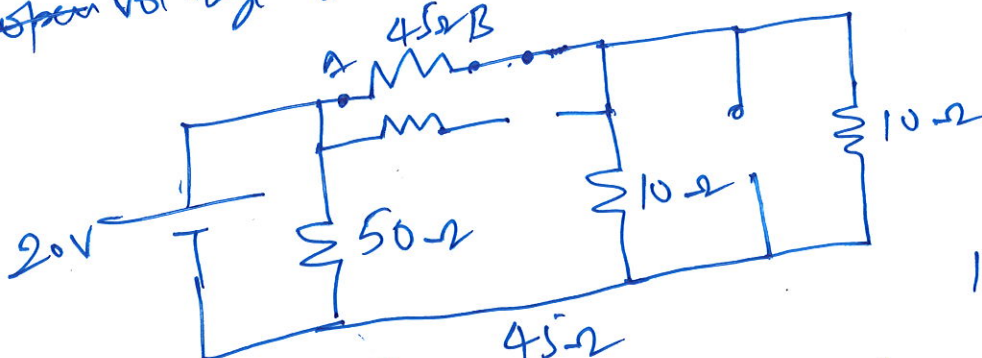Consider 20V source and redraw the circuit by open circuiting current sources and short circuiting voltage sources.




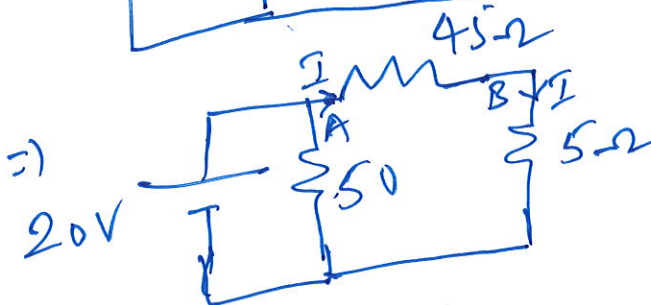
$$10 \Omega \parallel 10 \Omega = 5 \Omega$$



Voltage across (45 Ω + 5 Ω) is 20V.

$$\therefore I = \frac{20}{45+5} = \frac{20}{50} = 0.4 \text{ A (from A to B)} \quad (3)$$

Considering 2A source

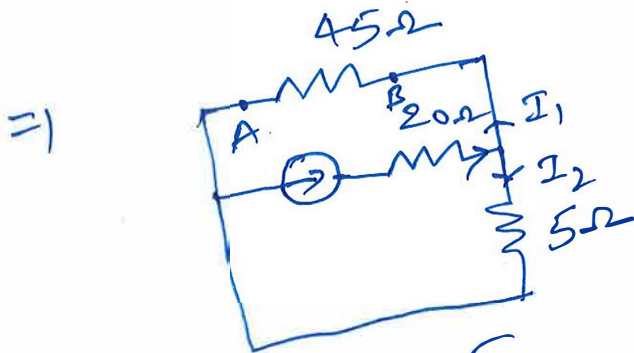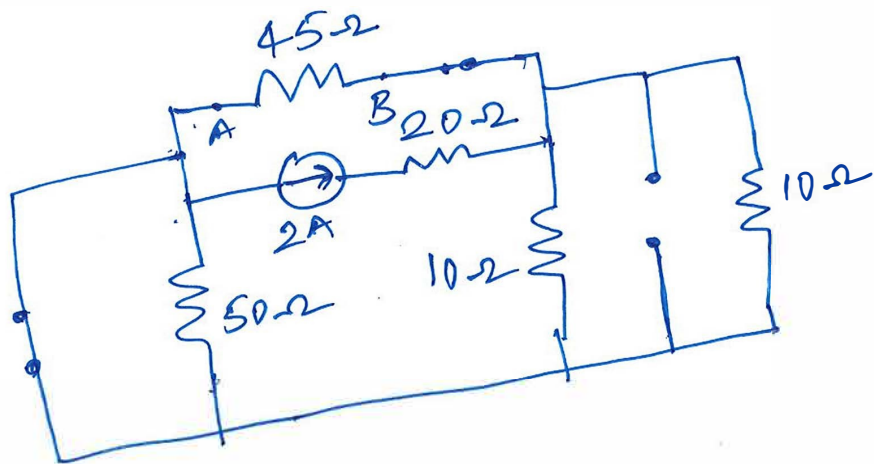

$$I_1 + I_2 = 2 \text{ A}$$

$$I_1 = \frac{2 \times 5}{45+5} =$$

$$2 \times 0.1 = 0.2 \text{ A (B to A)}$$

$$I_{\text{net}} = 0.4 - 0.2 = 0.2 \text{ A (A to B)}$$

$$P = I^2 R = (0.2)^2 \times 45 = \underline{1.8 \text{ W}}$$

3.

$$f(t) = 10 \sin(\omega t + 20^\circ)$$

$$g(t) = 10 \cos(\omega t - 80^\circ) = 10 \sin(\omega t + 90^\circ - 80^\circ)$$


$$= 10 \sin(\omega t + 10^\circ)$$

$$(\omega t + 20^\circ) - (\omega t + 10^\circ) = 10^\circ$$

$f(t)$ leads $g(t)$ by 10° (or)

$g(t)$ lags $f(t)$ by 10°

(4)

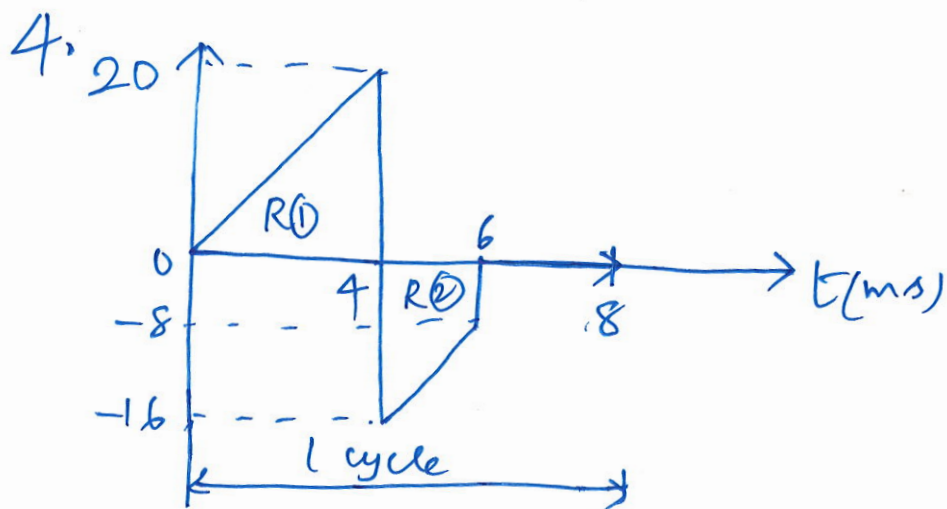

In region-I $f_1(t) = mt + c$

at $t=0$ $f_1(t)=0 \Rightarrow C=0$

at $t=4$ $f_1(t)=20 \Rightarrow 20 = m \cdot 4 \Rightarrow m = 5 \text{ V/ms}$

$$f_1(t) = 5t \quad \text{--- (A)}$$

In region-II $f_2(t) = mt + c$

at $t=4$, $f_2(t) = -16 \Rightarrow -16 = 4m + c$ --- (1)

at $t=6$ $f_2(t) = -8 \Rightarrow -8 = 6m + c$ --- (2)

from (1) & (2) $m = 4 \text{ V/ms}$, $C = -32 \text{ V}$

$$f_2(t) = 4t - 32$$


$$V_{\text{RMS}} = \sqrt{\frac{\int_0^4 (5t)^2 dt + \int_4^6 (4t - 32)^2 dt + \int_6^8 0^2 dt}{8-0}}$$

$$= \sqrt{\frac{\left. \frac{25t^3}{3} \right|_0^4 + \left. \frac{16t^3}{3} - \frac{256t^2}{2} + 1024t \right|_4^6}{8}}$$


$$= \sqrt{\frac{\frac{25(4)^3}{3} + \frac{16(6^3 - 4^3)}{3} - \frac{256(6^2 - 4^2)}{2} + 1024(6 - 4)}{8}}$$

$$= \left(\frac{1600}{3} + \frac{2432}{3} - 2560 + 2048 \right)^{1/2} = 2\sqrt{26} \text{ V}$$


5

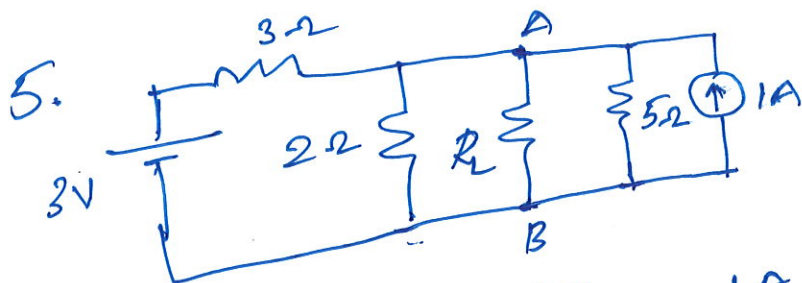
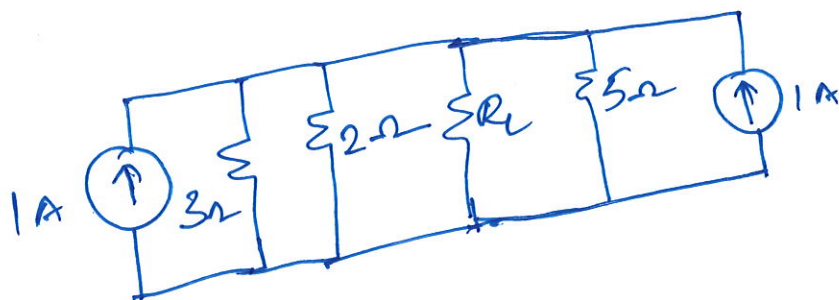
$$I_s = \frac{V_s}{R_s} = \frac{3V}{3\Omega} = 1A$$


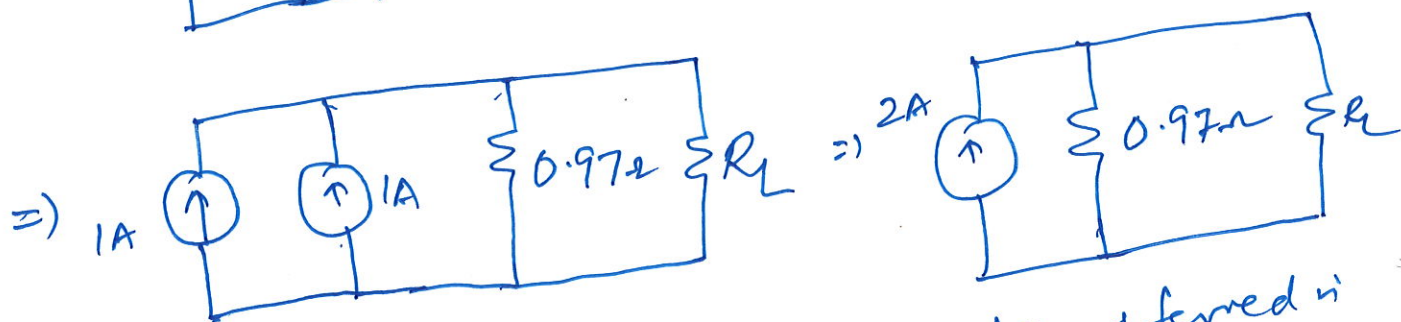
$$3 \parallel 2 \parallel 5 = 0.97\Omega$$



R_L for which maximum power is transferred is

0.97Ω