

Department of ECE, Bennett University

EECE105L: Fundamentals of Electrical and Electronics Engineering

Tutorial Sheet-4

**Topics Covered:** Source Transformation/Source conversion

1. For the circuit shown in Fig. 1, by converting the current source into voltage source, find the current through  $91\ \Omega$  resistor.

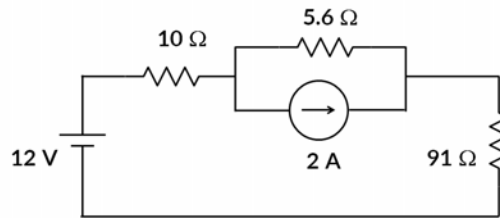


Fig. 1

2. For the network shown in fig. 2, by replacing all the current sources with a single current source, find the source voltage  $V_s$ .

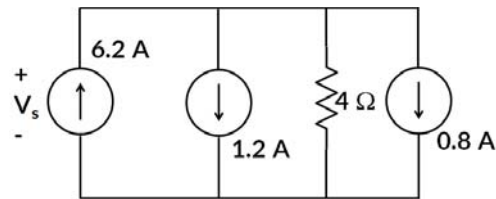


Fig. 2

3. For the network shown in fig. 3, find the voltage  $V_s$  and current through  $4\ \Omega$  resistor.

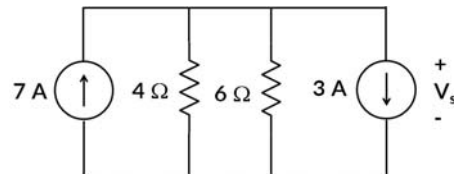


Fig. 3

4. For the circuit shown in fig. 4, determine the current through  $12\ \Omega$  resistor by changing the voltage sources into current sources.

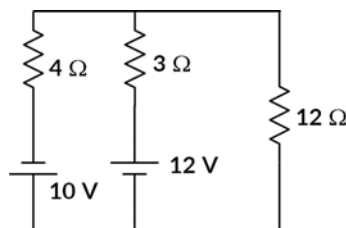


Fig. 4

5. In the circuit shown in fig. 5, find the voltage  $V_{ab}$  and current through  $6\ \Omega$  resistance.

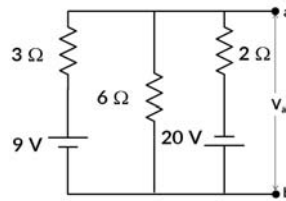


Fig. 5

6. For the circuit shown in fig. 6, find the voltage  $V_s$  and current through  $12\text{ V}$  source.

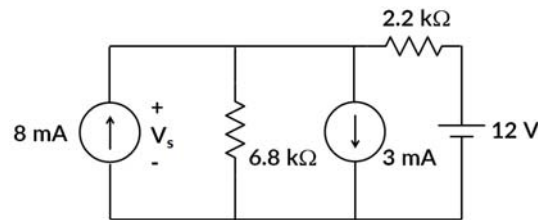


Fig. 6

#### Source Transformation/ Source Conversion

- 1) 218 mA
- 2) 16.8 V
- 3) 9.6 V, 2.4 A
- 4) 0.19 A
- 5) -7 V, -1.17 A
- 6) 17.35 V, 2.43 A