

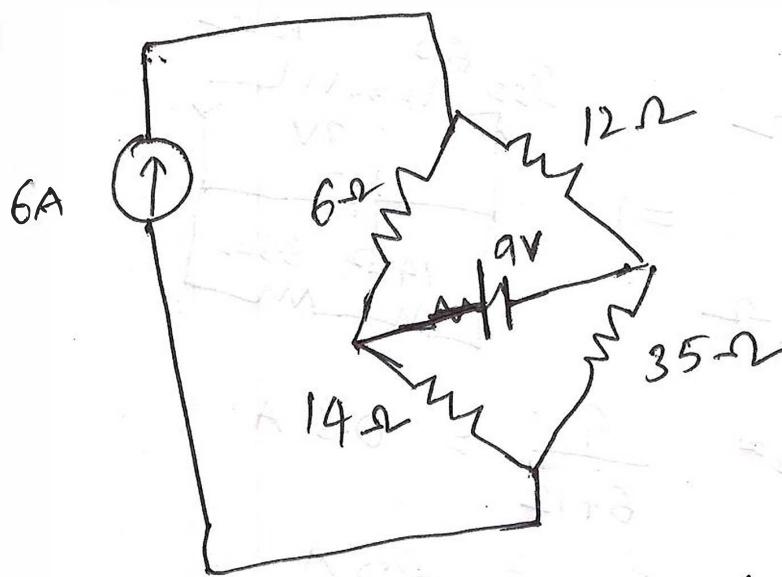


1)

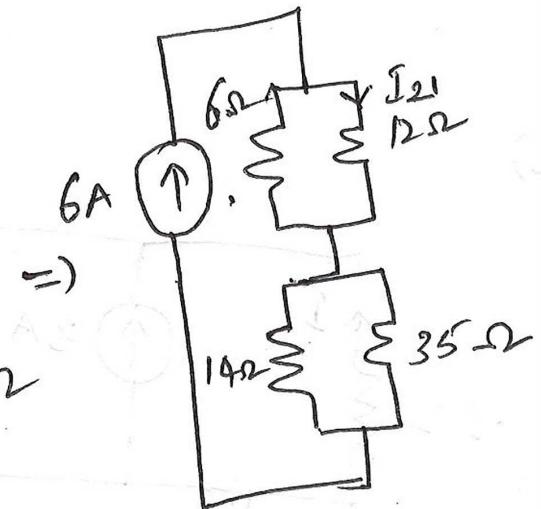

1st Consider the effect of 6A source.


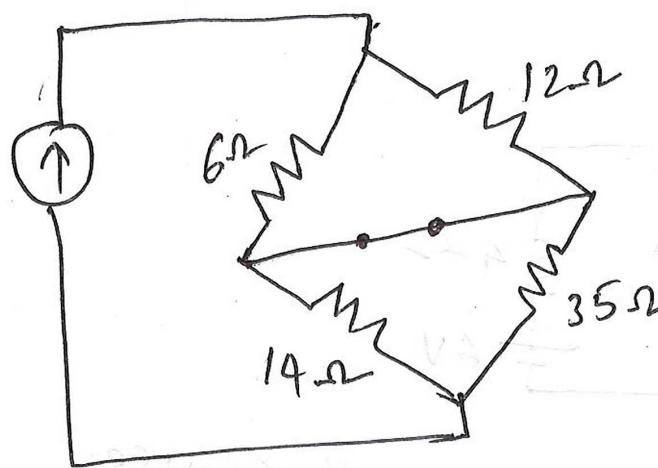


$$I_{21} = \frac{6A \times 6\Omega}{(6\Omega + 12\Omega)} = 2A$$

Consider the effect of 9V source.
Re-drawing the circuit,

(P.T.O)

(2)

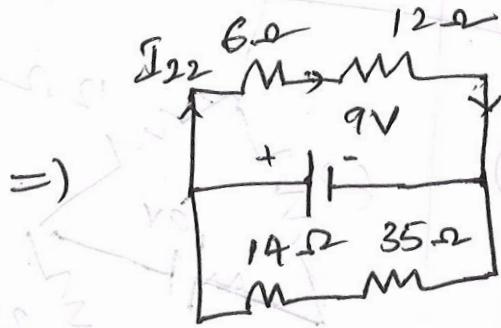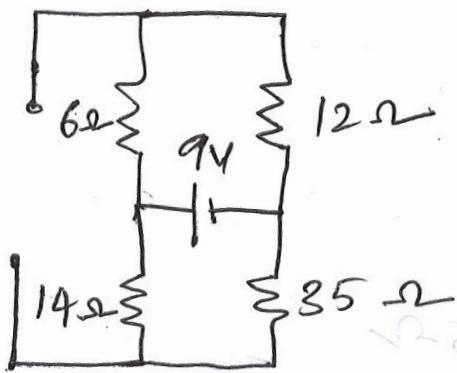


$$I_{22} = \frac{9}{6+12} = 0.5 \text{ A}$$

Thus,


$$I_2 = I_{21} + I_{22} = \underline{\underline{2.5 \text{ A}}}$$

2)

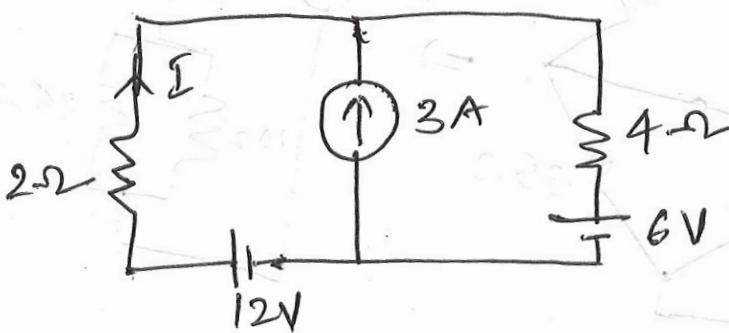


Consider the effect of 12V source.

Re-drawing the circuit,

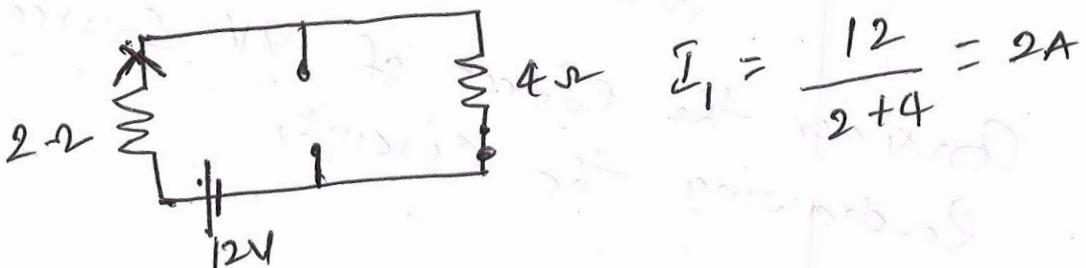


(3)

Consider the effect of 6V source:

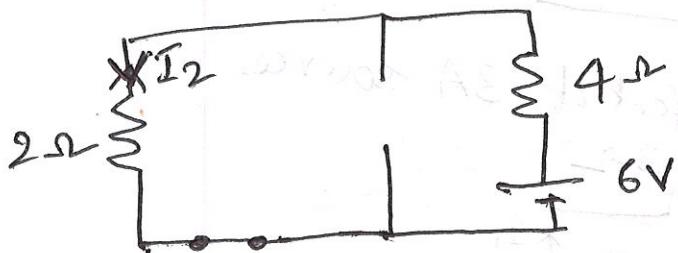

$$I_2 = \frac{6}{2+4} = 1 \text{ A}$$

Consider the effect of 3A source

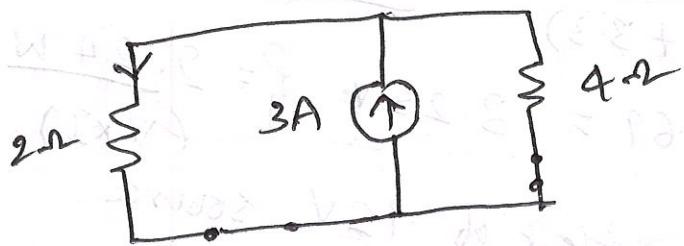

$$I_3 = \frac{3 \times 4}{2+4} = 2 \text{ A}$$


The total current through $2\ \Omega$ resistor

$$I = I_1 + I_2 + I_3 = 2 + 1 + 2 = 5 \text{ A}$$


(. . . I_1 is in opposite direction to I_2 and I_3)

3

4

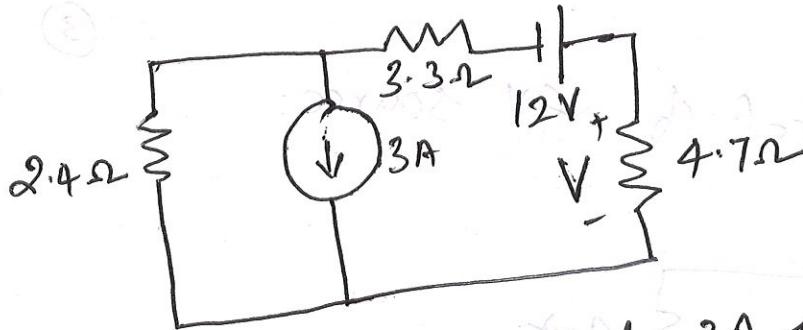


Considering the effect of 3A source,

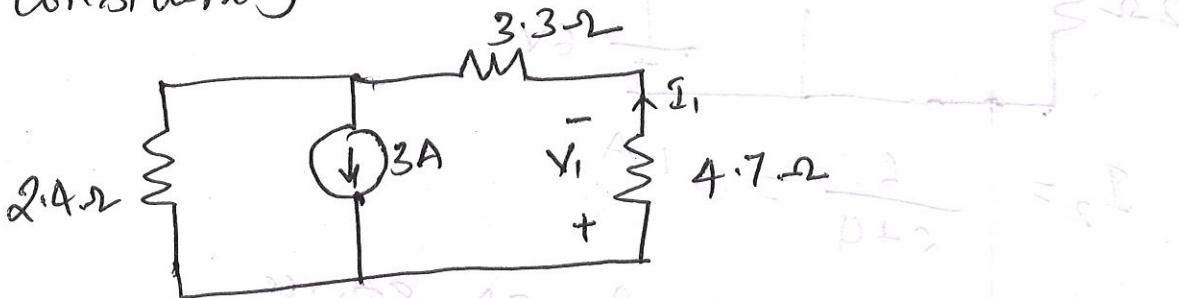

$$I_1 = \frac{2.4 \times 3A}{2.4 + (4.7 + 3.3)} = 0.69 A$$

$$V_1 = 4.7 \times 0.69 = 3.25 V \quad P_1 = 2.24 W \quad (V \times I)$$

considering the effect of 12V source

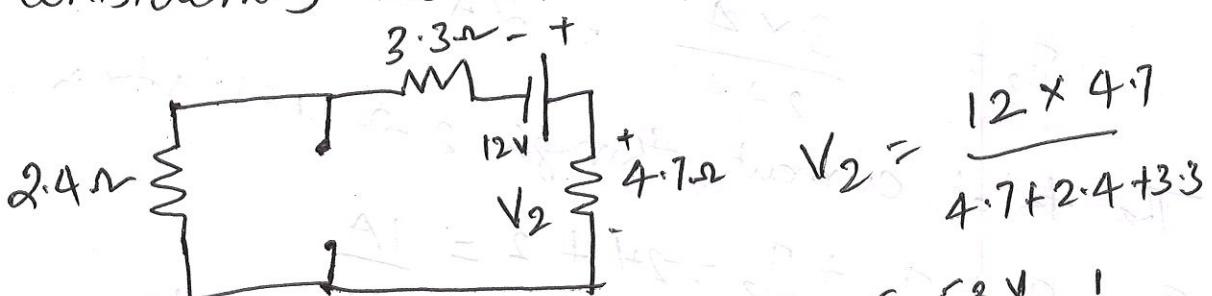


$$V_2 = \frac{12 \times 4.7}{4.7 + 2.4 + 3.3} = 5.53 V$$


$$V = 5.53 - 3.25 = \frac{2.28 V}{4.7} \quad P_2 = 6.51 W \quad (V^2/R)$$

$$P = \frac{V^2}{R} = \frac{(2.28)^2}{4.7} = 1.106 W$$

$$\underline{P_1 + P_2 \neq P}$$

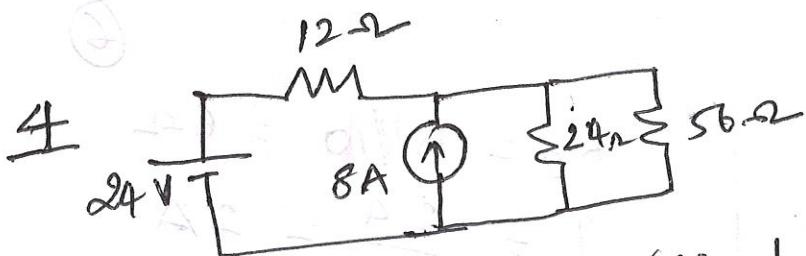

considering 24V source

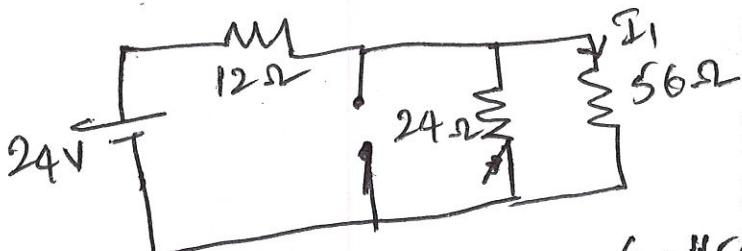

$$I_0 = \frac{24V}{R} \quad R = 12 + (24 \parallel 56) \\ = 28.8 \Omega$$


$$= 0.833 A$$

$$I_1 = \frac{0.833 \times 24}{24 + 56} = 0.25 A$$


$$I = I_1 + I_2 = 0.25 + 1 = 1.25 A$$



considering 42V source

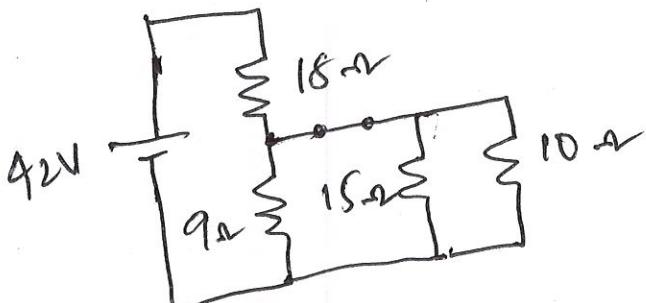

considering 8A source

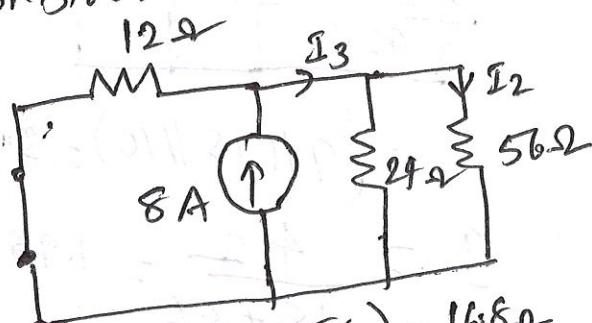


$$R_T = (24 \parallel 56) = 16.8 \Omega$$

$$I_3 = \frac{8 \times 12}{12 + 16.8} = 3.33 A$$

$$I_2 = \frac{3.33 \times 24}{24 + 56} = 1 A$$


considering 24V source

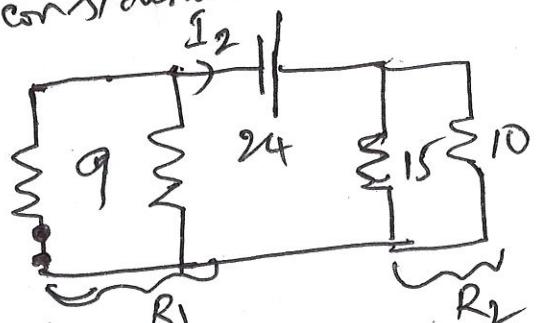

$$I_2 = \frac{24}{R_1 + R_2}$$

$$R_1 = 18 \parallel 9 = 6 \Omega$$

(5)

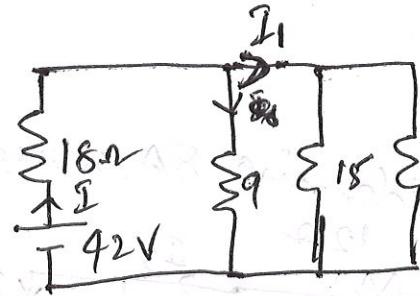

$$R_{\text{eq}} = (9 \parallel 15 \parallel 10) = 3.6 \Omega$$

$$I = \frac{42}{18 + 3.6} = 1.944 \text{ A}$$

$$I_1 = \frac{9 \times 1.944}{9 + (15 \parallel 10)} = 1.17 \text{ A}$$

(Total current flowing through 18Ω resistor gets divided in two parts. One part through 9Ω and other through $24V$ source)

$$I_{\text{eq}} = I_1 + I_2 = 2 + 1.17 = 3.17 \text{ A}$$

Power delivered by the source


$$P = V \cdot I = 24 \times 3.17 = 76.08 \text{ W}$$

(6)

$$R_2 = 15 \parallel 10 = 6 \Omega$$


$$I = \frac{24}{12} = 2 \text{ A}$$

6

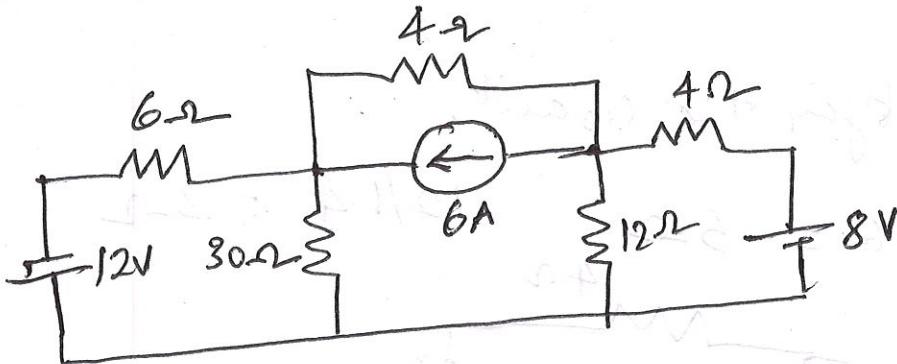

7


Considering the effect of 12V source

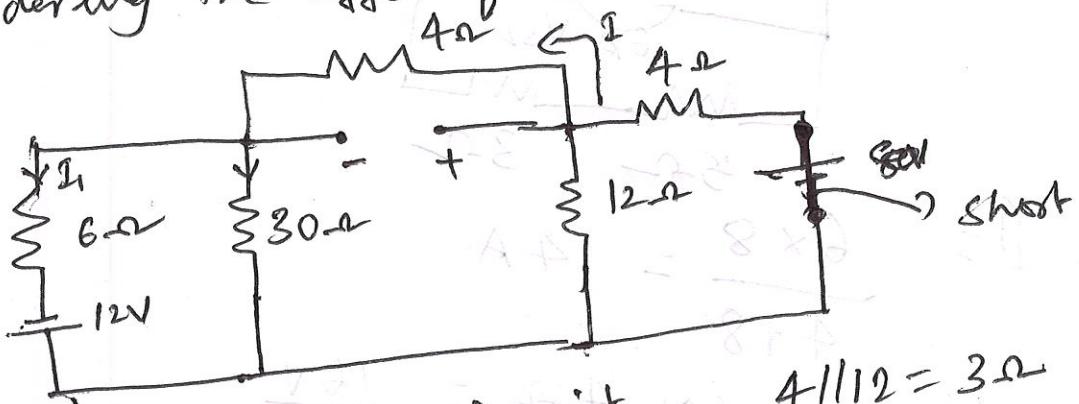

~~Q2 redrawing circuit~~

$$4 \parallel 12 = 3\Omega$$


$$4 + (4 \parallel 12) = 7\Omega$$

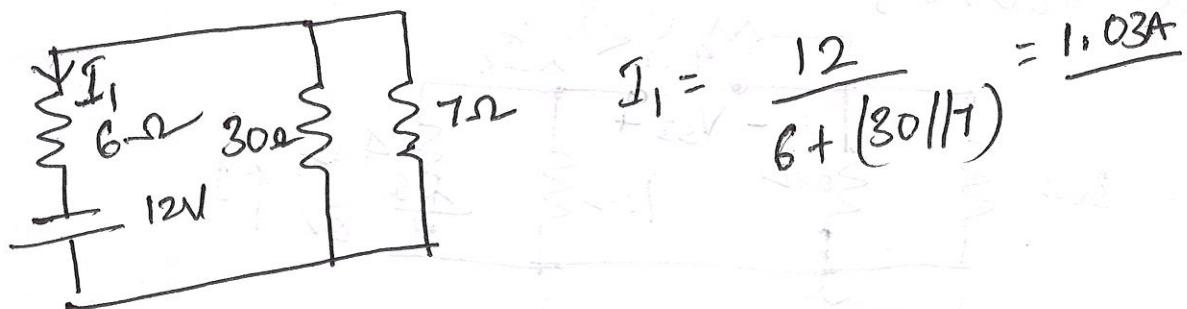

$$I = \frac{1.03 \times 30}{7 + 30} = 835.14 \text{ mA}$$

$$V_{S1} = I \times 4\Omega = 3.34 \text{ V}$$

Considering the effect of 6A Source:

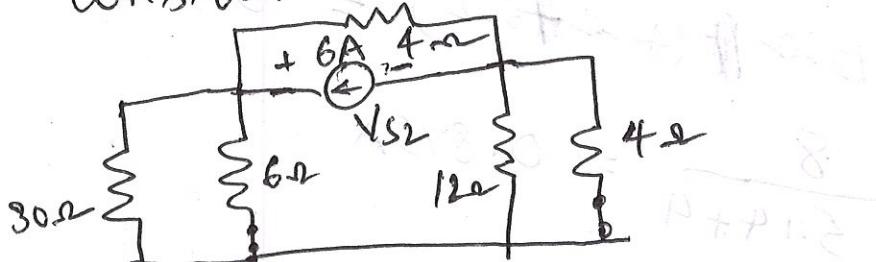


$$R_{eq} = \frac{283.0 \times 12}{283.0 + 12} = 11.2 \Omega$$

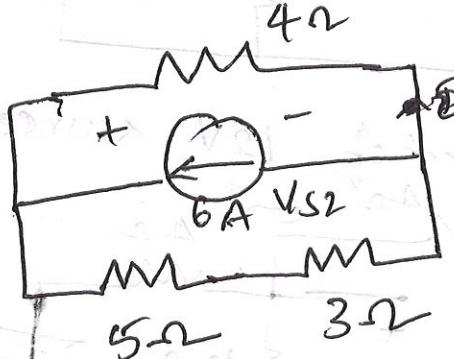(8)

Simplifying the circuit,


$$30/16 = 5\Omega \quad 12/14 = 3\Omega$$



$$I = \frac{6 \times 8}{4 + 8} = 4A$$


$$V_{S2} = 4A \times 4\Omega = 16V$$

Considering the effect of 8V Source:

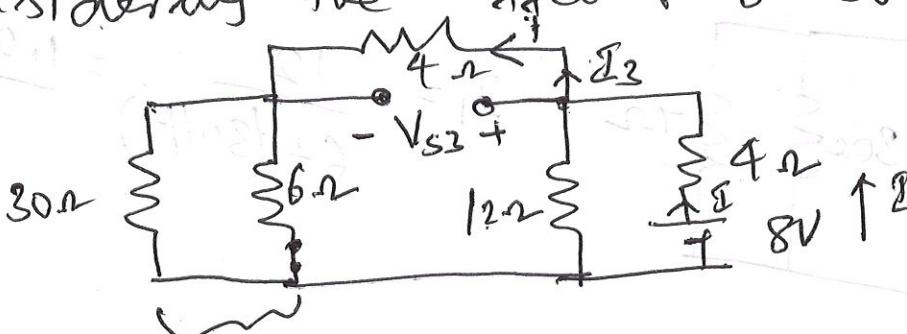

$$R = 30/16\Omega = 5\Omega$$

Simplifying the circuit

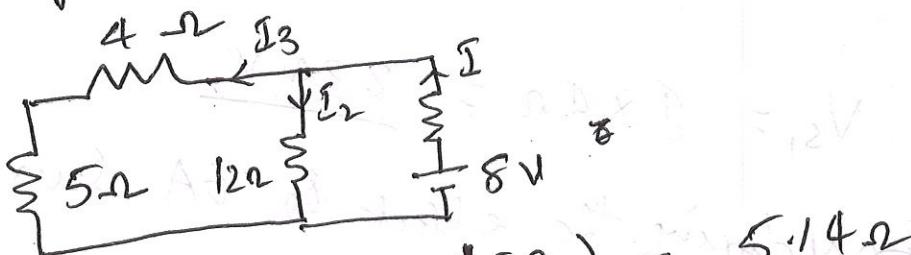

$$R = 12\Omega \parallel (4\Omega + 5\Omega) = 5.14\Omega$$

$$I = \frac{8}{5.14 + 4} = 0.875A$$


$$I_3 = \frac{12 \times 0.875}{12 + 9} = 0.5A$$

$$V_{S3} = 2V$$

$$V_S = -V_{S1} + V_{S2} - V_{S3} = -3.34 + 16 - 2 \\ = \underline{\underline{10.66V}}$$

10

7.


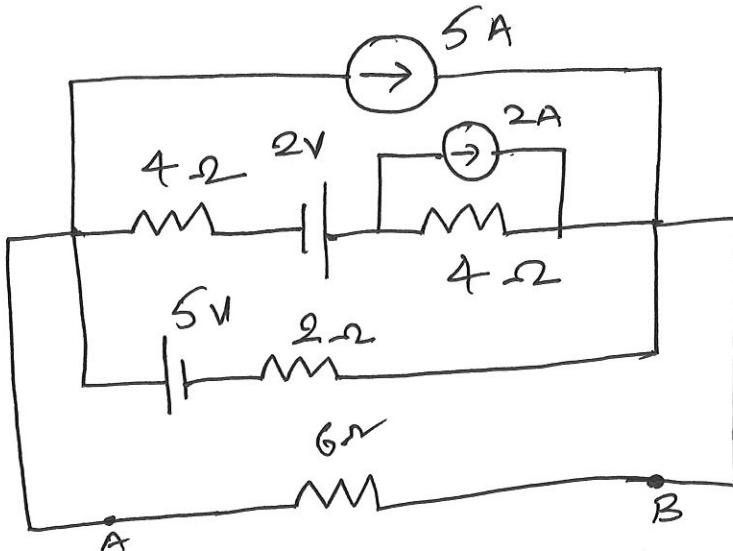


Consider 5A Source.


2A Source is open (current source)

5V Source is short } Voltage Sources.
2V Source is short }


redrawing the Circuit,

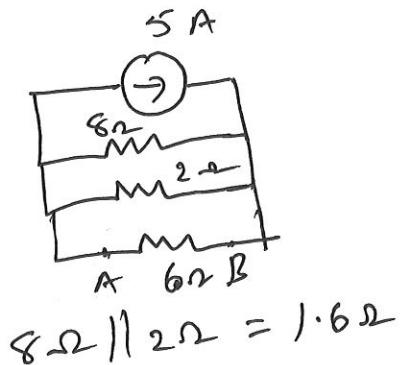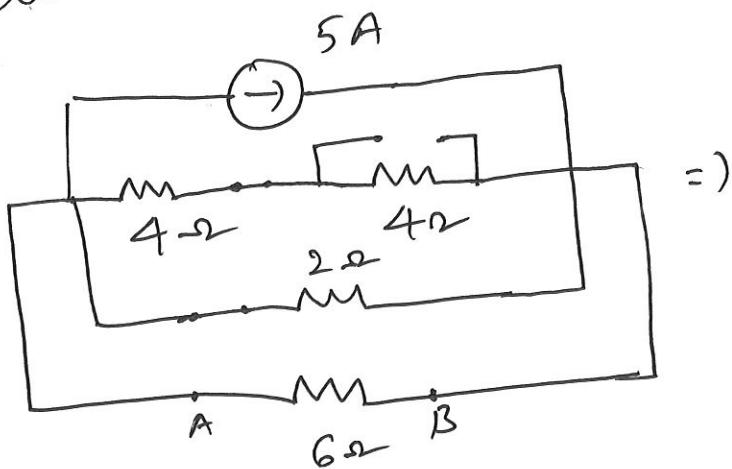

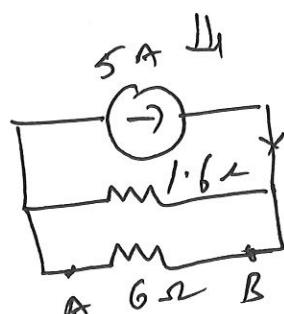
$$I_{6\Omega} (5A) = \frac{5 \times 1.6}{1.6 + 6} = 1.05A \text{ (B to A)}$$



Consider 2A Source

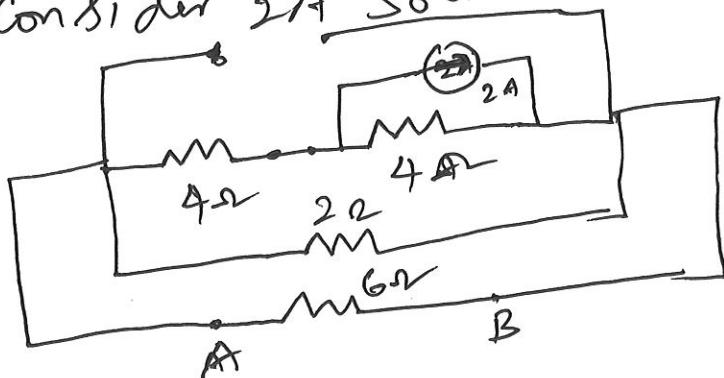


(11)

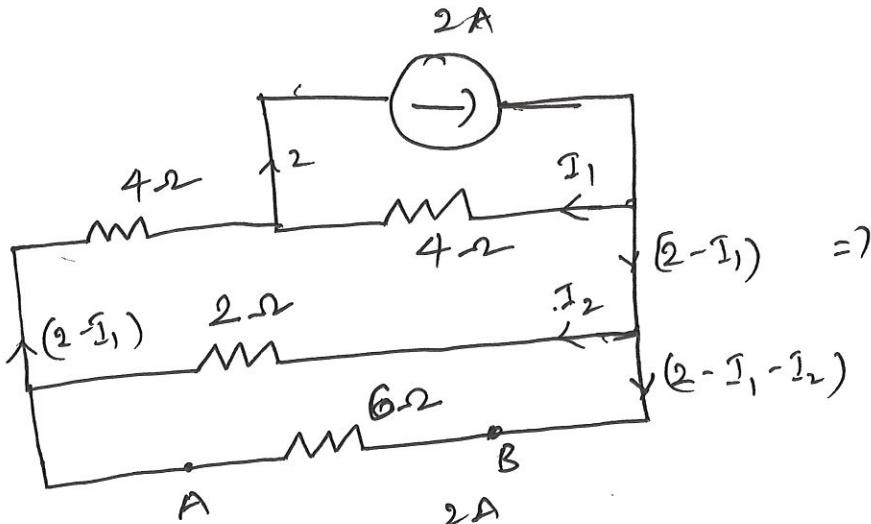

$$(2/16) = \frac{12}{8} = \frac{3}{2}$$

$$= 1.5 \Omega$$

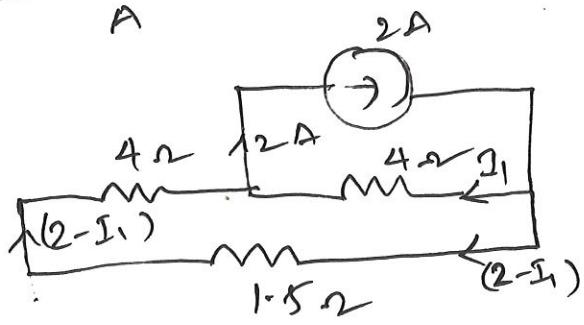

$$I_1 = \frac{2 \times 5.5}{4 + 4 + 1.5}$$

$$I_1 = 1.158 A$$


$$2 - I_1 = 0.842 A$$

$$I_2 = \frac{(2 - I_1) \times 6}{6 + 2} = \frac{0.842 \times 6}{8} = 0.632 A$$


$$2 - I_1 - I_2 = 0.21 A$$

$$I_{6\Omega} (2A) = 0.21 A \text{ (B to A)}$$

Consider 2V Source

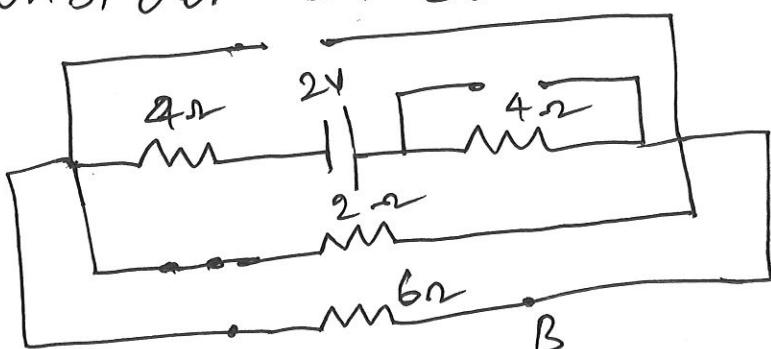


$$6/12 = 1.5 \Omega$$

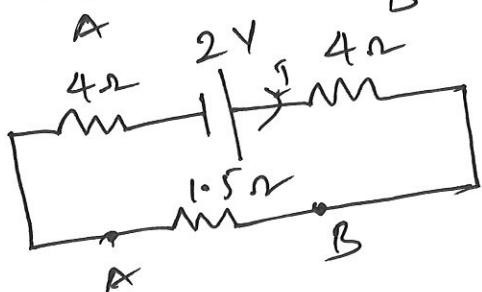

$$I = \frac{2}{4 + 4 + 1.5} = \frac{0.21 A}{}$$


(12)

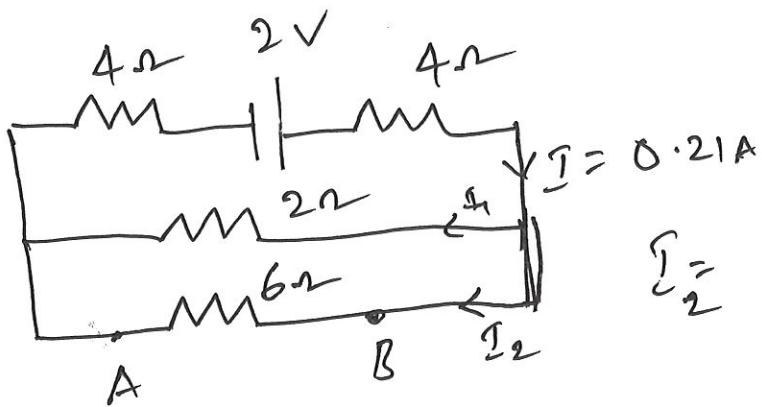

$$I_2 = \frac{0.21 \times 2}{2+8} = 0.042A$$


$$I_{6\Omega}(2V) = 0.042A \text{ (B to A)}$$

Consider 5V Source

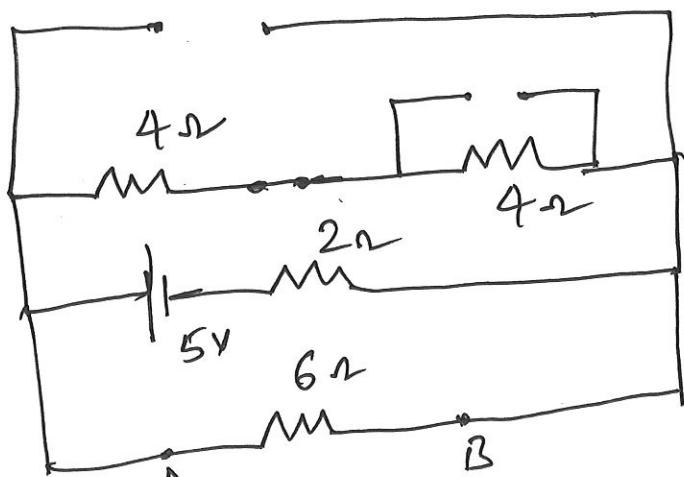


$$4+4=8\Omega$$
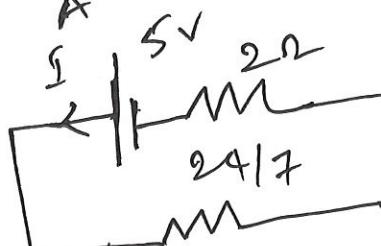
$$8\Omega \parallel 6\Omega = \frac{24}{7}\Omega$$



$$I = 0.921A$$

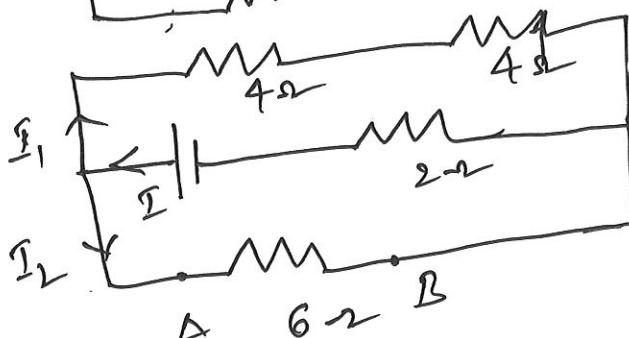

$$I_2 = 0.526A$$



$$I_{6\Omega}(5V) = 0.526A \text{ (A to B)}$$

$$I_{6\Omega} = 1.05 + 0.21 + 0.042 - 0.526 = 0.776A \text{ (B to A)}$$

$$P = V_{6\Omega} \cdot I_{6\Omega} = \frac{I_{6\Omega}^2 \cdot R}{6\Omega} = \underline{3.61W}$$

(13)


8.

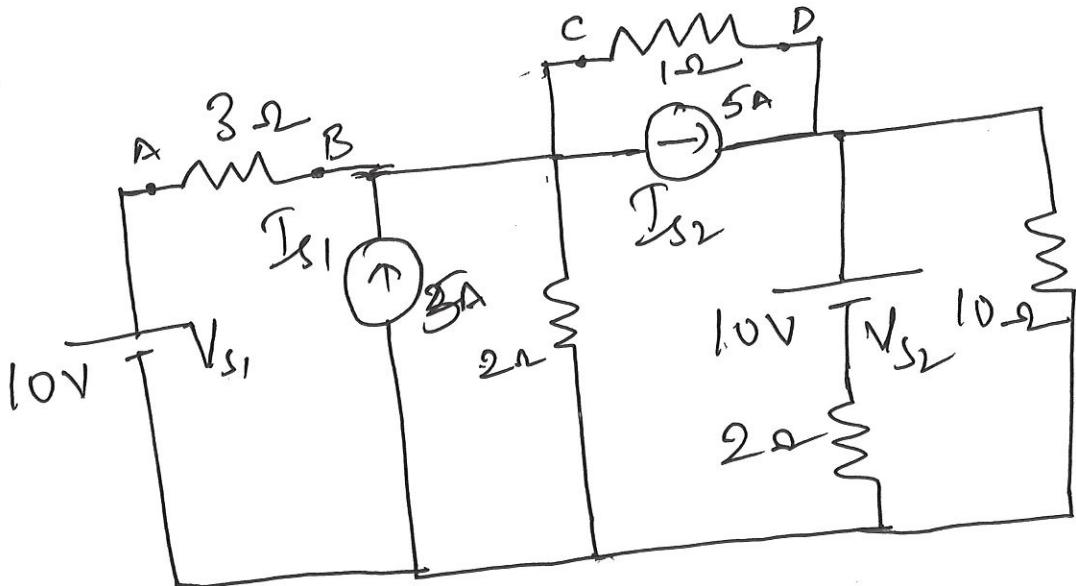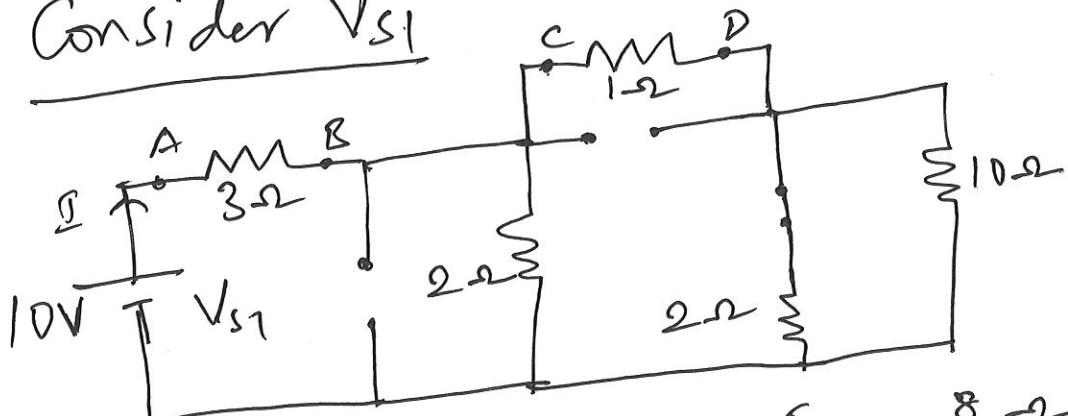Consider V_{S1} 

$$2\Omega \parallel 10\Omega = \frac{5}{3}\Omega \quad 1 + \frac{5}{3} = \frac{8}{3}\Omega$$

$$2\Omega \parallel \frac{8}{3}\Omega = \frac{8}{7}\Omega \quad \frac{8}{7}\Omega + 3\Omega = \frac{29}{7}\Omega$$

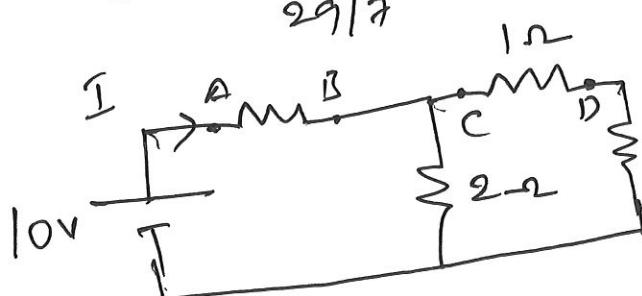
$$I = \frac{10}{29/7} = 2.41A \quad I_{3\Omega}(10V) = 2.41 \text{ (A to B)}$$



$$I_{1\Omega} = \frac{2.41 \times 2}{2 + 1 + 5/3} \\ = 1.03A$$



$$I_{1\Omega}(10V) = 1.03A \text{ (C to D)}$$

Consider V_{S2}

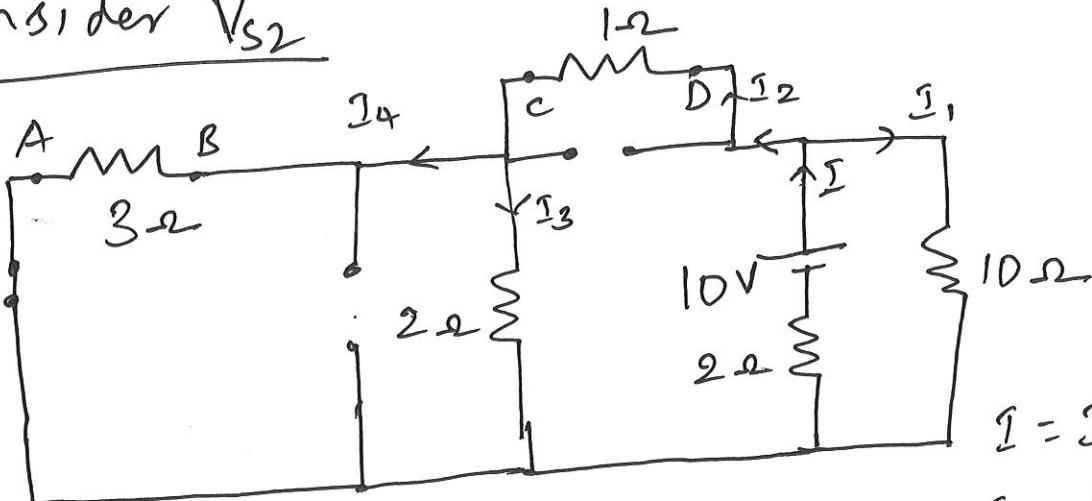

$$3 \parallel 2 = \frac{6}{5} \Omega \quad \frac{6}{5} + 1 = \frac{11}{5} \Omega$$

$$I_2 = I_3 + I_4$$

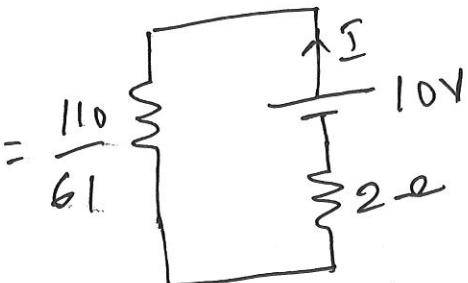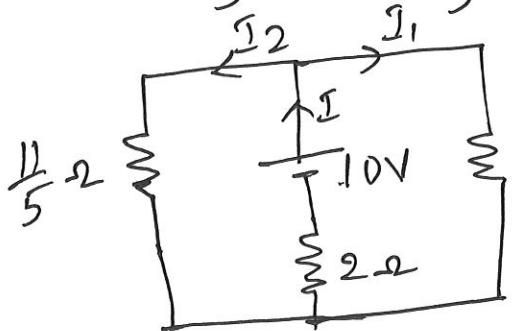


$$I = 2.63 \text{ A} \quad \left(= \frac{10}{\frac{110}{61} + 2} \right)$$

$$I_2 = \frac{2.63 \times 10}{10 + \frac{11}{5}} = 2.16 \text{ A} \quad I_{1-2} = 2.16 \text{ A} \quad (\text{D to C})$$

$$I_4 = \frac{2.16 \times 2}{2+3} = 0.864 \text{ A} \quad I_{3-2} = 0.864 \text{ A} \quad (\text{B to A})$$

Consider I_{S1}

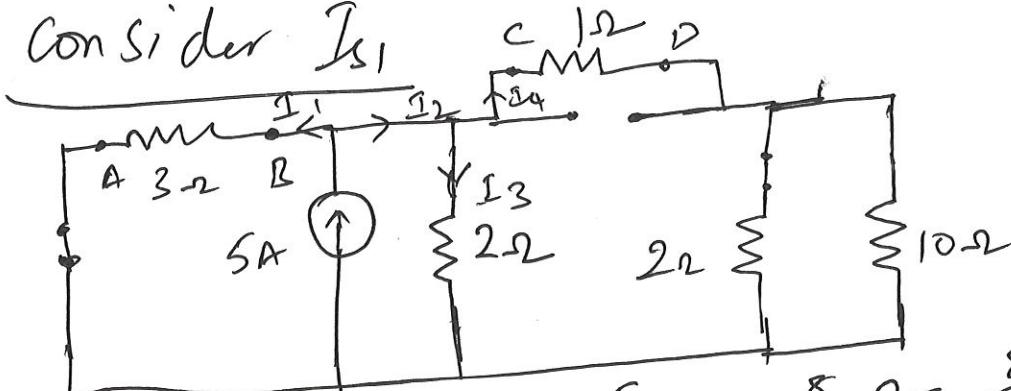

$$2 \parallel 10 = \frac{5}{3} \Omega$$

$$\frac{5}{3} + 1 = \frac{8}{3} \Omega$$

$$\frac{8}{3} \parallel 2 = \frac{8}{7} \Omega$$

(15)


$$I_1 = \frac{5 \times \frac{8}{7}}{3 + \frac{8}{7}} = 1.38 \text{ A} \quad I_{3\text{n}}(I_{S1}) = 1.38 \text{ A (B to A)}$$

$$I_2 = 5 - 1.38 = 3.62 \text{ A}$$

$$I_4 = \frac{3.62 \times 2}{2 + 1 + 5/3} = 1.55 \text{ A (C to D)}$$

$$I_{1-2}(I_{S1}) = 1.55 \text{ A (C to D)}$$


Consider I_{S2}

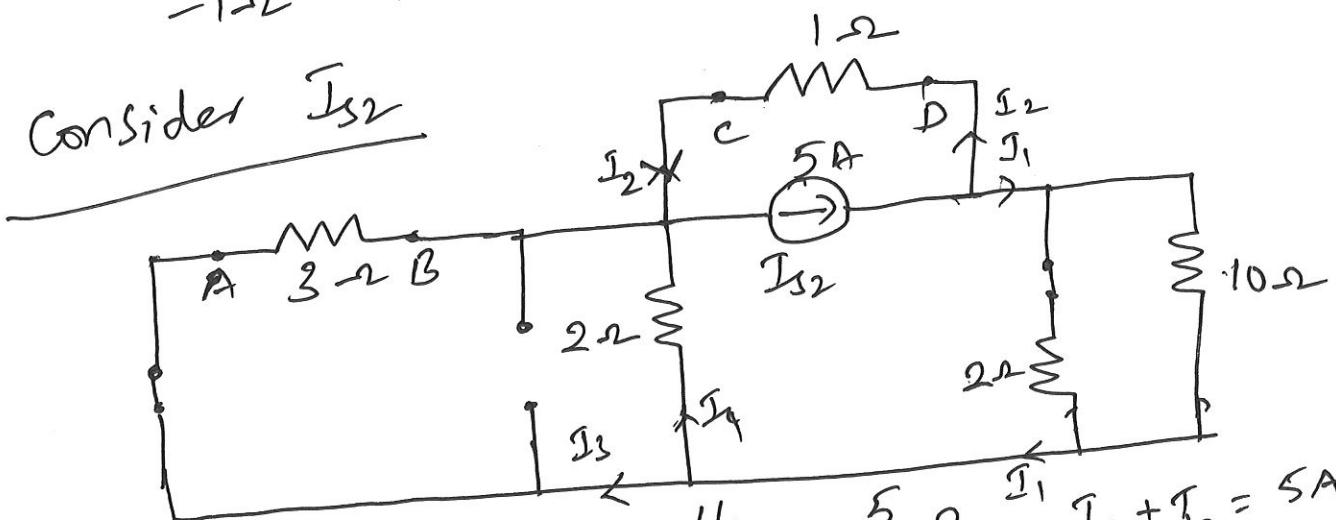

$$3//2 = 1.2 \text{ ohm}$$

$$2//10 = \frac{5}{3} \text{ ohm} \quad I_1 + I_2 = 5 \text{ A}$$

$$I_1 = I_3 + I_4$$

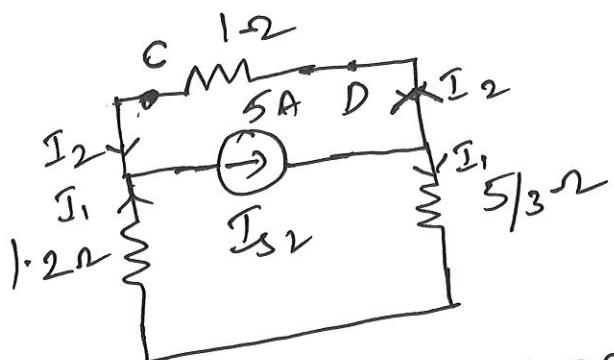

$$I_1 = \frac{5 \times 1}{1 + 1.2 + \frac{5}{3}} = 1.29 \text{ A}$$

$$I_2 = 3.71 \text{ A} \quad I_{1\text{n}}(I_{S2}) = 3.71 \text{ A (D to C)}$$

$$I_3 = \frac{1.29 \times 2}{2 + 3} = 0.516 \text{ A} \quad I_{3\text{n}}(I_{S2}) = 0.516 \text{ A (A to B)}$$

(16)


$$I_{32} = 2.41 - 0.864 - 1.38 + 0.516 \\ = 0.682 \text{ A}$$

$$P_{32} = 1.4 \text{ W}$$



$$I_{12} = 1.03 - 2.16 + 1.55 - 3.71 = -3.29 \text{ A}$$

$$P_{12} = 10.82 \text{ W}$$

9.

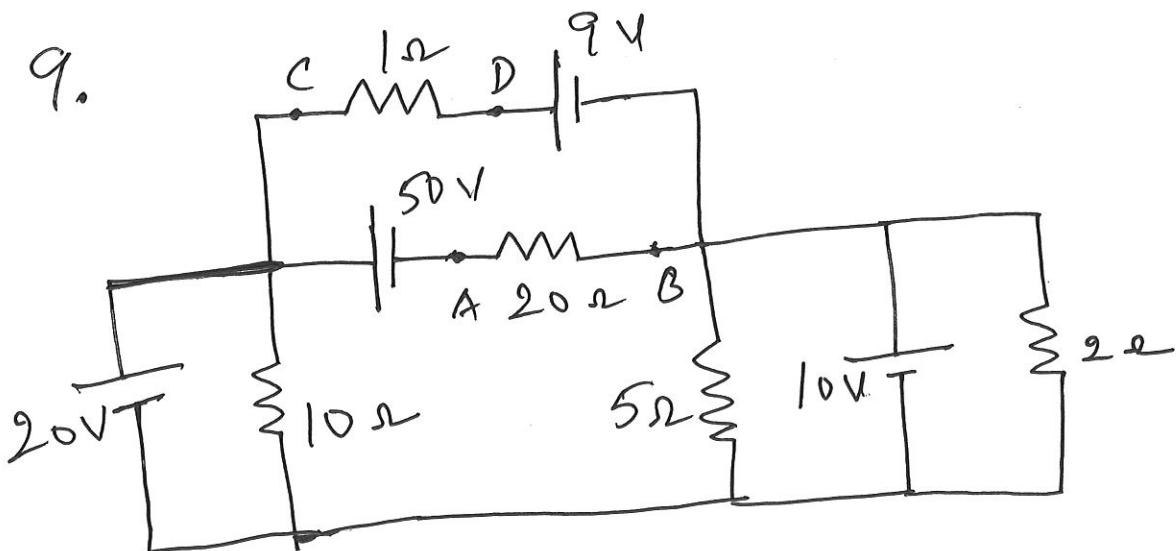

Consider 20 V source

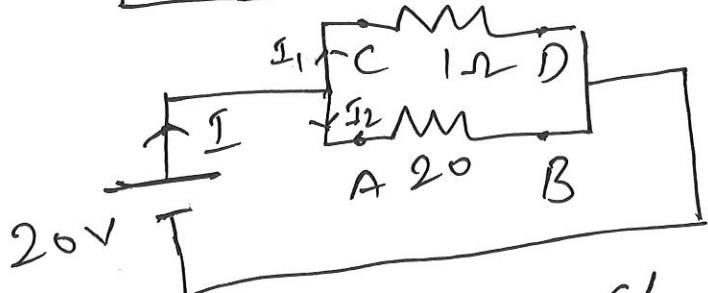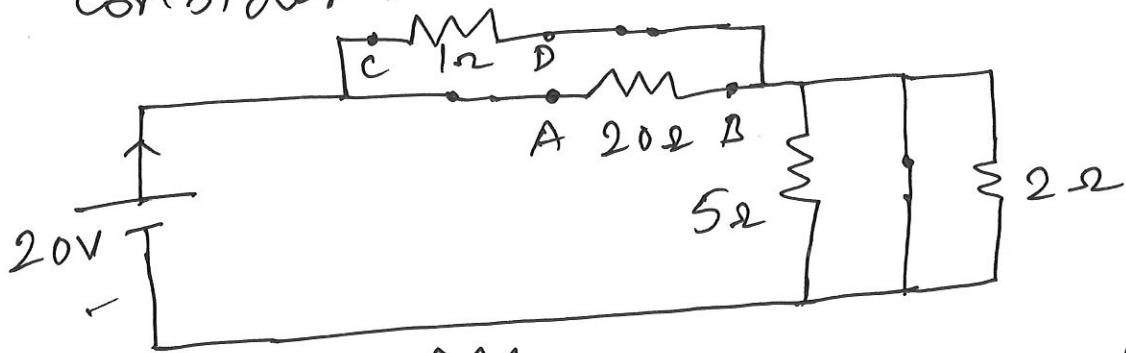

$$I_1 = \frac{20 \times 2}{21} = 19.05 \text{ A}$$

$$I_2 = 0.95 \text{ A}$$

$$I_{12}(20\text{V}) = 19.05 \text{ A} (\text{C to D})$$

$$I_{20\Omega}(20\text{V}) = 0.95 \text{ A} (\text{A to B})$$

(17)


$$I = \frac{20}{20//1} = \frac{20}{20/21} = 21 \text{ A}$$

$$I_1 = \frac{21 \times 20}{21} = 20 \text{ A} \quad I_2 = 1 \text{ A}$$


$$I_{12}(20V) = 20 \text{ A} \quad (\text{C to D})$$

$$I_{20\Omega}(20V) = 1 \text{ A} \quad (\text{A to B})$$

Consider 10V source

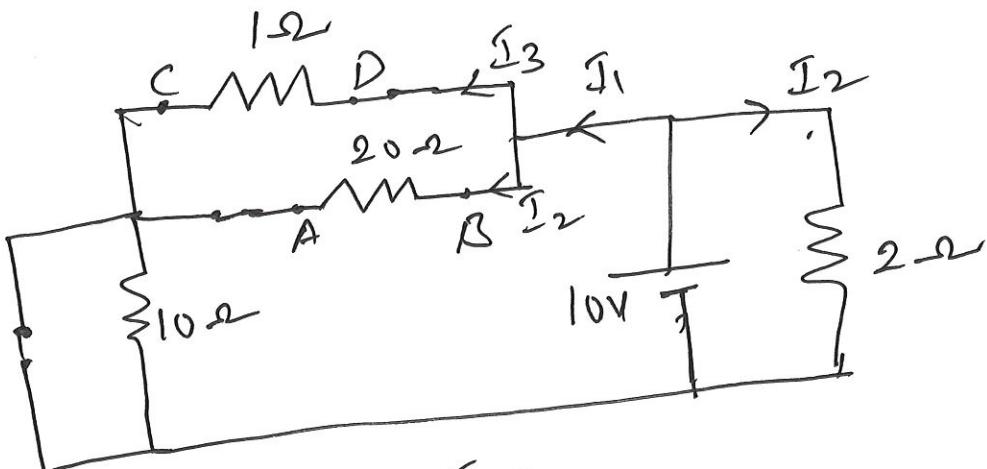

$$20//1 = 0.95 \Omega$$

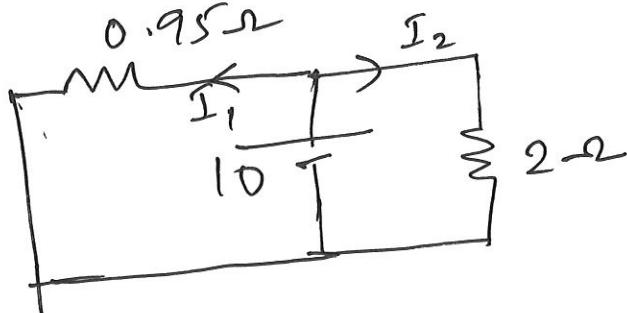


$$I_1 = \frac{10}{0.95} = 10.5 \text{ A}$$

$$I_2 = \frac{10.5 \times 1}{21} = 0.5 \text{ A} \quad I_1 = 10 \text{ A}$$


$$I_{20\Omega}(10V) = 0.5 \text{ A} \quad (\text{B to A})$$

$$I_{12}(10V) = 10 \text{ A} \quad (\text{B to C})$$

Consider 9V Source

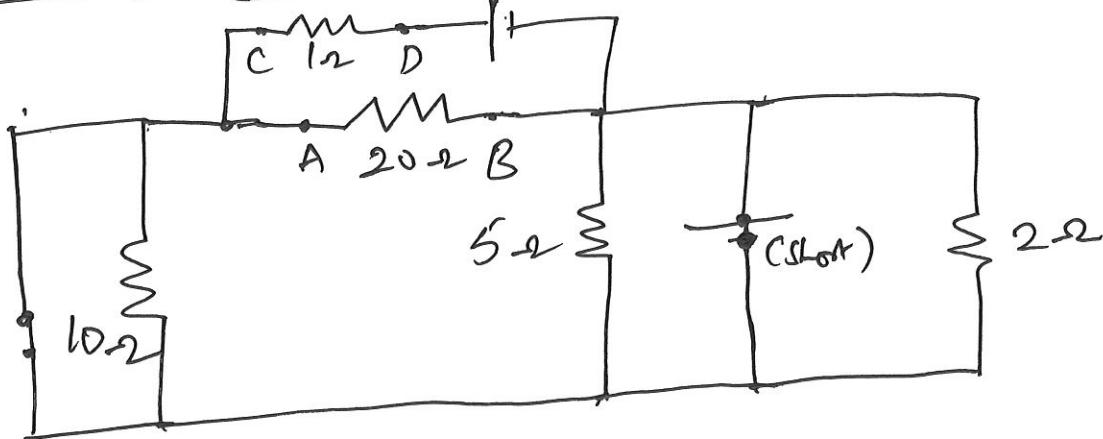


Simplifying,

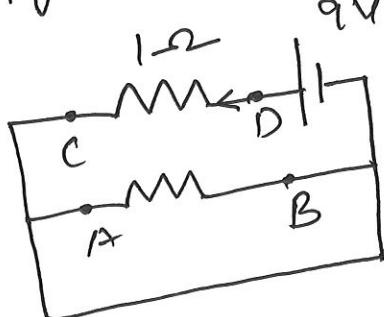



$$I_{20\Omega}(9V) = 0A$$

$$I_{1\Omega}(9V) = 9A \text{ (D to C)}$$

Consider 50V Source

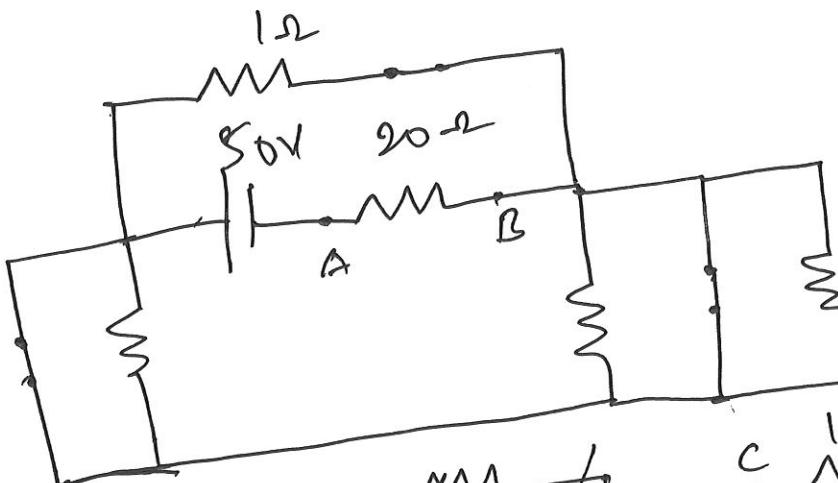

Simplifying

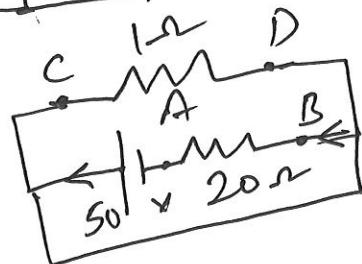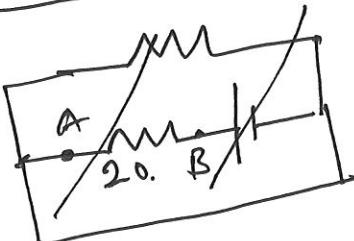

$$I_{20\Omega}(50V) = 2.5A \text{ (B to A)}$$

$$I_{1\Omega}(50V) = 0A$$

(19)

$$I_{20-2} = 1 - 0.5 + 0 - 2 \cdot 5 = -2 A$$

$$P_{20-2} = 80 W$$

$$I_{1-2} = 20 - 10 - 9 + 0 = 1 A$$

$$P_{1-2} = 1 W$$