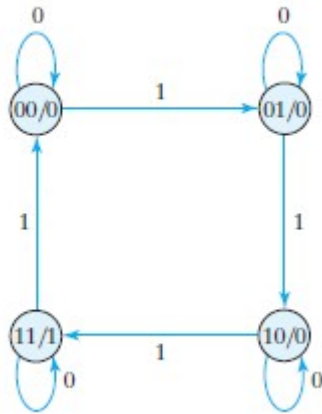


## Tutorial 12

### ECSE104L

Q1. Design circuit for the given state diagram using T flip flop.



Q2. Design circuit for the given state diagram using D flip flop.

