



BENNETT
UNIVERSITY
A TIMES GROUP INITIATIVE

Passive Circuit Elements

Rama Komaragiri

Passive Circuit Elements



- Circuit components (or circuit elements) which cannot control current by means of another electrical signal are called passive devices
- Example: Resistors, Capacitors and Inductors

Capacitors – Energy Storage Devices



Objective of Lecture

Explain the construction of a capacitor and how charge is stored.

Explain several types of capacitors

To calculate the relationship between charge, voltage, and capacitance

To calculate charging and discharging time of a capacitor

Find the relation between voltage, current, and capacitance; power; and energy

Evaluating Equivalent capacitance when a set of capacitors are in series and in parallel

Impedance of a capacitor

Capacitor

- Two conductive plates separated by an insulator (or dielectric) forms a capacitor.


- Commonly illustrated as two parallel metal plates separated by a distance, d .

$$C = \frac{\epsilon A}{d}$$

where $\epsilon = \epsilon_r \epsilon_0$

ϵ_r is the relative dielectric constant

ϵ_0 is the vacuum permittivity

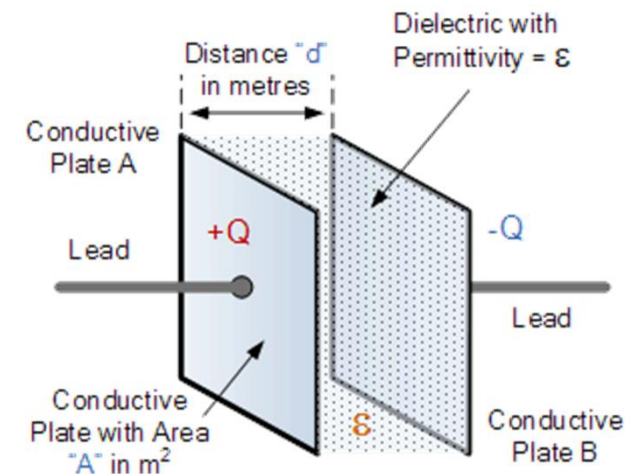


<http://www.electronics-tutorials.ws/capacitor/cap1a.gif>

Effect of Dimensions

- Capacitance increases with
 - increasing surface area of the plates,
 - decreasing spacing between plates, and
 - increasing the relative dielectric constant of the insulator between the two plates.

$$C = \frac{\epsilon A}{d}$$

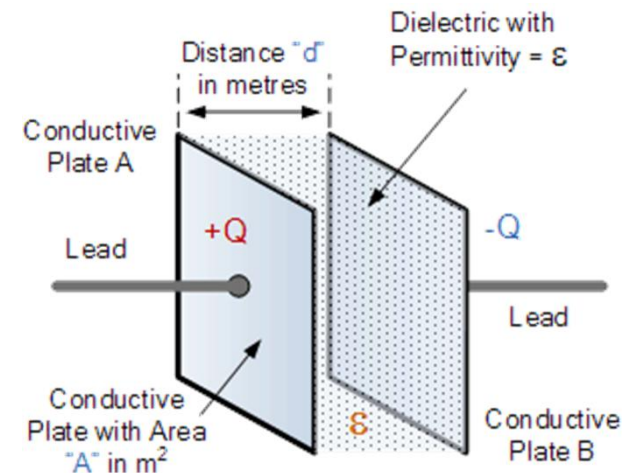

<http://www.electronics-tutorials.ws/capacitor/cap1a.gif>

Types of Capacitors

➤ Fixed Capacitors

– Nonpolarized

- May be connected into circuit with either terminal of capacitor connected to the high voltage side of the circuit.

- Insulator: Paper, Mica, Ceramic, Polymer


– Electrolytic

- The negative terminal must always be at a lower voltage than the positive terminal


- Plates or Electrodes: Aluminum, Tantalum

Nonpolarized

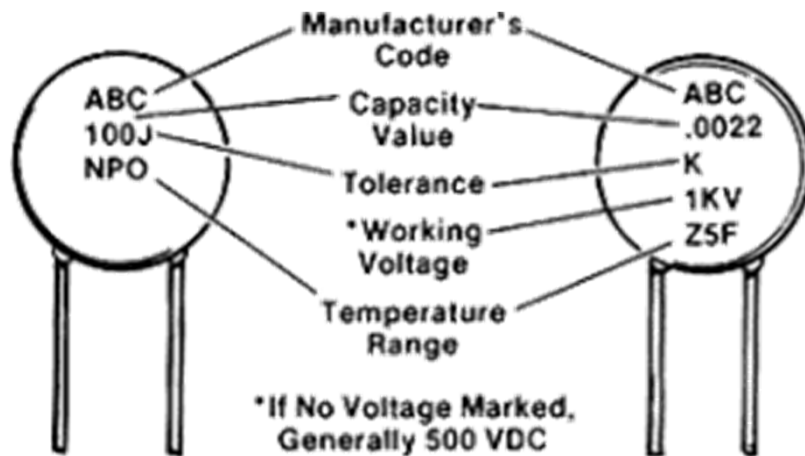- Difficult to make nonpolarized capacitors that store a large amount of charge or operate at high voltages.
 - Tolerance on capacitance values is very large
 - can be as high as $\pm 50\%$




Circuit Symbol

 


https://technick.net/img/guide_rcc/guide_rcc_cap_cdc.gif

Nonpolarized

➤ Cross section

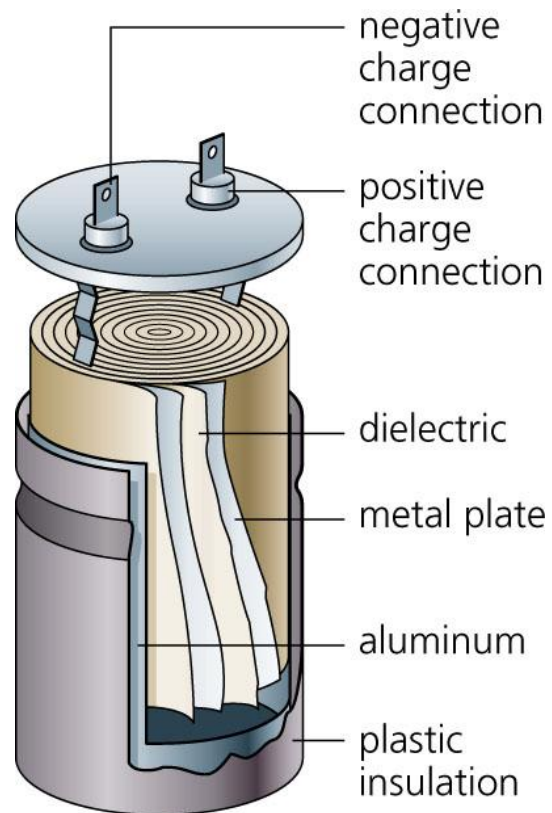


Circuit Symbol

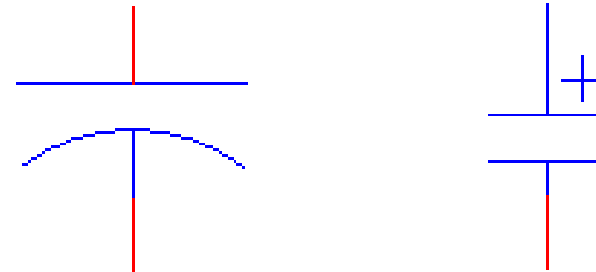


<http://www.digitivity.com/articles/capacitor-breakdown-thumb-404x615.jpg>

Variable Capacitors

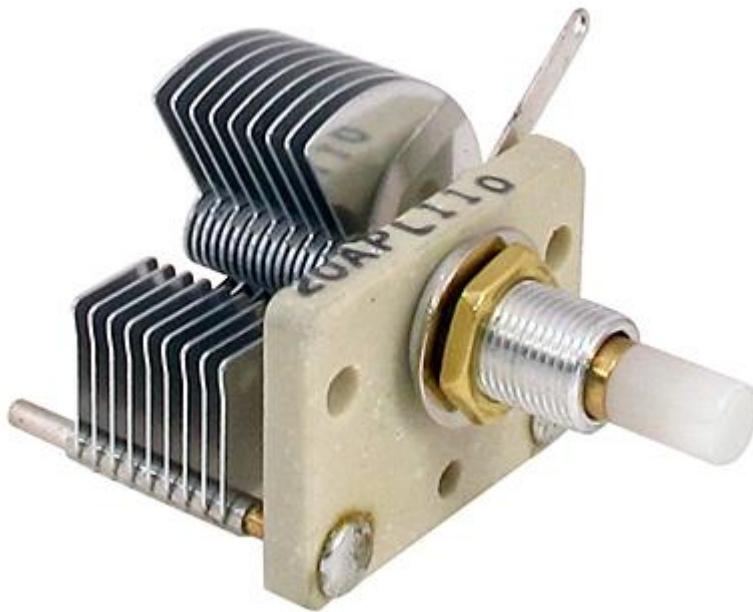- Cross-section area of capacitor plate is changed as one set of plates are rotated with respect to the other.





Circuit Symbol

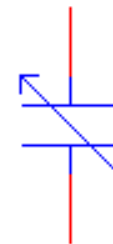

http://www.surplussales.com/Images/Capacitors/VariableCapacitors/cav-apl20-111_lg.jpg

MEMS Capacitor

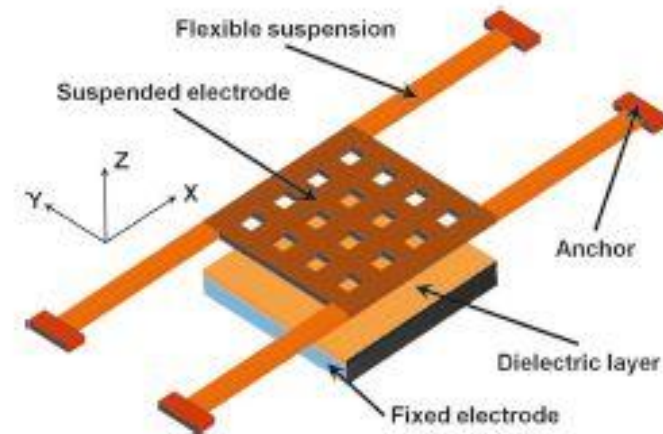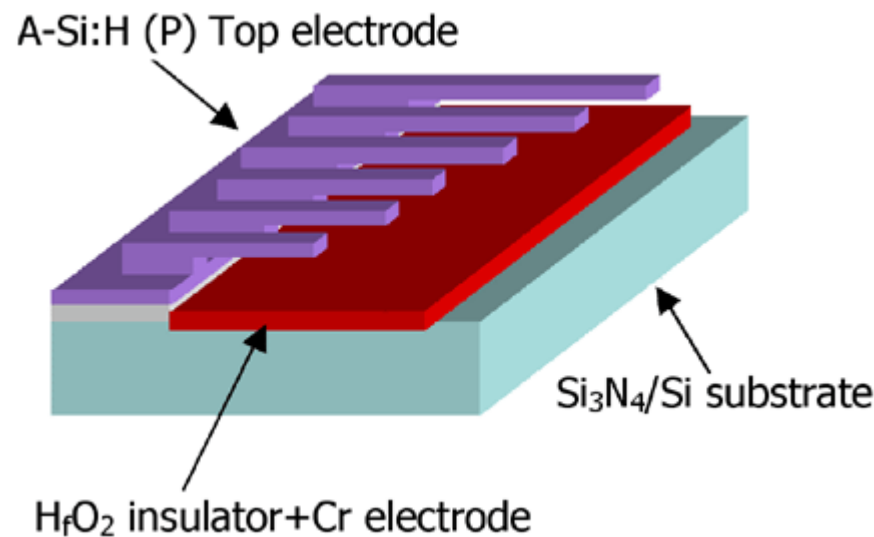- MEMS (Microelectromechanical system)
 - Can be a variable capacitor by changing the distance between electrodes.
 - Use in sensing applications as well as in RF electronics.




https://download.e-bookshelf.de/download/0003/9354/58/L-X-0003935458-0002444823.XHTML/images/Ch01_image001.jpg

[http://www.silvaco.com/tech lib TCAD/simulationstandard/2005/aug/a3/a3.html](http://www.silvaco.com/tech_lib_TCAD/simulationstandard/2005/aug/a3/a3.html)

Electric Double Layer Capacitor

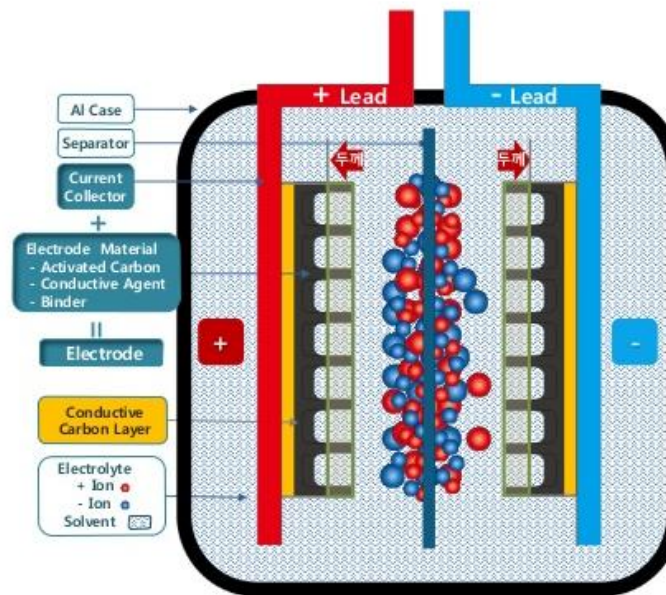- Also known as a supercapacitor or ultracapacitor
 - Used in high voltage/high current applications.
 - Energy storage for alternate energy systems.



<https://image.slidesharecdn.com/vinatechsupercapacitoraplicaciones-151113113806-lva1-app6891/95/supercapacitor-typical-applications-10-638.jpg?cb=1447415061>


Electrical Properties of a Capacitor

- Acts like an open circuit at steady state when connected to a d.c. voltage or current source.
- Voltage on a capacitor must be continuous
 - There are no abrupt changes to the voltage, but there may be discontinuities in the current.
- An ideal capacitor does not dissipate energy, it uses power when charging energy and returns power when discharging energy.

Sign Conventions

The sign convention used with a capacitor is the same as for a power dissipating device.

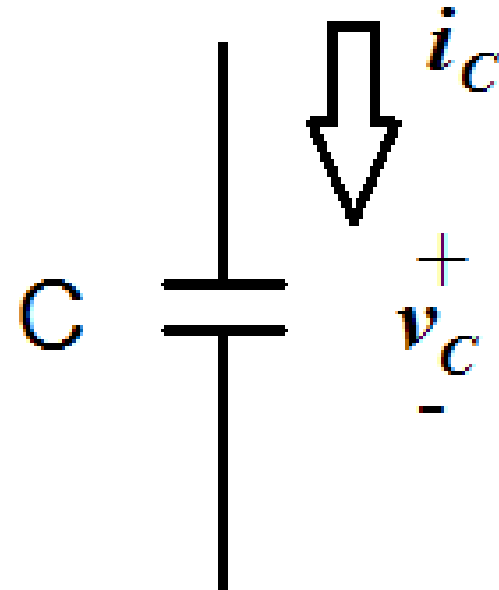- When current flows into the positive side of the voltage across the capacitor, it is positive and the capacitor is dissipating power.
- When the capacitor releases energy back into the circuit, the sign of the current will be negative.



Current-Voltage Relationships

$$q = Cv_c$$

➤ Let

$$v_c = V_0 \sin(\omega t)$$

$$i_c = \frac{dq}{dt}$$

$$i_c = C \frac{d}{dt} (V_0 \sin(\omega t))$$

$$= \omega C V_0 \cos(\omega t)$$

$$i_c = C \frac{dv_c}{dt}$$

$$= \omega C V_0 \sin\left(\frac{\pi}{2} - \omega t\right)$$

$$v_c = \frac{1}{C} \int_{t_o}^{t_1} i_c dt$$

➤ Current through capacitor leads voltage across capacitor by $\frac{\pi}{2}$

➤ What is the significance of above statement?

Current-Voltage Relationships

➤ Let $v_c = V_0 e^{j\omega t}$

$$i_c = C \frac{d}{dt} (V_0 e^{j\omega t}) = j\omega C V_0 e^{j\omega t}$$

$$i_c = C \frac{dv_c}{dt}$$

$$v_c = \frac{1}{C} \int_{t_0}^{t_1} i_c dt$$

➤ Re-writing the equation (similar to that of $V = IR$)

$$v_c = \frac{1}{j\omega C} i_c = -jX_c i_c = Z_c i_c, X_c = \frac{1}{\omega C}$$

➤ X_c is called as reactance (in ohm) of the capacitor

- When $\omega = 0$, $X_c = \infty$, means reactance is infinite → Capacitor blocks DC
- When $\omega = \infty$, $X_c = 0$, means capacitor behaves like a short at higher frequencies
- Frequency dependent electrical behavior of capacitance on circuit

Energy Storage

- Charge is stored on the plates of the capacitor.


Equation:

$$Q = CV$$

Units:

Farad = Coulomb/Voltage

Farad is abbreviated as F

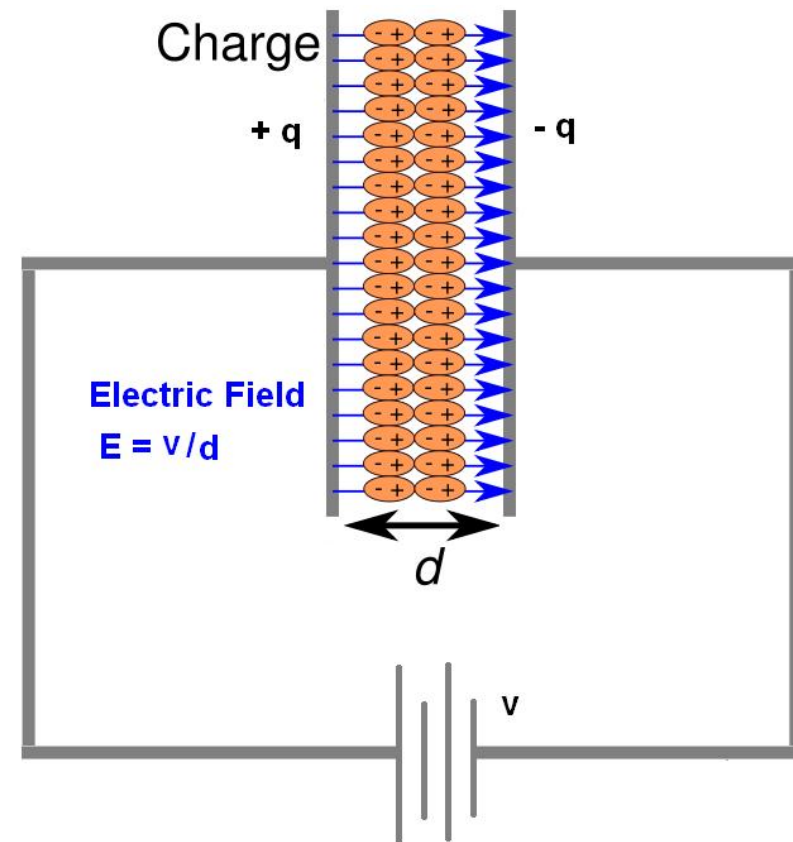

Power and Energy

- P is power and E is energy
- An ideal capacitor stores energy when charged and gives away energy while discharging

$$p_C = i_C v_C$$


$$p_C = C v_C \frac{dv_C}{dt}$$

$$w_C = \frac{1}{2} C v_C^2$$

$$w_C = \frac{q^2}{2C}$$

Capacitors in Parallel

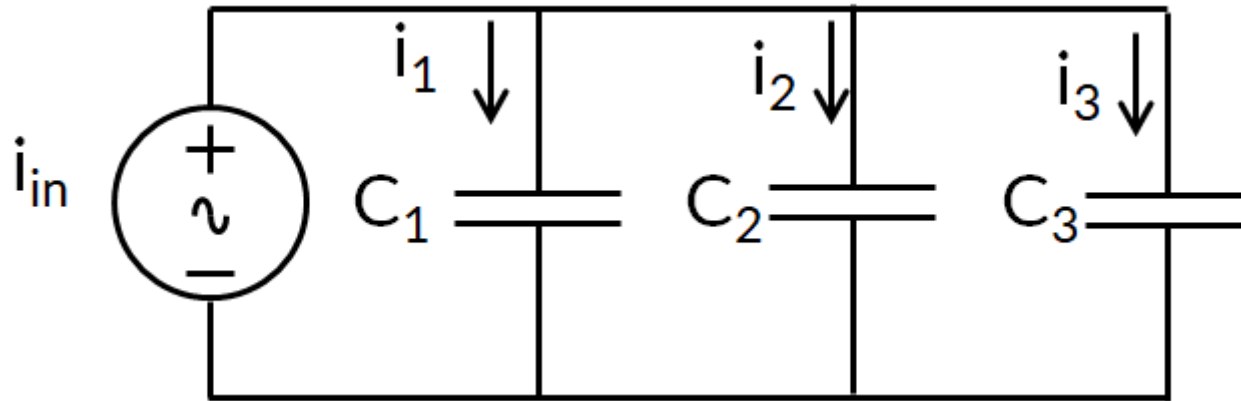- Consider capacitors connected in parallel configuration
 - Voltage across the capacitors is equal
 - Current divides



- Writing KCL,

$$i_{in} = i_1 + i_2 + i_3$$

- Noting the current voltage relation for a capacitor as $i = C \frac{dv}{dt}$

C_{eq} for Capacitors in Parallel

- If C_{eq} is the net capacitance, then $i_{in} = C_{eq} \frac{dv}{dt}$
- Writing current voltage relations for individual capacitances as

$$i_1 = C_1 \frac{dv}{dt}, i_2 = C_2 \frac{dv}{dt}, i_3 = C_3 \frac{dv}{dt}$$


- Substituting into KCL,

$$i_{in} = C_1 \frac{dv}{dt} + C_2 \frac{dv}{dt} + C_3 \frac{dv}{dt}$$

- Thus


$$C_{eq} = C_1 + C_2 + C_3$$

$$C_{eq} = \sum_{p=1}^m C_p$$

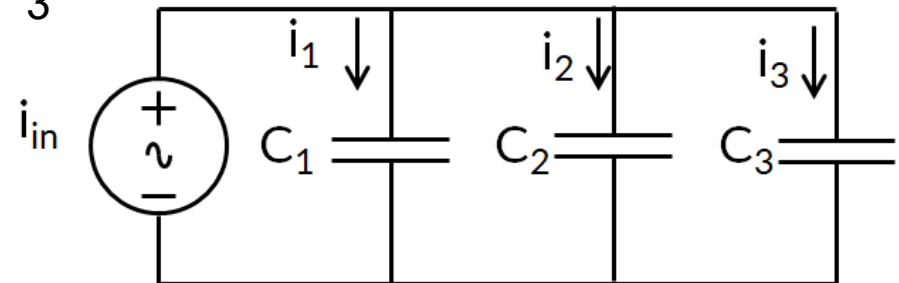

Capacitors in Series

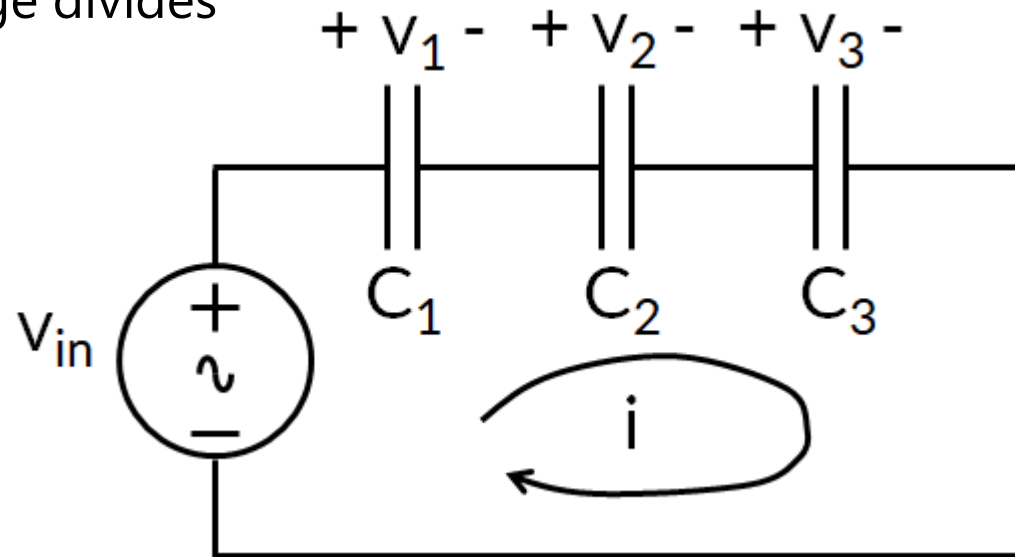- Consider capacitors connected in series configuration
 - Current through the capacitors is same
 - Voltage divides



- Applying KVL

$$V_{in} = V_1 + V_2 + V_3$$

C_{eq} for Capacitors in Series

- Noting the relation between voltage across the capacitor and current through a capacitor as

$$v_1 = \frac{1}{C_1} \int_{t_0}^{t_1} i dt, v_2 = \frac{1}{C_2} \int_{t_0}^{t_1} i dt, v_3 = \frac{1}{C_3} \int_{t_0}^{t_1} i dt$$

- If C_{eq} is the total capacitance, then

$$v_{in} = \frac{1}{C_{eq}} \int_{t_0}^{t_1} i dt$$

- Substituting back into KVL

$$v_{in} = \frac{1}{C_1} \int_{t_0}^{t_1} i dt + \frac{1}{C_2} \int_{t_0}^{t_1} i dt + \frac{1}{C_3} \int_{t_0}^{t_1} i dt$$

- Thus,

$$\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3}$$

$$C_{eq} = \left[\sum_{s=1}^n \frac{1}{C_s} \right]^{-1}$$

General Equations for C_{eq}

➤ Parallel Combination

- If m capacitors are in parallel, then

$$C_{eq} = \sum_{p=1}^m C_p$$


• Series Combination

- If n capacitors are in series, then:

$$C_{eq} = \left[\sum_{s=1}^n \frac{1}{C_s} \right]^{-1}$$

Properties of a Real Capacitor

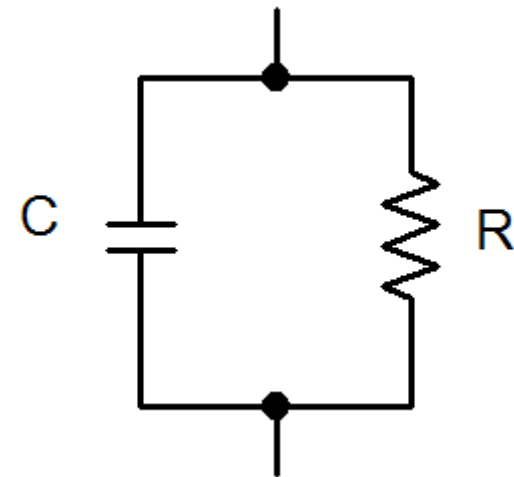- A real capacitor does dissipate energy due leakage of charge through its insulator.
 - Real capacitor is modeled by keeping a resistor in parallel with an ideal capacitor.



Charging a capacitor


- One of the functions of capacitor is storing charge (and thus energy)
- Capacitor has an ability to store charge when a potential difference is applied across the capacitor plates
- Energy is stored in the electric field between positive and negative plates.
- When a voltage is applied across a capacitor, current flows into the capacitor plates and develops a potential difference across the capacitor
- With time, the potential difference between the battery and the capacitor become smaller and the flow rate of electrons (thus current flow) reduces
- The charging process continues until the capacitor becomes fully charged.
- The charging current follows an exponential curve.

Charging a capacitor

- To start with, it is easy to store charge in the capacitor.
- As more charge is stored on the plates of the capacitor, it becomes increasingly difficult to place additional charge on the plates due to Coulombic repulsion
- When the initial charge on the capacitor plates is small, as charge is stored on the capacitor plates, the voltage across the capacitor increases rapidly
- As the charge on the capacitor plates increases, it becomes difficult to add extra charges on plate and voltage across the capacitor increases more slowly
- Coulombic repulsion from the charge already on the plates creates an opposing force to limit the addition of more charge on the plates
- The charging current follows an exponential curve.

Charging a capacitor

- Consider the circuit shown in figure

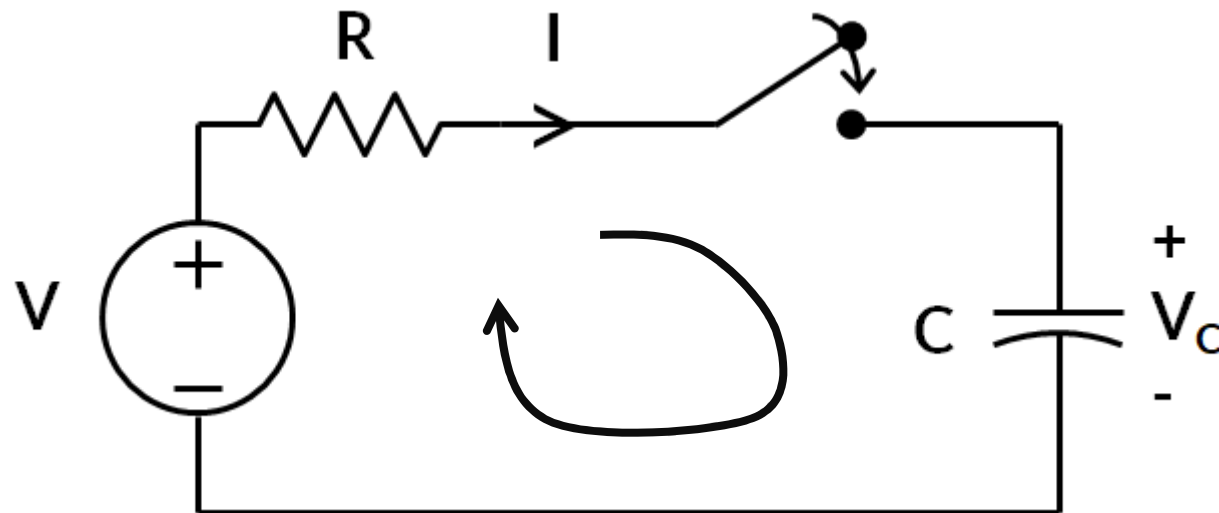

- Apply KVL

$$V = V_R + V_C$$

- Noting that $C = \frac{q}{V_C} \Rightarrow V_C = \frac{q}{C}$ and $V_R = Ri_C$

Charging a capacitor

$$V = iR + \frac{q}{C}$$

$$VC = RC \frac{dq}{dt} + q$$


$$VC - q = RC \frac{dq}{dt}$$

$$\int \frac{dt}{RC} = \int \frac{dq}{VC - q} \quad \int \frac{dt}{RC} = - \int \frac{d(VC - q)}{VC - q}$$

$$C_1 + \frac{t}{RC} = -\ln(VC - q)$$

$$VC - q = e^{C_1 - \frac{t}{RC}}$$
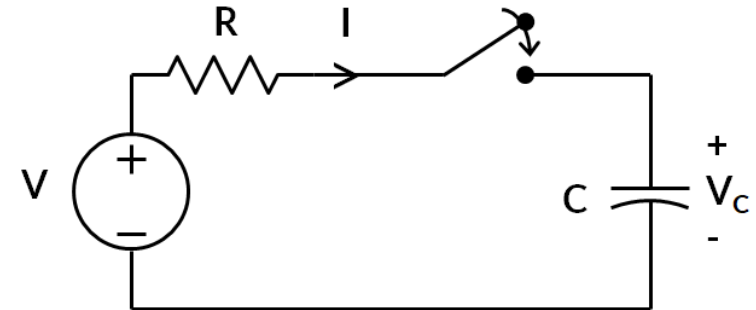
$$VC - q = C_2 e^{-\frac{t}{RC}} \quad C_2: \text{Integration constant, } (e^{C_1} = C_2)$$



C_1 : Integration constant

Charging a capacitor

- Using the initial boundary condition: at time $t = 0$, when the capacitor is not initially uncharged, $q = 0$

$$VC - q = C_2 e^{-\frac{t}{RC}} \Rightarrow C_2 = VC$$

$$VC - q = VC e^{-\frac{t}{RC}}$$


$$q = VC \left(1 - e^{-\frac{t}{RC}} \right)$$

$$V_C = \frac{q}{C} = V \left(1 - e^{-\frac{t}{RC}} \right) \Rightarrow \boxed{V_C = V \left(1 - e^{-\frac{t}{RC}} \right)}$$

$$i = \frac{dq}{dt} = VC \frac{d}{dt} \left(1 - e^{-\frac{t}{RC}} \right) \quad i = VC \left(0 - e^{-\frac{t}{RC}} \times -\frac{1}{RC} \right) \Rightarrow \boxed{i = \frac{V}{R} e^{-\frac{t}{RC}}}$$

Note: C_2 indicates total charge in the system, not stored in the capacitor

Charging of a capacitor

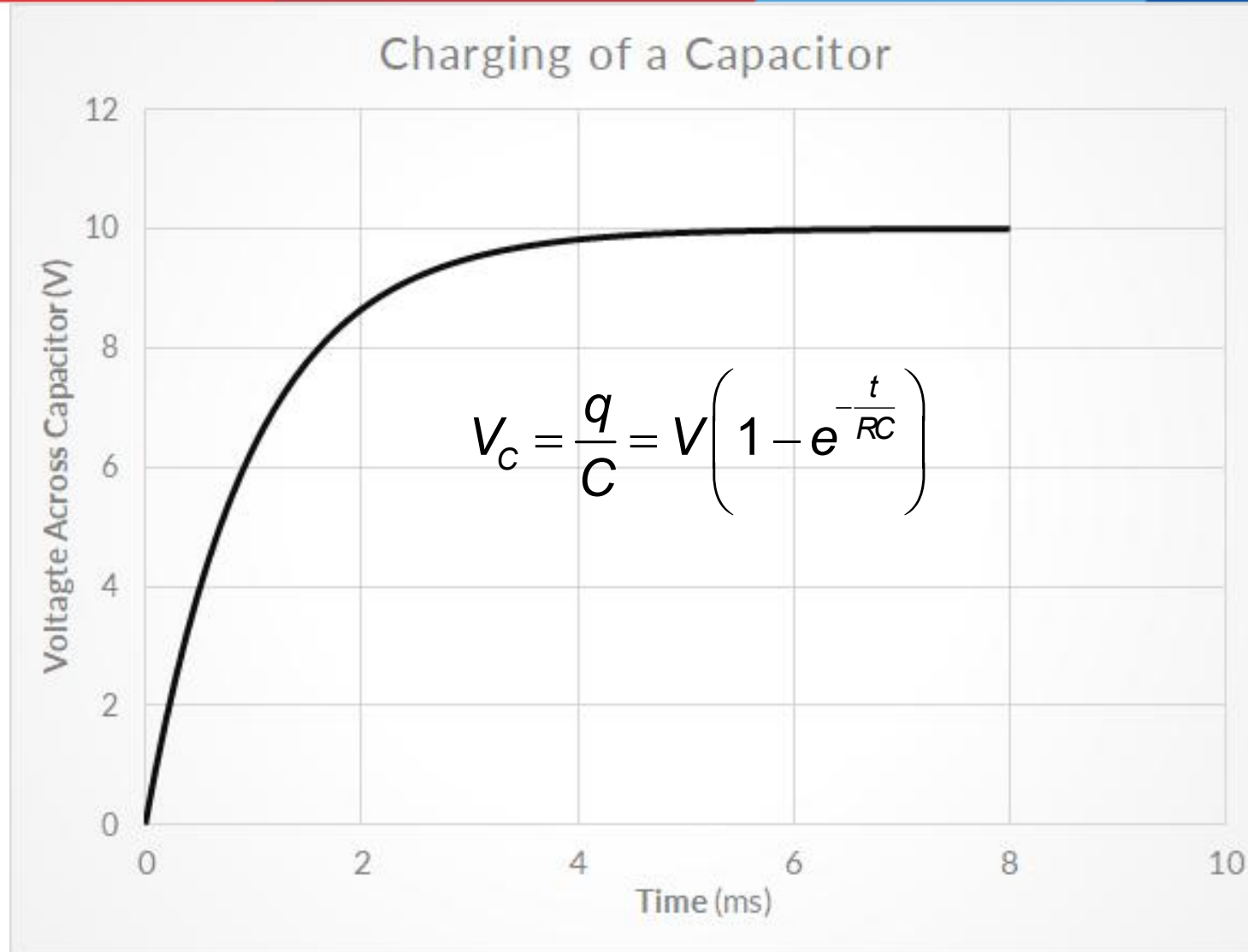

Time Constant

- The rate of charging is determined by the charging equation determined by the RC constant in the exponential term.

$$V_c = \frac{q}{C} = V(1 - e^{-t/RC})$$

- The term RC is termed the **time constant (most famously RC time constant)** since it affects the rate of charge. Mathematically, this is the time taken for the capacitor to reach 0.632 of the fully charged value.

Time Constant

- According to the charging equation, theoretically, capacitors takes infinite time to charge completely.
- For all practical purposes, it is assumed that a capacitor can be charged completely in only five times of the time constant, meaning the capacitor is said fully charged after $5 \times RC$.
- After 5 time constant, q , V_c and current will be over 99% ($1 - e^{-5} = 0.9932$) to their final values.

Example: Charging a Capacitor

- An uncharged capacitor of capacitance $400\ \mu\text{F}$ is connected to a $50\ \text{V}$ D.C. supply in series along with a current limiting resistor of $5\ \text{k}\Omega$. Calculate


- The voltage of the capacitor at the end of 0.4 seconds of charging
- The charging current at the end of 0.4 seconds
- The time taken for the capacitor to be charged to 30 volts.

- i. Using the charge formula,

$$\tau = RC = 200 \times 10^{-6} \times 5 \times 10^3 = 2\ \text{sec}$$

$$V_c = \frac{q}{C} = V \left(1 - e^{-\frac{t}{\tau}} \right)$$
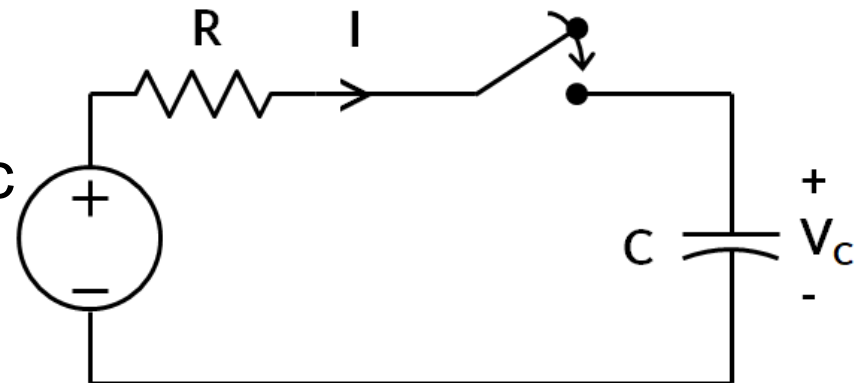
$$V_c = 50 \left(1 - e^{-\frac{0.4}{2}} \right) = 9.06\ \text{V}$$



Example: Charging a Capacitor

ii) The charging current at the end of 0.4 seconds

$$i_c = \frac{V}{R} e^{-\frac{t}{RC}} \quad i_c = \frac{50}{2000} e^{-\frac{0.4}{2}} = 4.53 \text{ mA}$$

iii) To charge the capacitor to 30 Volts, using the formula,

$$V_c = \frac{q}{C} = V \left(1 - e^{-\frac{t}{\tau}} \right) \quad 30 = 50 \left(1 - e^{-\frac{t}{2}} \right)$$

$$1 - 0.6 = e^{-\frac{t}{2}} \quad -\frac{t}{2} = \ln(0.4) = -0.916$$

$$t = 1.83 \text{ s}$$

Charging an initially charged Capacitor

- The ability to add charge to a capacitor depends on:
 - the amount of charge already on the plates of the capacitor and the force (voltage) driving the charge towards the plates (i.e., current)
- If at the start of charging, the capacitor is charged to a voltage of V_1 Volts,
- Then the initial condition gets modified as at $t = 0$, $q = CV_1$
- Thus, applying boundary condition

$$C_2 = C(V - V_1)$$

$$VC - CV_1 = C_2 e^{-\frac{t}{RC}}$$

$$VC - q = C(V - V_1) e^{-\frac{t}{RC}}$$

$$q = VC(1 - e^{-\frac{t}{RC}}) + V_1 C e^{-\frac{t}{RC}}$$

Charging an initially charged Capacitor

$$V_C = \frac{q}{C} = V - Ve^{-\frac{t}{RC}} + V_1 e^{-\frac{t}{RC}}$$

$$V_C = V \left(1 - e^{-\frac{t}{RC}} \right) + V_1 e^{-\frac{t}{RC}}$$

$$i_c = \frac{dq}{dt} = VC \frac{d}{dt} \left(1 - e^{-\frac{t}{RC}} \right) + V_1 C \frac{d}{dt} \left(e^{-\frac{t}{RC}} \right)$$

$$i_c = \frac{V}{R} e^{-\frac{t}{RC}} - \frac{V_1}{R} e^{-\frac{t}{RC}} \Rightarrow i_c(t) = \frac{(V - V_1)}{R} e^{-\frac{t}{RC}}$$

Example: Charging an initially charged Capacitor

- A capacitor of capacitance $400\ \mu\text{F}$ is initially charged to $40\ \text{V}$ is connected to a $80\ \text{V}$ D.C. supply in series along with a current limiting resistor of $5\ \text{k}\Omega$. Calculate the voltage of the capacitor at the end of 0.4 seconds of charging.
- **Solution:** Using the formula for capacitor with an initial voltage,

$$V_C = V + (V_1 - V)e^{-\frac{t}{RC}}$$

$$\tau = RC = 2\ \text{sec}$$

$$V_C = 80 + (40 - 80)e^{-\frac{0.4}{2}} = 47.25\ \text{V}$$

Discharging a Capacitor



- › Coulombic repulsion between charges already existing the plates creates a force that lets charges to discharge out of the capacitor once the voltage on the charge in the capacitor is decreased
- › Coulombic repulsion decreases as charge more charge is removed from the capacitor plates.
- › Initially, voltage across the capacitor decreases rapidly as charge is removed from the plates
- › As more and more charge is removed, voltage across the capacitor decreases more slowly as it becomes difficult to force the remaining charge out of the capacitor.

Discharging a capacitor

› Applying KVL

$$V_R + V_C = 0$$

$$0 = i \times R + \frac{q}{C}$$

$$-\frac{q}{C} = i \times R$$

$$-\int \frac{dq}{RC} = \int \frac{dq}{q}$$


$$-\frac{t}{RC} + C_1 = \ln q$$

$$q = e^{-t/RC + C_1}$$

$$q = C_2 e^{-\frac{t}{RC}}$$

C_1 : integration constant

C_2 : integration constant

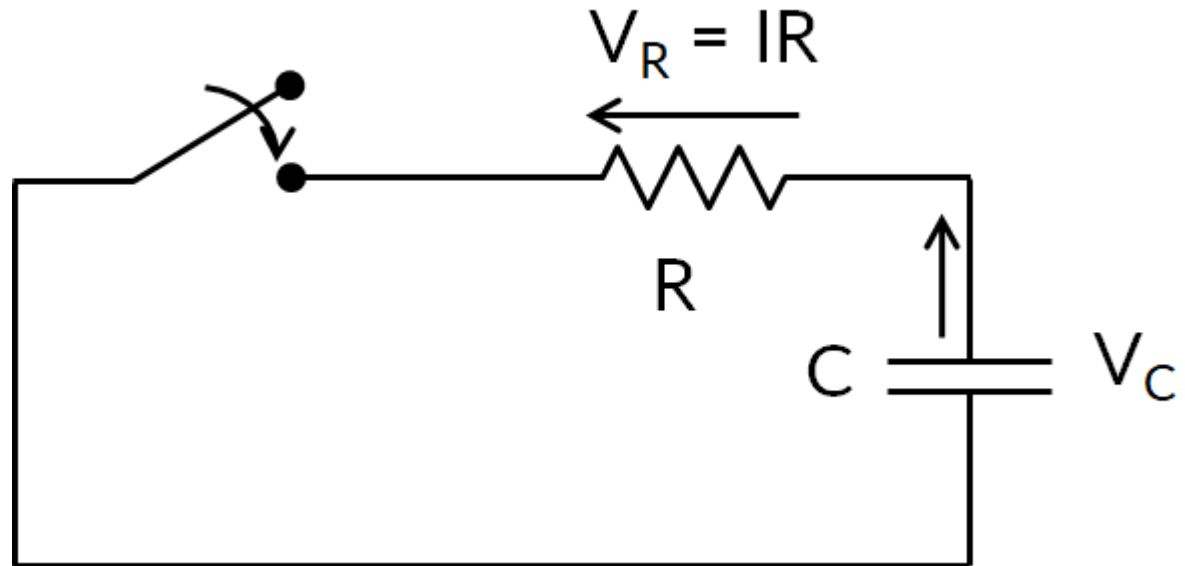

Discharging a capacitor

Substitute boundary condition, at $t = 0$,

Voltage across $C = V$, $q = VC$

$$C_2 = VC$$
$$q = VCe^{-\frac{t}{RC}}$$


$$V_c = \frac{q}{C} = Ve^{-\frac{t}{RC}}$$

$$i = \frac{dq}{dt} = VC \times -\frac{1}{RC} e^{-\frac{t}{RC}}$$

$$i = -\frac{V}{R} e^{-\frac{t}{RC}}$$

(Note that the negative sign indicate that the current is opposite to the charging current's direction)

Discharging a capacitor

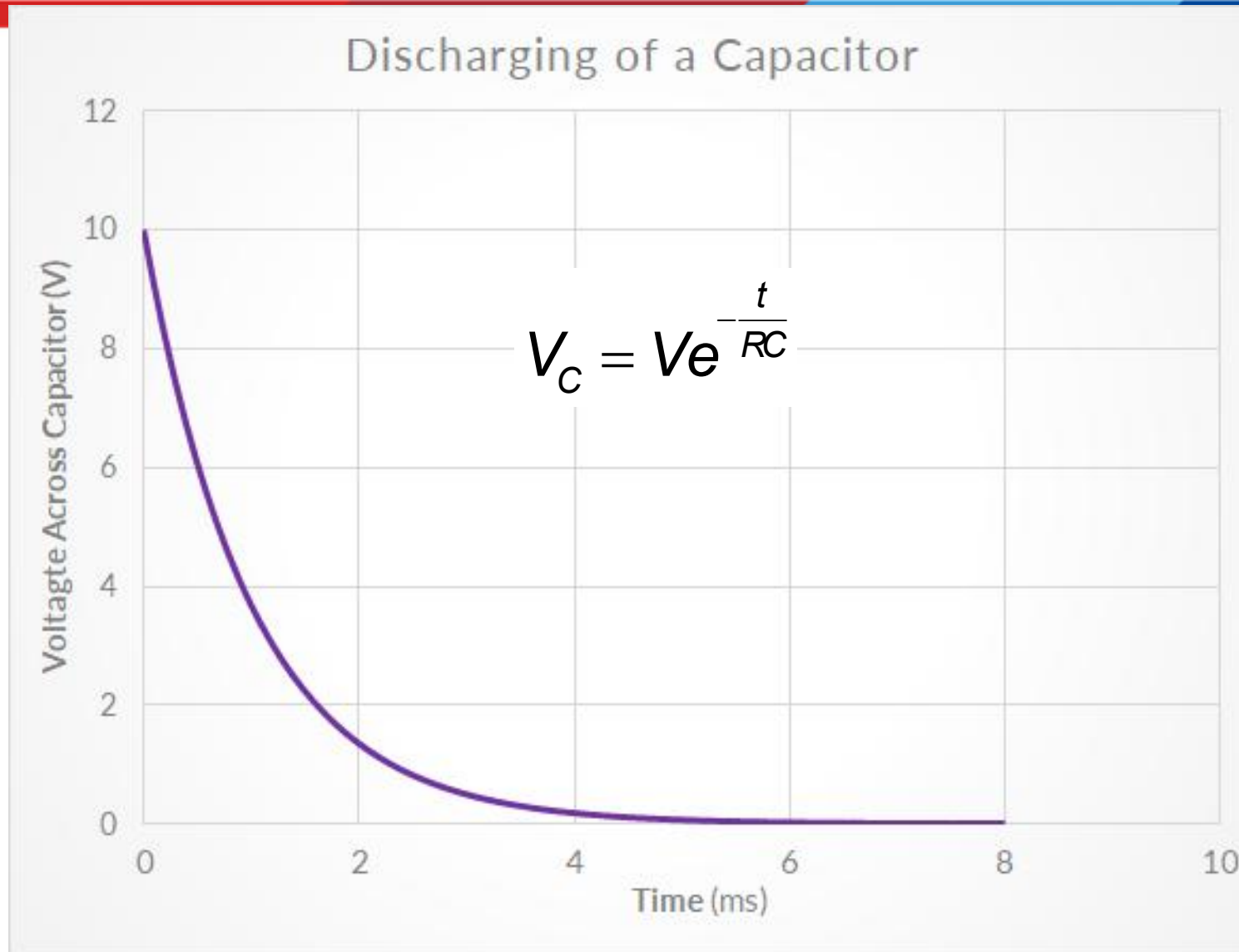


Example: Discharging a capacitor

- A 2 μF capacitor previously charged to 40 Volts is to be discharged through a resistance of 5 $\text{k}\Omega$. Find the voltage across the terminals of the capacitor at the end of 18 ms.
- **Solution:** Using the formula for a discharging capacitor,

$$V_C = V e^{-\frac{t}{RC}} \quad \tau = RC = 10 \text{ ms}$$
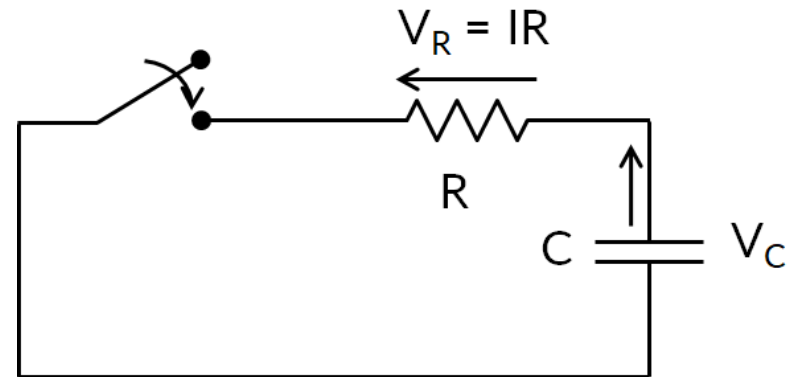
$$V_C = 40 e^{-\frac{18}{10}} = 6.61 \text{ V}$$



Example: Discharging a capacitor

- A $1000\ \mu\text{F}$ capacitor previously charged to 80 Volts is
to be discharged through a resistance of $20\ \text{k}\Omega$. Find
the voltage across the terminals of the capacitor at the
end of 15 seconds.

Summary

- Capacitors are energy storage devices.
- Capacitor stores energy in electric field
- A capacitor act like an open circuit at steady state when a DC voltage or current has been applied.
- Capacitor behaves like a open circuit at very low frequencies and as a short circuit at higher frequencies
- Reactance of a capacitor decreases as frequency of operation increases
- In a capacitor, current leads voltage by a phase $\pi/2$ (voltage or lags current by a phase $\pi/2$)

Summary

- The voltage across a capacitor must be a continuous function; the current flowing through a capacitor can be discontinuous.

$$i_C = C \frac{dv_C}{dt} \quad v_C = \frac{1}{C} \int_{t_0}^{t_1} i_C dt$$

- RC time constant is a time constant in which the charge on capacitor can increase or decrease by a factor e
- The equations for equivalent capacitance for

capacitors in parallel

$$C_{eq} = \sum_{p=1}^P C_P$$

capacitors in series

$$C_{eq} = \left[\sum_{s=1}^S \frac{1}{C_s} \right]^{-1}$$



BENNETT
UNIVERSITY
A TIMES GROUP INITIATIVE

Inductors

Energy Storage Devices


Objective of Lecture



- Describe
 - The construction of an inductor
 - How energy is stored in an inductor
 - The electrical properties of an inductor
 - Relationship between voltage, current, and inductance; power; and energy
 - Equivalent inductance when a set of inductors are in series and in parallel

Inductors

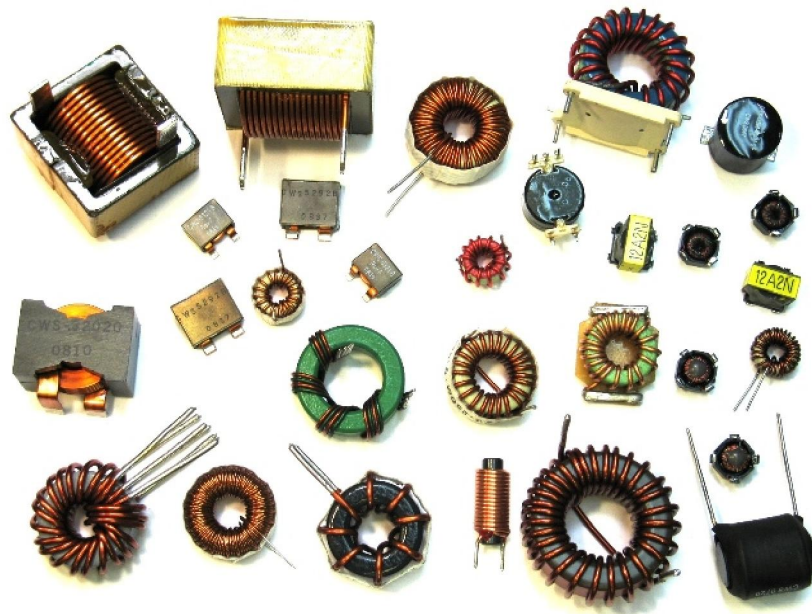- Generally formed by a coil of conducting wire
 - Conducting wire is usually wrapped around a solid core.
 - In the absence of a core, the inductor is said to have an 'air core'.




https://is.alicdn.com/img/pb/859/856/326/326856859_550.jpg
<https://www.autodesk.com/products/eagle/blog/wp-content/uploads/2017/06/Inductors-Group.jpg>


Circuit Symbols

- L , inductance, has the units of Henry (H)


$$1 \text{ H} = 1 \frac{\text{Vs}}{\text{A}}$$

Inductor symbols


generic, or air-core

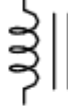
iron core

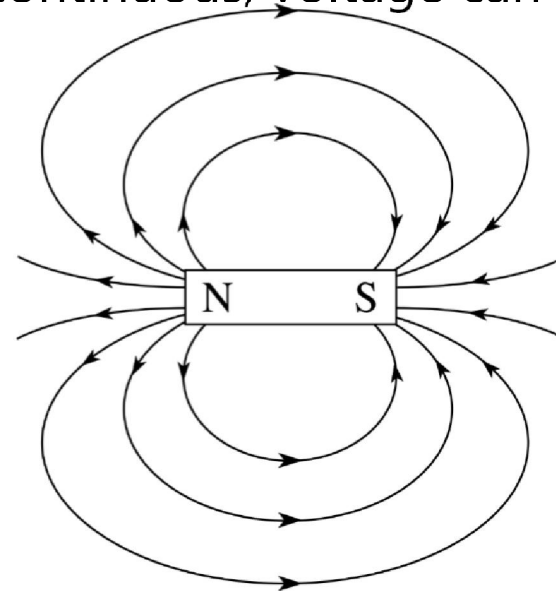
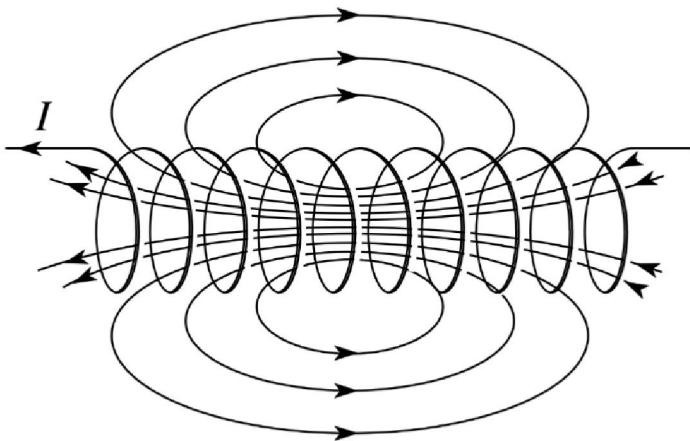

iron core
(alternative)


generic
(newer symbol)

<https://www.ibiblio.org/kuphaldt/electricCircuits/DC/00355.png>

Inductor

- Inductor stores energy in an magnetic field created by an electric current flowing through it
 - Inductor opposes change (chokes) in current flowing through a conductor.
 - Current through an inductor is continuous; voltage can be discontinuous.



http://www.physics.brocku.ca/PPLATO/h-flap/phys4_4f_4.png

Calculations of L

For a solenoid (toroidal inductor)

$$L = \frac{N^2 \mu A}{\ell} = \frac{N^2 \mu_r \mu_o A}{\ell}$$

N is the number of turns of wire


A is the cross-sectional area of the toroid in m².

μ_r is the relative permeability of the core material

μ_o is the vacuum permeability ($4\pi \times 10^{-7}$ H/m)

ℓ is the length of the wire used to wrap the toroid in meters
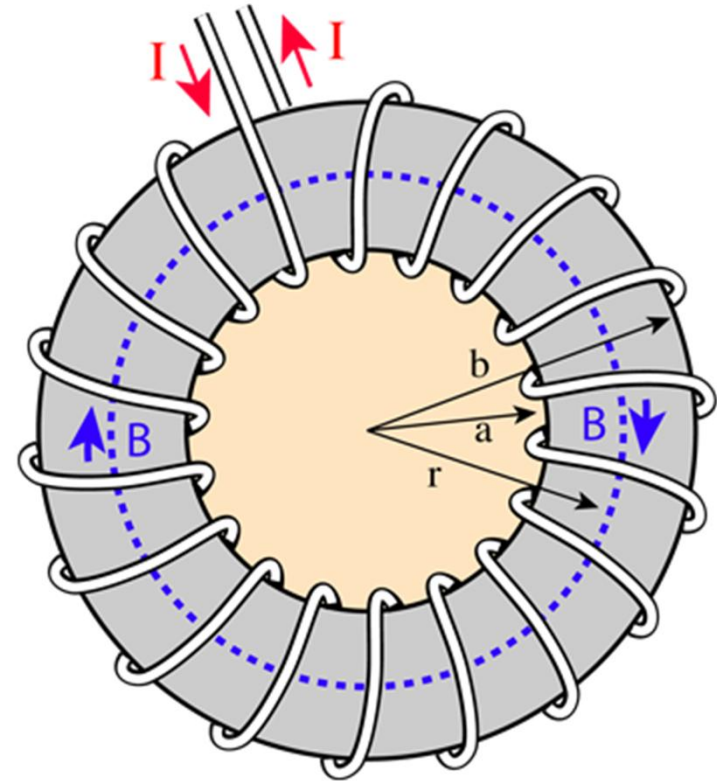
<http://hyperphysics.phy-astr.gsu.edu/hbase/magnetic/imgmag/tor.png>




Wire

- A bare wire has its share of inductance

$$L = \ell \left[\ln \left(4 \frac{\ell}{d} \right) - 1 \right] (2 \times 10^{-7}) H$$

d is the diameter of the wire in meters.

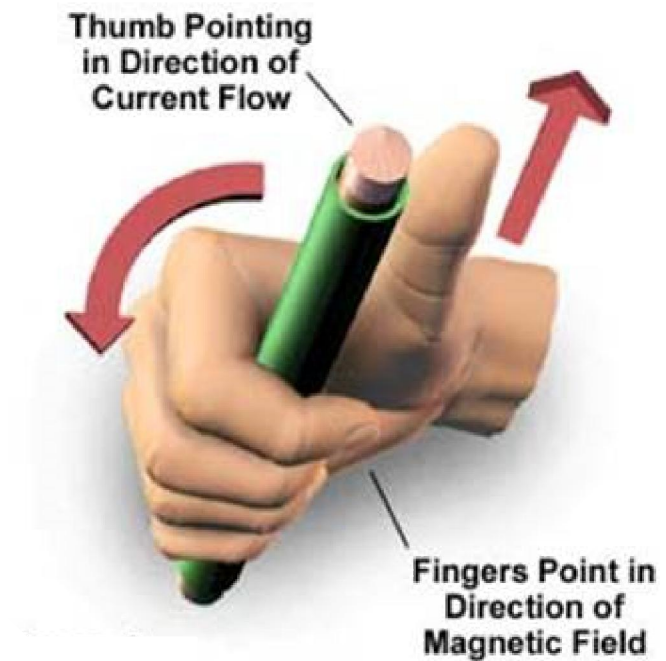


Properties of an Inductor

- Inductor acts like an short circuit in steady state
- Current through an inductor must be continuous, meaning there are no abrupt changes to the current but there can be abrupt changes in the voltage across an inductor.
- No energy or power is dissipated by an ideal inductor. Ideal inductor absorbs energy or power from the circuit when storing energy and restores energy into circuit while discharging


Properties of a Real Inductor

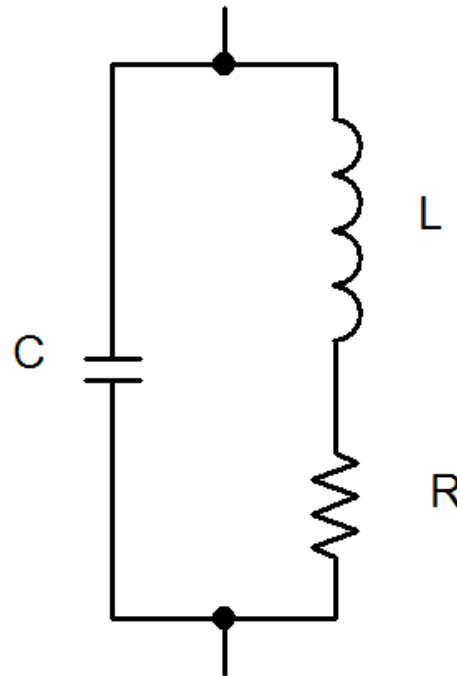- Due to resistive losses and capacitive coupling between turns of wire



Sign Convention

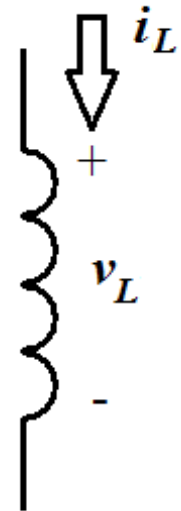- When current flows into the positive side of the voltage across the inductor, the current is positive and the inductor is dissipating power
- When an inductor releases energy back into the circuit, the sign of the current is negative.



Current - Voltage Relationships

$$v_L = L \frac{di}{dt}$$

$$i_L = \frac{1}{L} \int_{t_o}^{t_1} v_L dt$$

› Let $i_L = I_0 \sin(\omega t)$

$$v_L = L \frac{d}{dt} (I_0 \sin(\omega t))$$

$$= \omega L I_0 \sin(\omega t)$$

$$= \omega L I_0 \sin\left(\frac{\pi}{2} - \omega t\right)$$

- › Voltage across inductor leads current through inductor by $\frac{\pi}{2}$
- › What is the significance of above statement?

Current-Voltage Relationships

➤ Let $i_L = I_0 e^{j\omega t}$

$$v_L = L \frac{d}{dt} (I_0 e^{j\omega t}) = j\omega L I_0 e^{j\omega t}$$

➤ Re-writing the equation (similar to that of $V = IR$)

$$v_L = j\omega L i_L = jX_L i_L = Z_L i_L, X_L = \omega L$$

$$v_L = L \frac{di}{dt}$$

$$i_L = \frac{1}{L} \int_{t_0}^{t_1} v_L dt$$

➤ X_L is called as reactance (in ohm) of an inductor

- When $\omega = 0$, $X_L = 0$, means reactance is zero → inductor behaves like a short at DC
- When $\omega = \infty$, $X_L = \infty$, means inductor behaves like an open circuit at higher frequencies
- Frequency dependent electrical behavior of inductance on circuit


Power and Energy

$$p_L = v_L i_L = Li_L \int_{t_o}^{t_1} i_L dt$$

$$w = \int_{t_o}^{t_1} L \frac{di_L}{dt} i_L dt = L \int_{t_o}^{t_1} i_L di_L$$

Inductors in Series

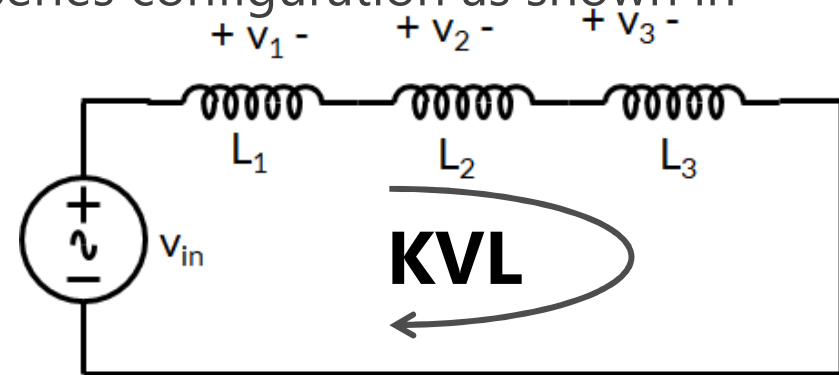- Consider inductors connected in a series configuration as shown in the circuit



- Applying KVL

$$V_{in} = V_1 + V_2 + V_3$$

- Noting the relation between voltage across the inductor and current through inductor, $V_1 = L_1 \frac{di}{dt}$, $V_2 = L_2 \frac{di}{dt}$, $V_3 = L_3 \frac{di}{dt}$
- If L_{eq} is the total inductance of the circuit, then


$$V_{in} = L_{eq} \frac{di}{dt} = L_1 \frac{di}{dt} + L_2 \frac{di}{dt} + L_3 \frac{di}{dt}$$

$$L_{eq} = L_1 + L_2 + L_3$$

$$L_{eq} = \sum_{s=1}^S L_s$$

Inductors in Parallel

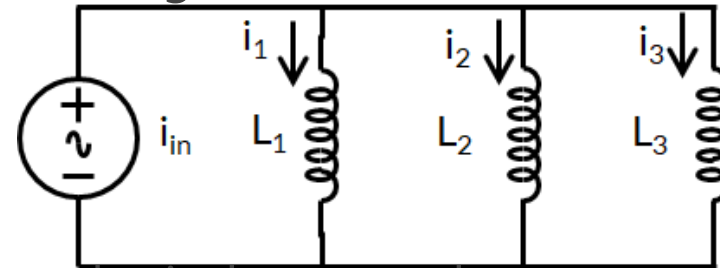- Consider inductors connected in a parallel configuration as shown in the circuit



- Applying KCL $i_{in} = i_1 + i_2 + i_3$

- Noting the relation between voltage across the inductor and current

through inductor,

$$i_1 = \frac{1}{L_1} \int_{t_0}^{t_1} v dt, i_2 = \frac{1}{L_2} \int_{t_0}^{t_1} v dt, i_3 = \frac{1}{L_3} \int_{t_0}^{t_1} v dt$$

- If L_{eq} is the total inductance of the circuit, then

$$i_{in} = \frac{1}{L_{eq}} \int_{t_0}^{t_1} v dt = \frac{1}{L_1} \int_{t_0}^{t_1} v dt + \frac{1}{L_2} \int_{t_0}^{t_1} v dt + \frac{1}{L_3} \int_{t_0}^{t_1} v dt$$

$$\frac{1}{L_{eq}} = \frac{1}{L_1} + \frac{1}{L_2} + \frac{1}{L_3} \quad L_{eq} = \left[\sum_{p=1}^n \frac{1}{L_p} \right]^{-1}$$

General Equations for L_{eq}

➤ Series Combination

- If m inductors are in series, then

$$L_{eq} = \sum_{s=1}^S L_s$$


• Parallel Combination

- If n inductors are in parallel, then:

$$L_{eq} = \left[\sum_{p=1}^n \frac{1}{L_p} \right]^{-1}$$

Current through an Inductor

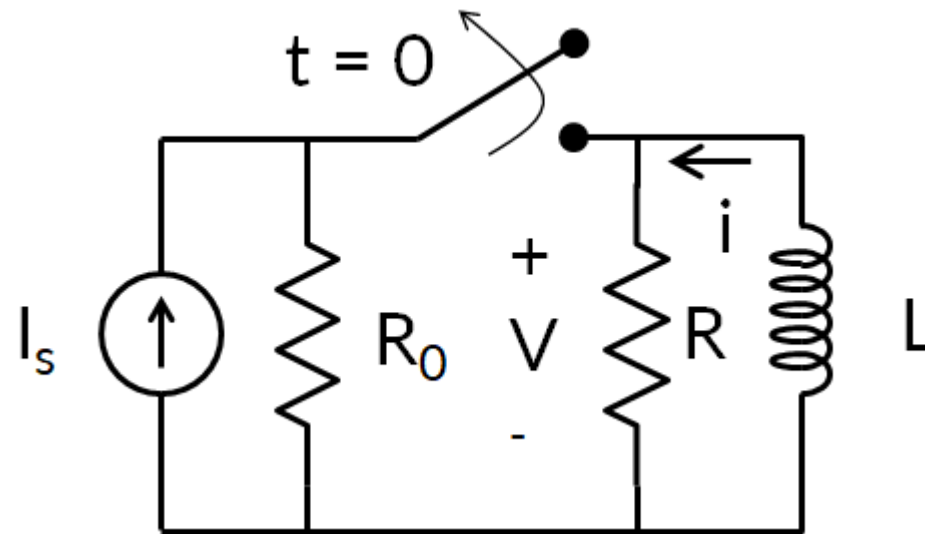
- Consider the following circuit, for which the switch is closed for $t < 0$, and at $t = 0$, the switch is opened.



- The dc voltage V across the resistor R , supplies a constant current to the RL circuit

Current through an Inductor

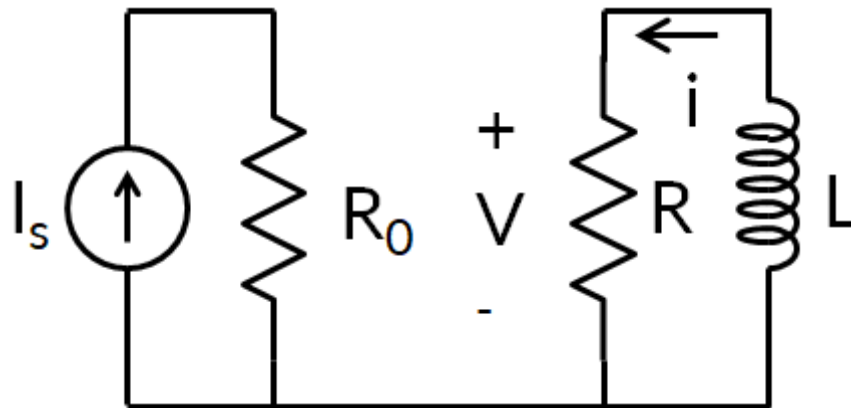- For $t \leq 0$, $i(t) = I_0$
- For $t \geq 0$, the circuit reduce to



- Note:
 - 0^- : is used to denote the time just prior to switching.
 - 0^+ is used to denote the time immediately after switching.

Discharge current through an Inductor

➤ Applying KVL to the circuit:

$$➤ \quad v(t) + Ri(t) = 0 \quad \rightarrow \quad L \frac{di(t)}{dt} + Ri(t) = 0$$

$$➤ \quad L \frac{di(t)}{dt} = -Ri(t) \quad \rightarrow \quad \frac{di(t)}{i(t)} = -\frac{R}{L} dt$$

➤ Thus, the current is given by

$$\ln \frac{i(t)}{i(0)} = -\frac{R}{L} t$$

Discharge Current through an Inductor

- Finally, the discharge current through the inductor (de-energizing the inductor through a current) is given by

$$i(t) = i(0)e^{-\frac{R}{L}t} = I_0 e^{-\frac{R}{L}t}$$


- The voltage $v(t)$ across the resistor R is given by

$$v(t) = i(t)R = I_0 R e^{-\left(\frac{R}{L}\right)t}$$


- Time constant τ is given by

$$\tau = \frac{L}{R}$$

Discharge through Inductor

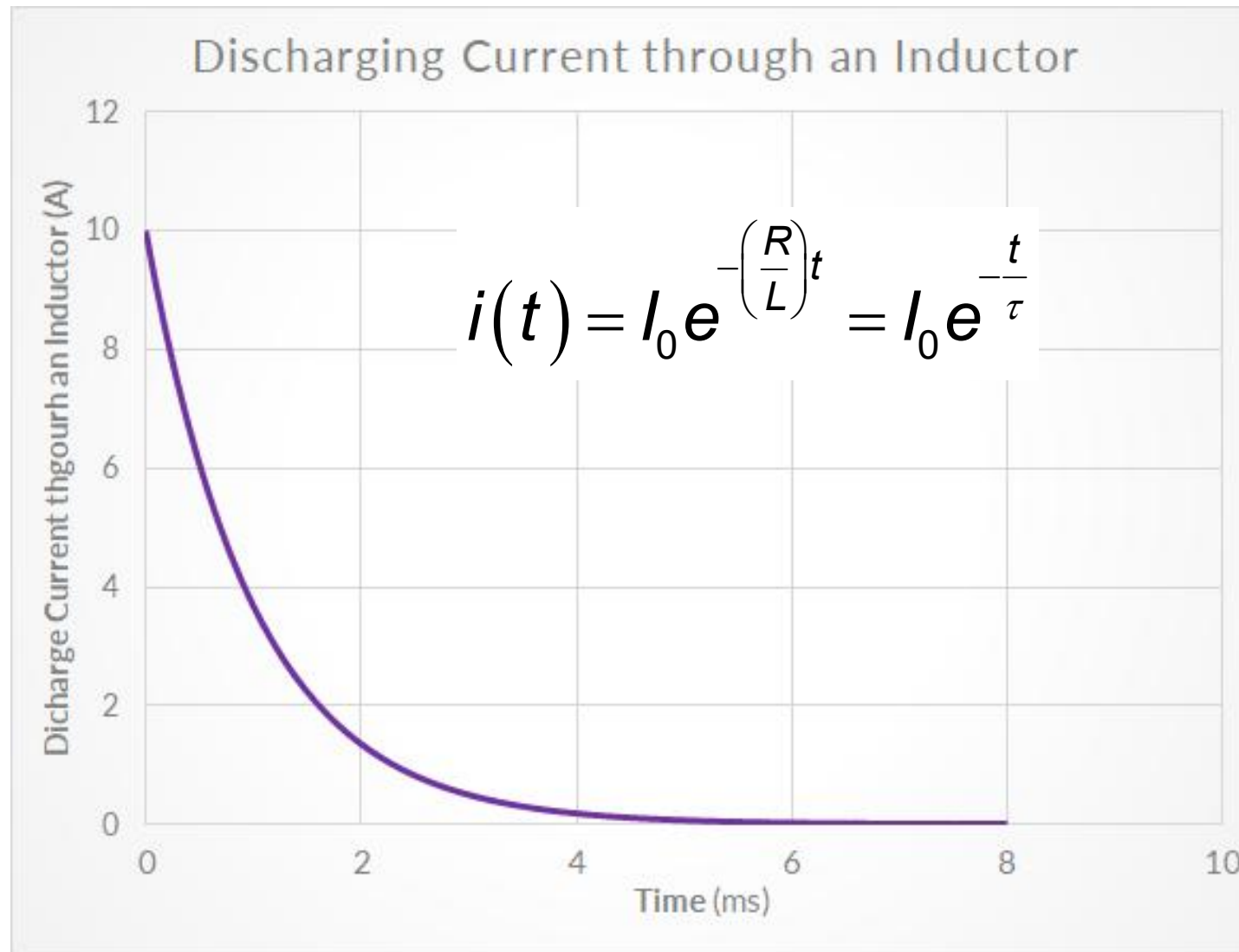

Charging Current through an Inductor

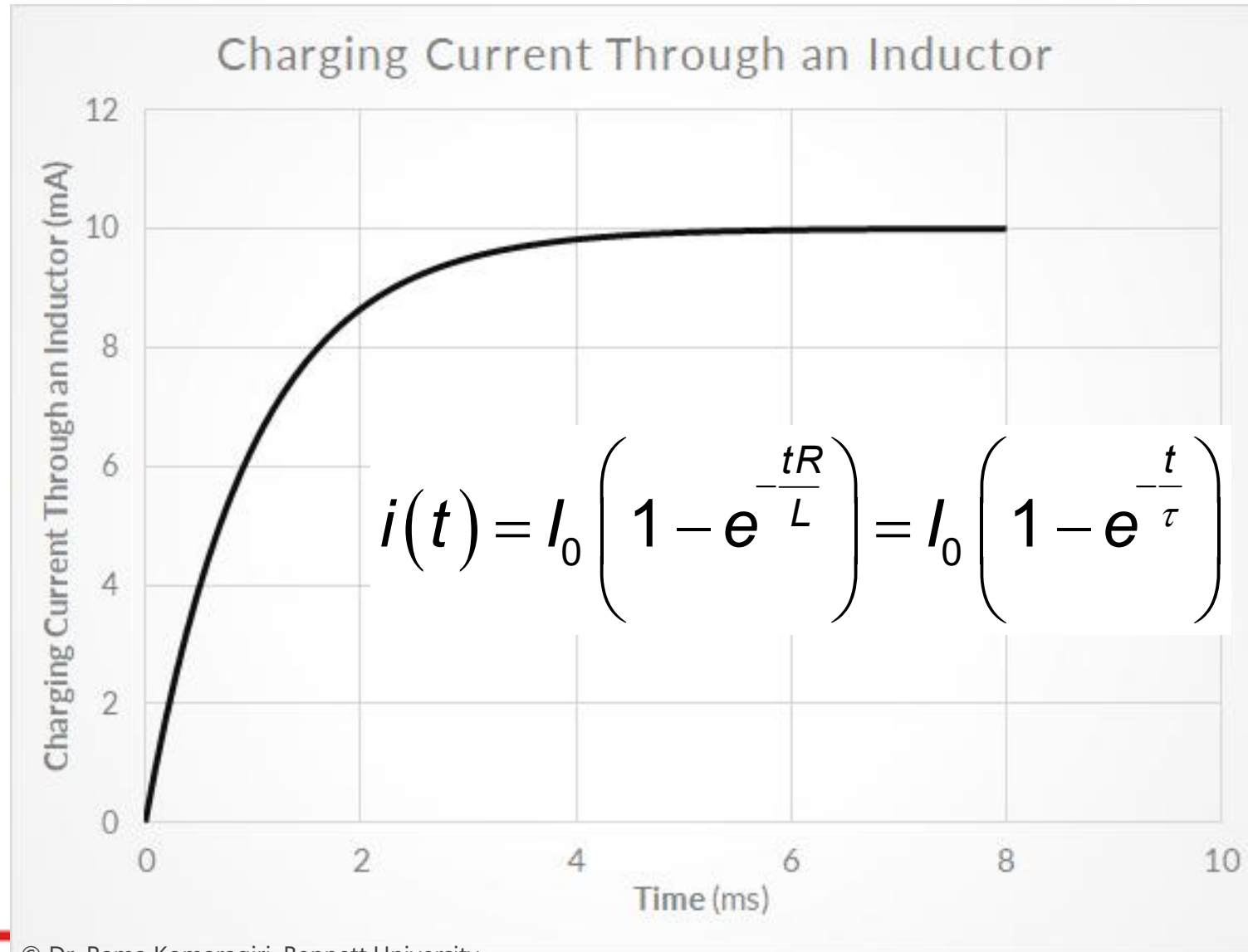

Summary

- Inductor is a energy storage device
- Inductors store energy in a magnetic field
- An ideal inductor acts like a short circuit at low frequencies and open circuit at higher frequencies
- Reluctance of an inductor increases as frequency increases
- In an inductor, voltage leads current by a phase $\pi/2$ (or current lags voltage by a phase $\pi/2$)
- The current through an inductor must be continuous; the voltage across an inductor can be discontinuous.

Summary

- › Inductors store energy in a magnetic field
- › An ideal inductor acts like a short circuit at low frequencies and open circuit at higher frequencies
- › Reluctance of an inductor increases as frequency increases
- › The current through an inductor must be continuous; the voltage across an inductor can be discontinuous.
- › The equation for equivalent inductance for


inductors in series

$$L_{eq} = \sum_{s=1}^m L_s$$

inductors in parallel


$$L_{eq} = \left[\sum_{p=1}^n \frac{1}{L_p} \right]^{-1}$$

Impedance Calculation

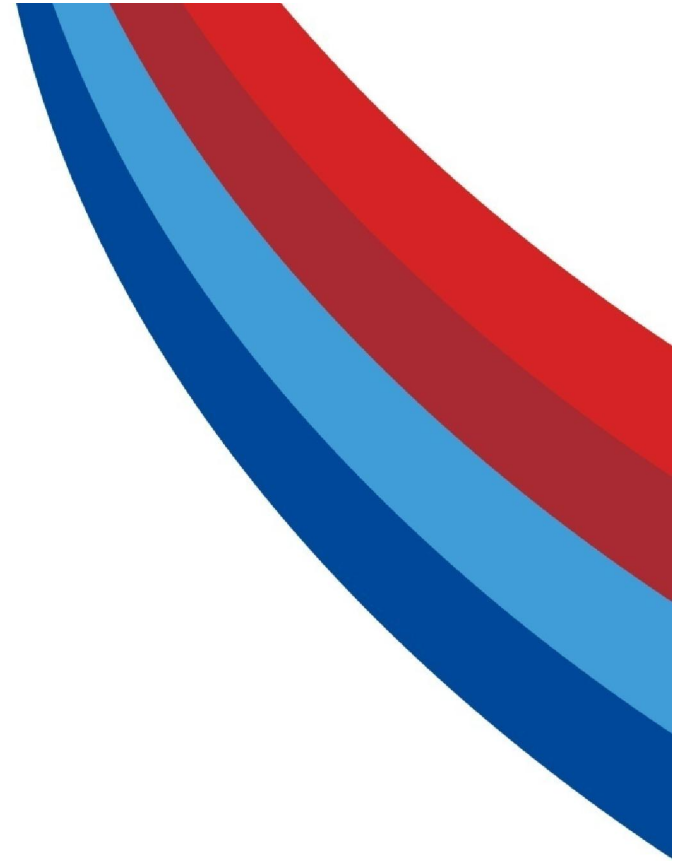

Example 1

- Calculate impedance of the following circuit at a frequency of 50 Hz.
- At 50Hz, the angular frequency $\omega = 2\pi f = 2 \times \pi \times 50 = 314 \text{ rad/s}$
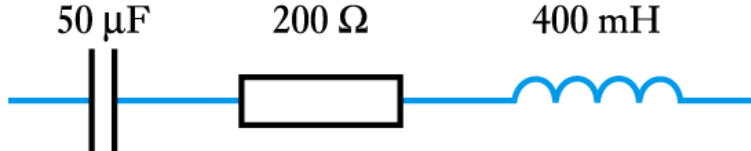
$$Z_c = -jX_c = \frac{1}{j\omega C} = \frac{1}{j314 \times 50 \times 10^{-6} \text{ F}} = -j63.7 \Omega$$


$$Z_L = jX_L = j\omega L = j314 \times 400 \times 10^{-3} = j125.6 \Omega$$

- The capacitor, resistor and inductor are in series,

$$\mathbf{Z} = \mathbf{Z}_C + \mathbf{Z}_R + \mathbf{Z}_L = R + j(X_L - X_C) = R + j\left(\omega L - \frac{1}{\omega C}\right)$$

$$\mathbf{Z} = 200 + j\left(314 \times 400 \times 10^{-3} - \frac{1}{314 \times 50 \times 10^{-6}}\right) = (200 + j62) \Omega$$

Example 2

➤ Calculate the current i through the circuit.

➤ **Solution:** $i = \frac{V}{Z}$

➤ $\omega = 250 \text{ rad/sec}$

$$Z = R - jX_C = R - j\frac{1}{\omega C}$$

$$Z = 100 - j\frac{1}{250 \times 10^{-4}} = 100 - j40 \Omega$$

$$|Z| = \sqrt{100^2 + 40^2} = 107.7 \Omega$$

$$\angle Z = \tan^{-1} \frac{-40}{100} = -21.8^\circ$$

$$Z = 107.7 \angle -21.8^\circ$$

$$i = \frac{V}{Z} = \frac{100 \angle 0}{107.7 \angle -21.8} = 0.93 \angle 21.8^\circ$$

