

Department of ECE, Bennett University

EECE105L: Fundamentals of Electrical and Electronics Engineering

Tutorial Sheet-14

Topics Covered: Applications of Diodes

If not mentioned, assume non-ideality factor ( $\eta$ ) as 1.5, reverse saturation current  $I_0$  as 5 nA, built-in the voltage of the diode is 0.6 V

Half wave rectification:

1. Assume a sinusoidal waveform with an amplitude of 10 V and 60 Hz is applied to the circuit shown in fig. 1. Draw the output waveform across the resistor and diode by assuming the diode is (i) ideal (ii) non-ideal.

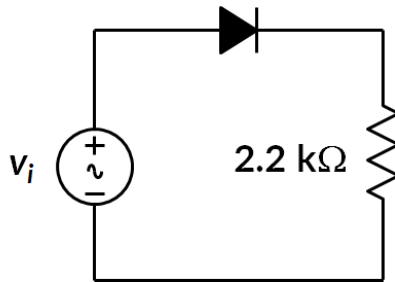


Fig. 1

2. Assume a sinusoidal waveform with an amplitude of 10 V and 60 Hz is applied to the circuit shown in fig. 2. Draw the output waveform across the resistor and diode by assuming the diode is (i) ideal (ii) non-ideal.

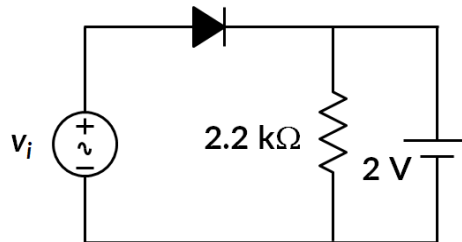


Fig. 2

Full wave rectification:

3. A full-wave bridge rectifier with a 120 V RMS sinusoidal input has a load resistance of 1 kΩ. Answer the following:
  - i) What is the voltage available across the load?
  - ii) What is the peak inverse voltage of each diode?
  - iii) When the diodes are conducting, what is the maximum current through each diode?

- iv) What should be the minimum power rating of the diode?
4. A full-wave bridge rectifier with a 200 V peak-to-peak input has a load resistance of 3.3 k $\Omega$ . Draw the output voltage waveform as seen across the load.

### Clippers and Clampers

5. For the inputs shown in the circuit shown in Fig. 3 and Fig. 4, draw the output voltage across the load resistor  $R_L$ .

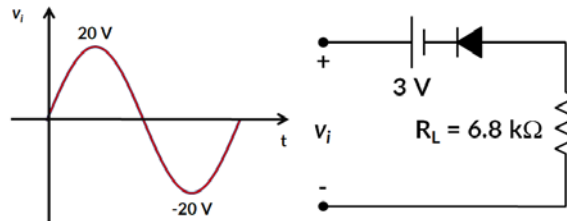


Fig. 3

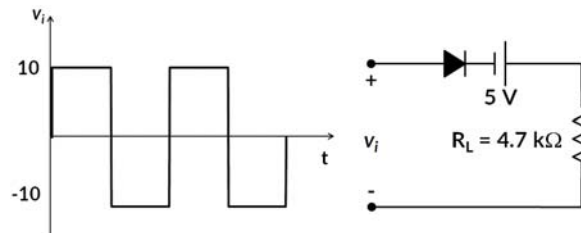


Fig. 4

6. Consider the circuit shown in fig. 5. Determine the current through the resistor and voltage across the diode. Assume that the cut-in voltage of the diode is 0.6 V.

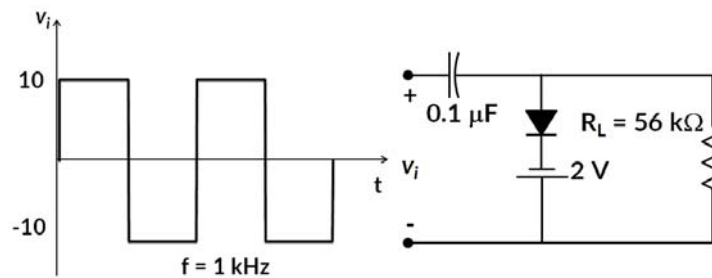


Fig. 5

Answers: will be discussed in tutorial sessions

----- END OF QUESTIONS -----