

# Nodal Analysis and Mesh Analysis

Dr. Rama Komaragiri

# Nodal Analysis and Mesh Analysis


- Two powerful methods used to analyse a given circuit
- Based on systematic application of Kirchhoff's laws
- Can be used to automate circuit analysis
- Applications
  - Design of large circuits (Integrated Circuits (ICs) or chips)
  - Board design

# Nodal Analysis

- A voltage is always defined as the potential difference between two points.
- The voltage at a certain point of a circuit means that the voltage is measured between the point under consideration and some other point in the circuit.
- In most cases that reference point is referred to as ground.
- The node method or the node voltage method or nodal analysis, is a very powerful approach for circuit analysis
- Nodal analysis based on the application of KCL, KVL and Ohm's law.


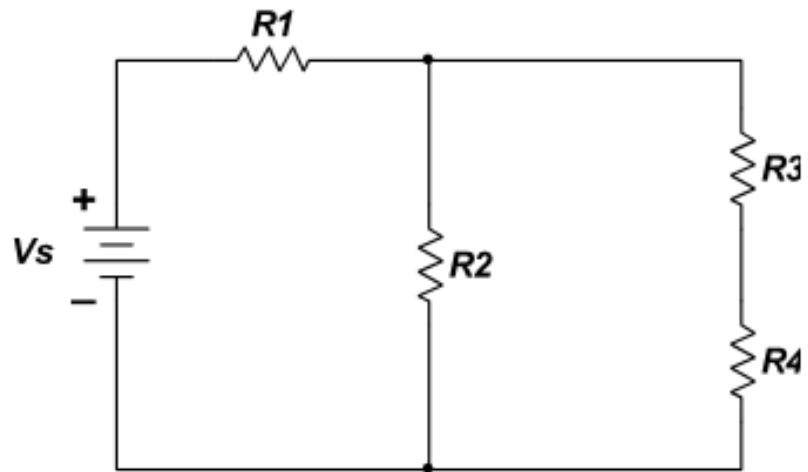
# Nodal Analysis

- Consider a typical circuit shown in the figure
- The procedure for analyzing a circuit with the node method is based on the few steps.




# Nodal Analysis

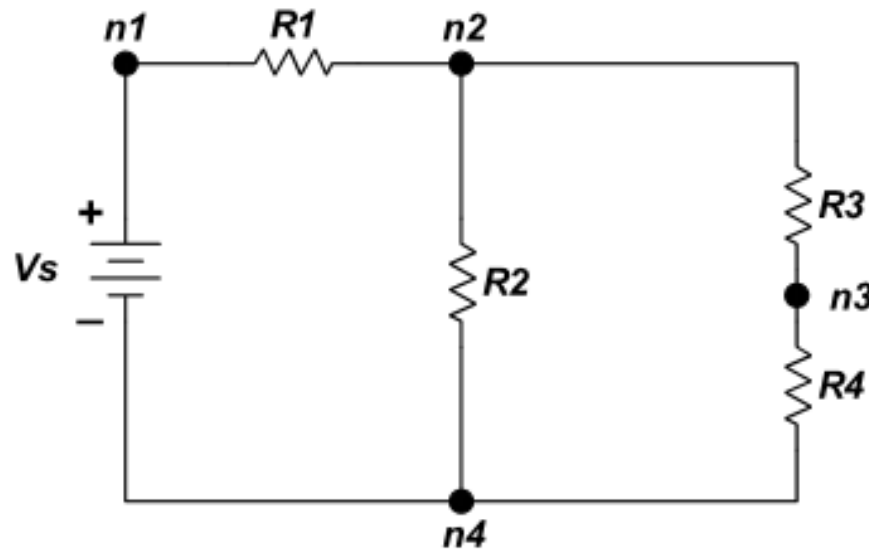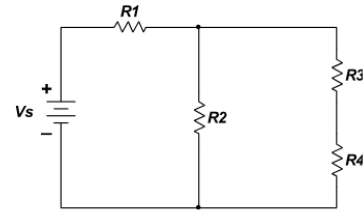- 1) Label all circuit parameters and separately list the unknown parameters and the known.
- 2) Identify all nodes of the circuit.



# Nodal Analysis

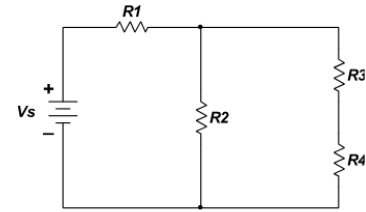

3) Select a node as the reference node.


- a) This reference node is called as the ground
- b) Assign a potential of 0 Volts to the ground
- c) All other voltages in the circuit are measured with respect to the reference node (ground node).

How to select a reference node:

A useful reference node makes the problem easier to understand and solve.



General guidelines to select the reference node.

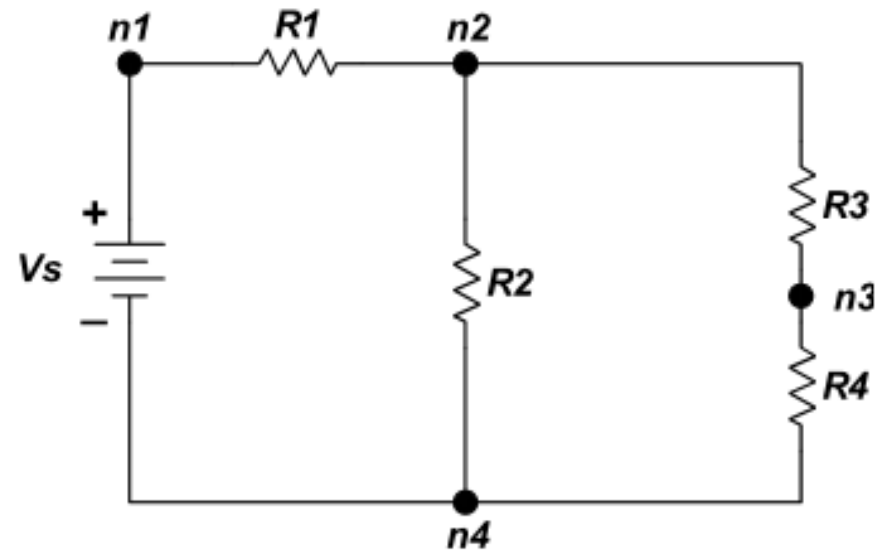- 1. Largest number of elements connected to it.
- 2. One which is connected to the maximum number of voltage sources.






# Nodal Analysis

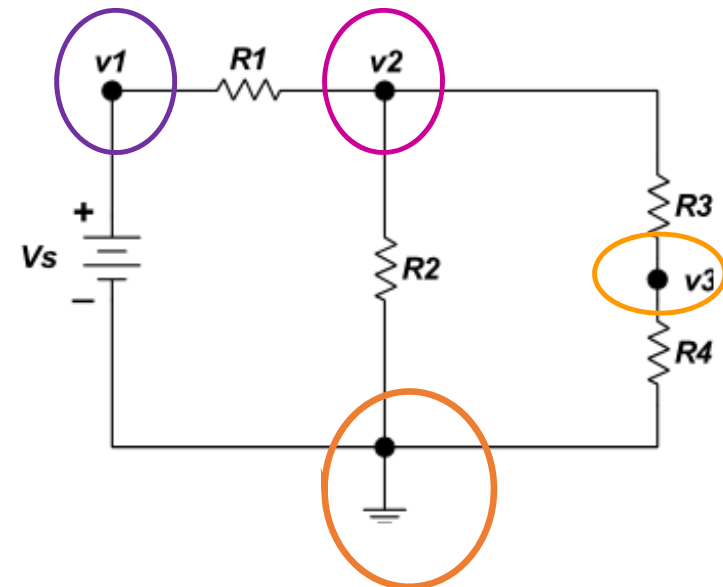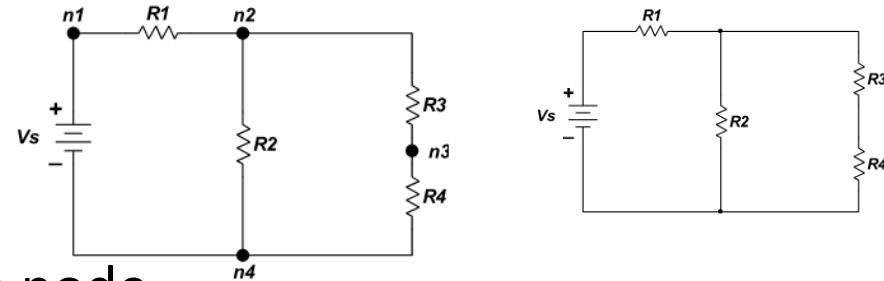- 4) For the circuit shown, ***n4*** is the reference node
- 5) The reference node is assigned voltage 0 V indicated by ground symbol.
- 6) Label the voltages at all other nodes (node voltages are labelled ***v1***, ***v2***, ***v3***).




Node  $n4$  is replaced with ground symbol

# Nodal Analysis

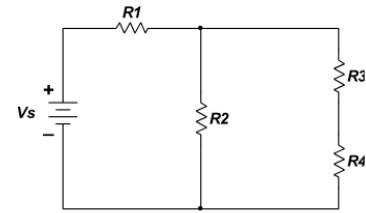
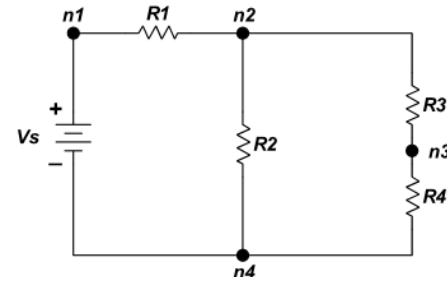
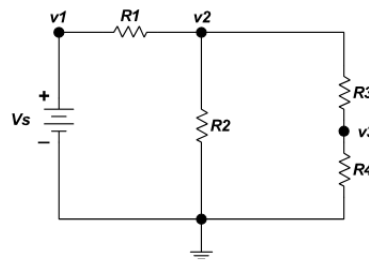


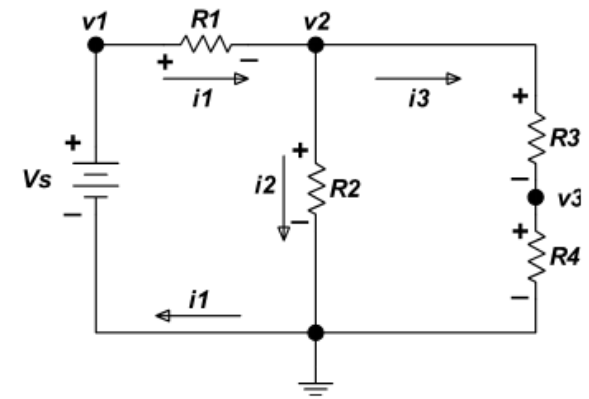7) Assign polarities and current direction






# Nodal Analysis

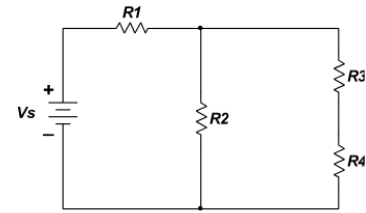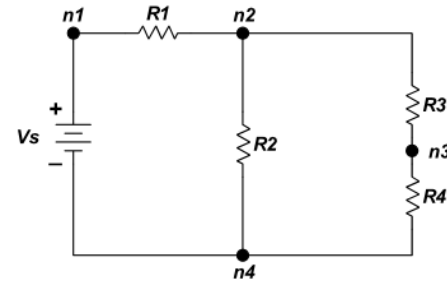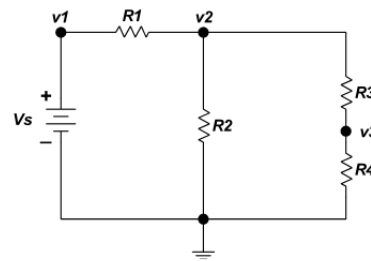

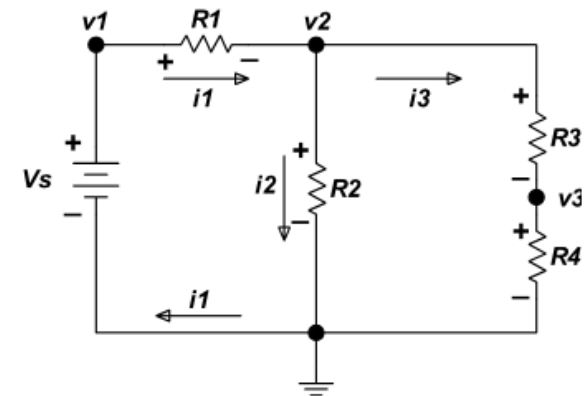7) Assign polarities and current direction



# Nodal Analysis

8) Apply KCL at each node and express the branch currents in terms of the node voltages.

a) At node ***n1***,  $v_1 = V_s$ .

b) KCL at node ***n2*** associated with voltage  $v_2$  results in




$$i_1 = i_2 + i_3$$

c) Currents  $i_1$ ,  $i_2$  and  $i_3$  can be expressed in terms of voltages  $v_1$ ,  $v_2$  and  $v_3$  as

$$i_1 = \frac{V_s - v_2}{R_1}$$

$$i_2 = \frac{v_2}{R_2}$$

$$i_3 = \frac{v_2 - v_3}{R_3}$$

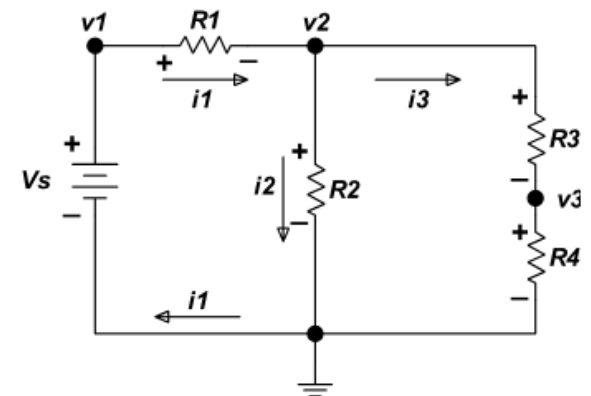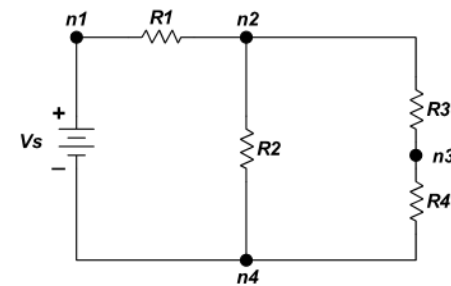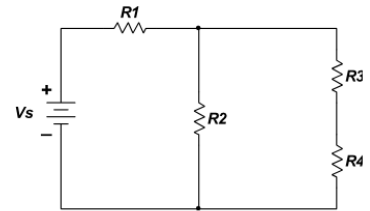

# Nodal Analysis

d) By combining the above equations from 8(b) and 8(c)

$$\frac{V_s - v_2}{R_1} - \frac{v_2}{R_2} - \frac{v_2 - v_3}{R_3} = 0$$

e) Re-writing the above equation as a linear function of unknown voltages  $v_2$  and  $v_3$  results in

$$v_2 \left( \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right) - v_3 \frac{1}{R_3} = V_s \frac{1}{R_1}$$

f) KCL at node  $n_3$  (voltage  $v_3$ ) results in

$$\frac{v_2 - v_3}{R_3} - \frac{v_3}{R_4} = 0 \Rightarrow -v_2 \frac{1}{R_3} + v_3 \left( \frac{1}{R_3} + \frac{1}{R_4} \right) = 0$$

# Nodal Analysis


g) Next step is write them in the form of a matrix (this example might be easy to solve without writing matrix).

$$v_2 \left( \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right) - v_3 \frac{1}{R_3} = V_s \frac{1}{R_1}$$

$$-v_2 \frac{1}{R_3} + v_3 \left( \frac{1}{R_3} + \frac{1}{R_4} \right) = 0$$

$$\begin{bmatrix} \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} & -\frac{1}{R_3} \\ -\frac{1}{R_3} & \frac{1}{R_3} + \frac{1}{R_4} \end{bmatrix} \begin{bmatrix} v_2 \\ v_3 \end{bmatrix} = \begin{bmatrix} V_s \\ 0 \end{bmatrix}$$

# Nodal Analysis

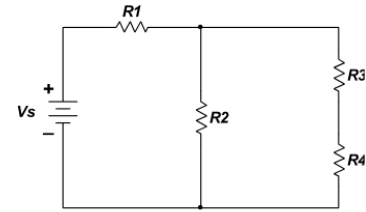


- 9) Solve the resulting simultaneous equations for the node voltages.
- 10) Once the node voltages are known, the branch currents are obtained by using Ohm's law.


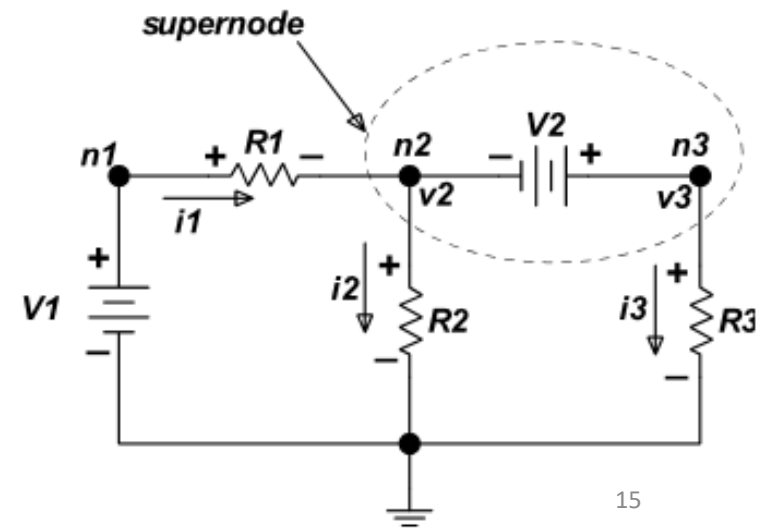
# Nodal analysis with floating voltage sources

- A voltage source which is not connected to the reference node is called as a floating voltage source
    - Special care must be taken while analyzing the circuit
  - The voltage source  $V_2$  is not connected to the reference node and thus it is a **floating voltage source**.
- 
- ❖ Part of the circuit enclosed by the dotted ellipse is called a supernode.
  - ❖ KCL is applicable at supernode.
  - ❖ Supernode introduces an extra constraint.



# Nodal analysis with floating voltage sources

- Applying KCL at supernode results in


$$i_1 = i_2 + i_3$$

- Writing in terms of node voltages,

$$\frac{V_1 - v_2}{R_1} = \frac{v_2}{R_2} + \frac{v_3}{R_3}$$

- The relation between node voltages  $n_2$  and  $n_3$  is needed to completely define the problem
- The constraint is

$$V_2 = v_3 - v_2$$

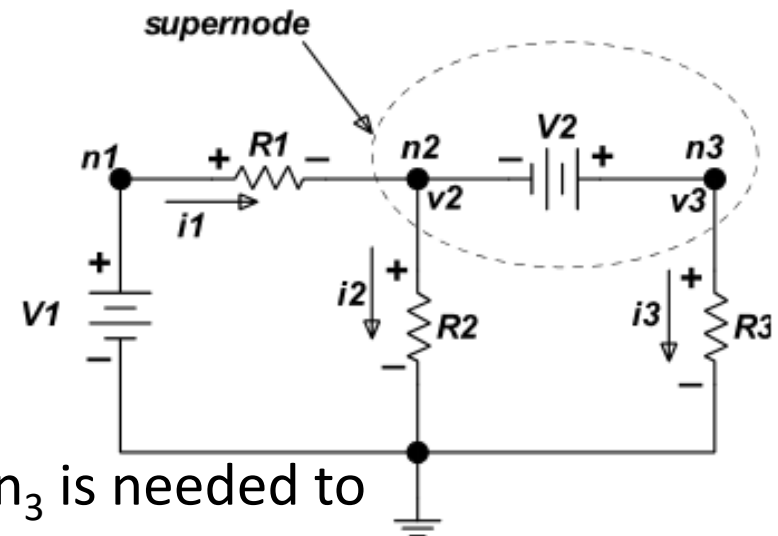



# Nodal analysis with floating voltage sources

- Combining the equations results in


$$v_2 = \frac{\frac{V_1}{R_1} - \frac{V_2}{R_3}}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}}$$

$$v_3 = \frac{\frac{V_1}{R_1} - \frac{V_2}{R_3}}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}} - V_2$$

# Nodal Analysis: Circuit with voltage and current source

- After initial steps of the nodal method, apply KCL to the designated nodes.
- The current source  $I_s$  constraints the current  $i_3$  such that  $i_3 = I_s$
- At node **n1**,  $V_s = v_1$ .
- KCL at node **n2** results in

$$i_1 = i_2 + i_3 = i_2 + I_s$$

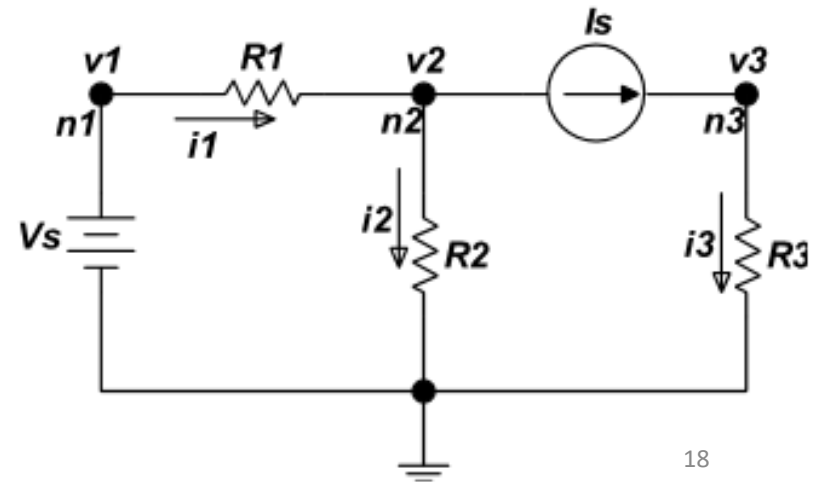

# Nodal Analysis: Circuit with voltage and current source

- Applying Ohm's law results in


$$\frac{V_s - v_2}{R_1} = \frac{v_2}{R_2} + \frac{v_3}{R_3}$$

- The current source results in a constraint given by

$$v_3 = I_s R_3$$


- Combining above results yields in
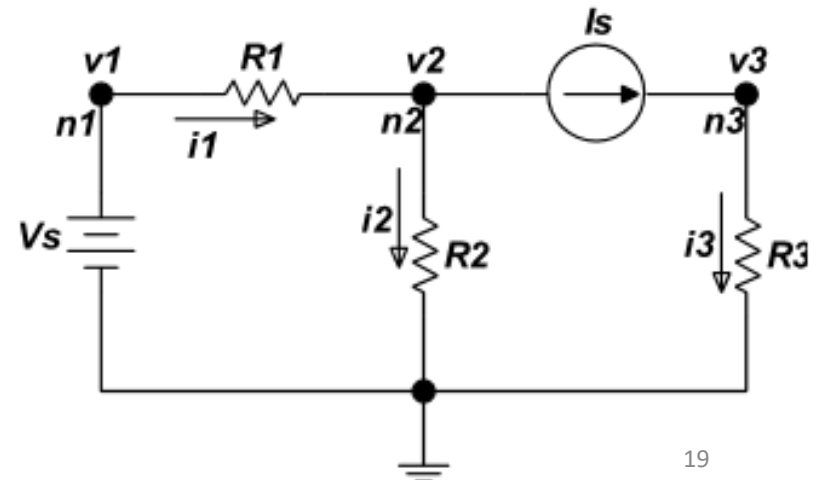
$$v_2 = \frac{\frac{V_s}{R_1} - I_s R_3}{\frac{1}{R_1} + \frac{1}{R_2}}$$



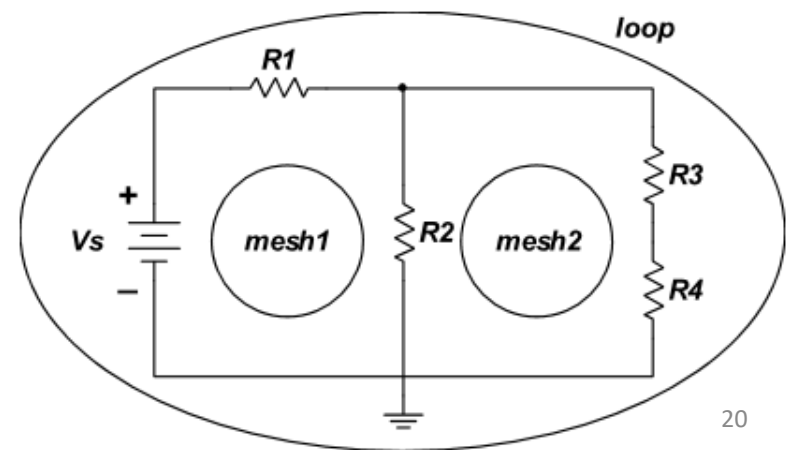
# The Mesh Method

- Mesh method uses mesh currents as the circuit variables
- Method is similar to Nodal analysis
- Primarily KVL is used
- A mesh is defined as a loop which does not contain any other loops




# The Mesh Method

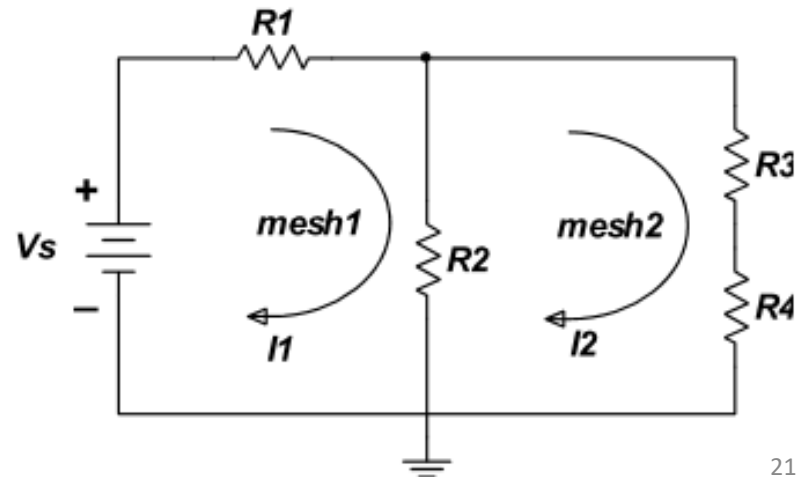- 1) Label all circuit parameters and separately list the unknown parameters and the known.
  - 2) Identify all nodes of the circuit.
  - 3) Assign mesh currents and label polarities.
- The direction of the mesh currents  $I_1$  and  $I_2$  is taken in clockwise direction
  - Definition for the current direction is arbitrary
  - Helps if consistency is maintained in defining these current directions (easy to debug).


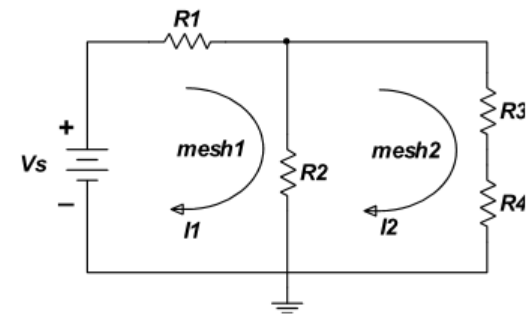
# The Mesh Method

- In certain parts of the mesh, the branch current and mesh current can be same.
- The branch of the circuit containing resistor  $R_2$  is shared by the two meshes and thus the branch current
  - The current flowing through  $R_2$  is the difference of the two mesh currents.
  - Mesh current are indicated by using the symbol  $I$  and the symbol  $i$  is used to indicate the branch currents.



$$I_2(R_3 + R_4) + (I_2 - I_1)R_2 = 0$$

# The Mesh Method

4) Apply KVL at each mesh and express the voltages in terms of the mesh currents.



- Consider mesh 1
- Care must be taken to carry all the information of the shared branches.
- The direction of mesh current  $I_2$  on the shared branch is from mesh 2.
- Applying KVL to mesh 1

$$I_1 R_1 + (I_1 - I_2) R_2 - V_s = 0$$

e) Considering mesh 2

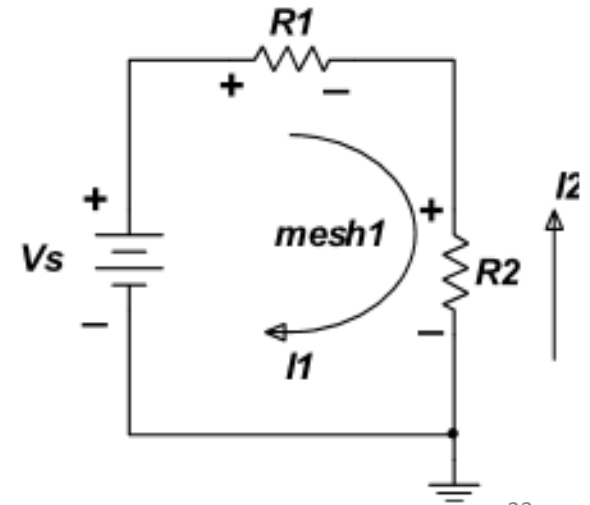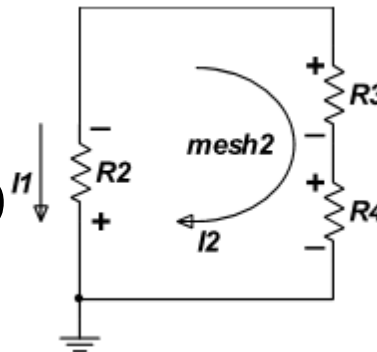f) Apply KVL

$$I_2 (R_3 + R_4) + (I_2 - I_1) R_2 = 0$$



# The Mesh Method

5) Solve the resulting simultaneous equations for the mesh currents.

$$\begin{aligned}I_1(R_1 + R_2) - I_2R_2 &= V_s \\ -I_1R_2 + I_2(R_2 + R_3 + R_4) &= 0\end{aligned}$$

a) Writing the equations in matrix for

$$\begin{bmatrix} R_1 + R_2 & -R_2 \\ -R_2 & R_2 + R_3 + R_4 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} V_s \\ 0 \end{bmatrix}$$




# The Mesh Method

- 7) As the mesh currents are known, the voltages may be obtained from Ohm's law.
- 8) The branch currents can be found as

$$i_1 = I_1$$


$$i_2 = I_1 - I_2$$

$$i_3 = I_2$$

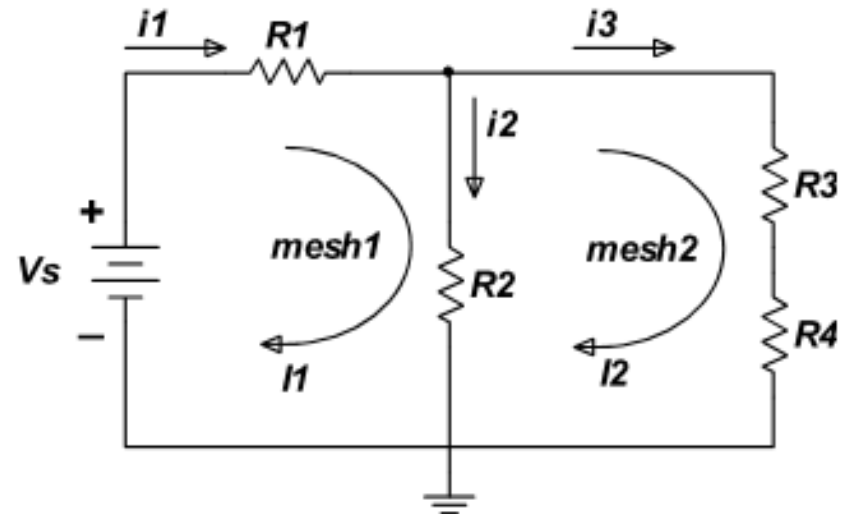
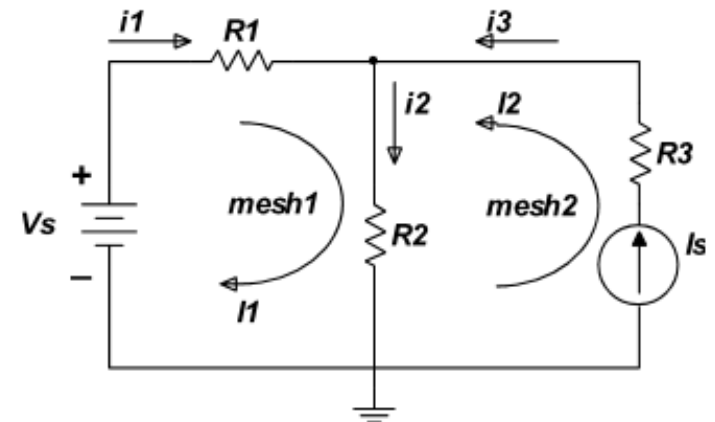
# The Mesh Method: With Current Sources

- The mesh current of the mesh containing the current source is equal to the current of the current source: i.e.  $I_2 = I_s$
- In defining the direction of the mesh current use the direction of the current as defined by the current source (direction that of  $I_s$ ).
- In this example, the branch current  $i_3 = I_s$ .



# The Mesh Method: With Current Sources

- Applying KVL around mesh1

$$I_1 R_1 + (I_1 + I_s) R_2 = V_s$$

- Solving for  $I_1$ ,

$$I_1 = \frac{V_s - I_s R_2}{R_1 + R_2}$$

