

Department of ECE, Bennett University

EECE105L: Fundamentals of Electrical and Electronics Engineering

Tutorial Sheet-7

**Topics Covered:** Superposition Theorem (Principle of Superposition)

- Using superposition theorem, find the current flowing through  $12\ \Omega$  resistance in fig. 1.

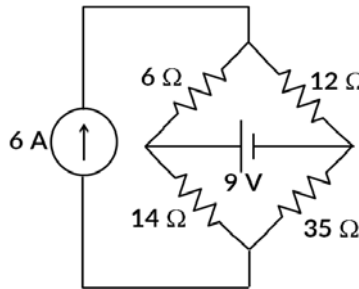


Fig. 1

- Using superposition principle (superposition theorem), in the circuit shown in fig. 2, find the current flowing through  $2\ \Omega$  resistance.

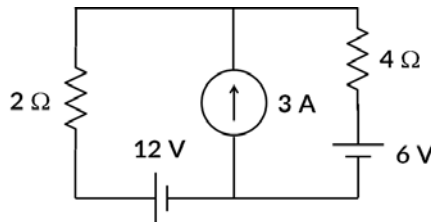


Fig. 2

- Using superposition theorem, for the circuit shown in fig. 3, determine the voltage across the  $4.7\ \Omega$  resistor and power delivered to the resistor. Find the power delivered to  $4.7\ \Omega$  resistor solely by voltage source and solely by current source. What are your observations and reasons for discrepancies if any.

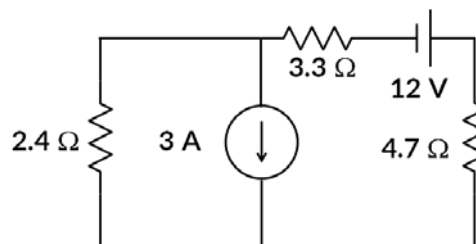


Fig. 3

- Using superposition theorem, find the current through  $56\ \Omega$  resistor for the circuit in fig. 4.

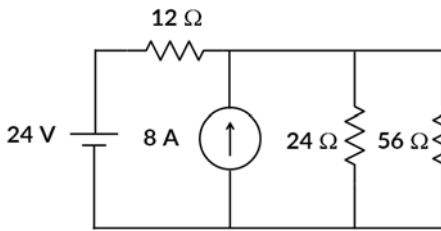


Fig. 4

5. Using superposition theorem, for the 24 V source shown in fig. 5, find the current through and power consumed or delivered by the 24 V source.

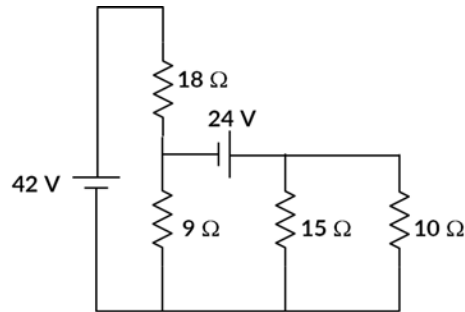


Fig. 5

6. Find the voltage across 6 A source shown in fig. 6.

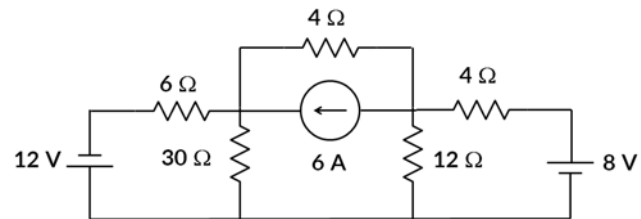


Fig. 6

7. For the circuit shown in fig. 7, using superposition theorem, find the power consumed by 6 Ω resistor.

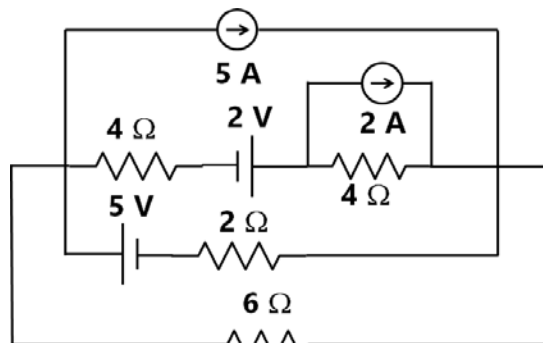


Fig. 7

8. For the circuit shown in fig. 8, using superposition theorem, find the power consumed by  $3\ \Omega$  resistor and  $1\ \Omega$  resistor.

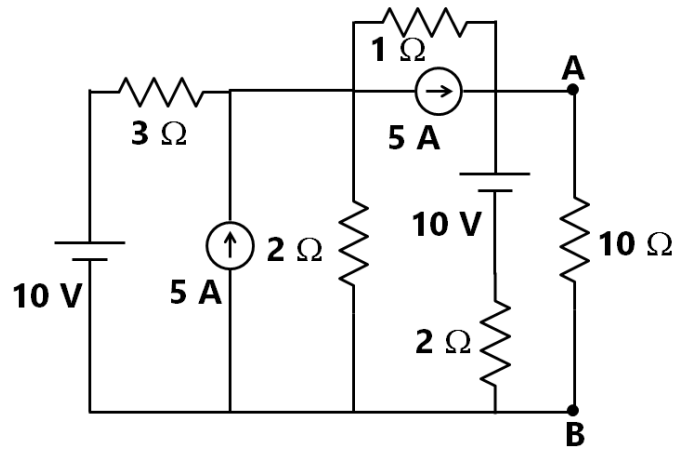


Fig. 8

9. For the circuit shown in fig. 9, using superposition theorem, find the power consumed by  $1\ \Omega$  resistor and  $20\ \Omega$  resistor.

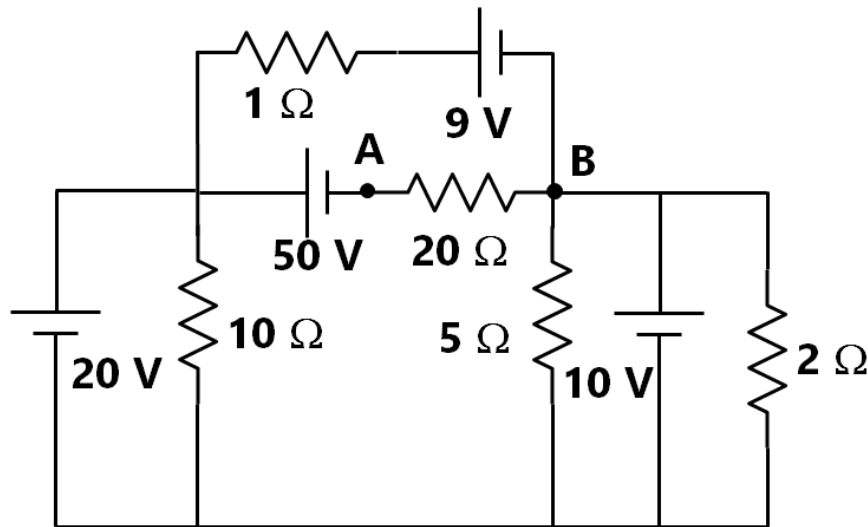


Fig. 9

----- END OF QUESTIONS -----

**Answers:**

**Superposition Theorem**

- 1)  $I(6\ \text{mA}) = 2\ \text{A}$ ,  $I(9\ \text{V}) = 0.5\ \text{A}$ ,  $I = 2.5\ \text{mA}$
- 2)  $I(3\ \text{A}) = 1\ \text{A}$ ,  $I(12\ \text{V}) = 2\ \text{A}$ ,  $I(6\ \text{V}) = -2\ \text{A}$ ,  $I = 1\ \text{A}$

- 3)  $V(3\text{ A}) = -3.25\text{ V}$ ,  $P(3\text{ A}) = 2.24\text{ W}$ ;  $V(12\text{ V}) = 5.53\text{ V}$ ,  $P(12\text{ V}) = 8.78\text{ W}$ ,  $P = 1.106\text{ W}$
- 4)  $I(24\text{ V}) = 0.25\text{ A}$ ,  $I(8\text{ A}) = 1\text{ A}$ ,  $I = 1.25\text{ A}$
- 5)  $I(42\text{ V}) = 1.17\text{ A}$ ,  $I(24\text{ V}) = 2\text{ A}$ ,  $I = 3.17\text{ A}$ ,  $P = 76.08\text{ W}$
- 6)  $V_{S1}(12\text{ V}) = -3.34\text{ V}$ ,  $V_{S2}(8\text{ V}) = -2\text{ V}$ ,  $V_{S3}(3\text{ A}) = -16\text{ V}$ ,  $V = 10.66\text{ V}$
- 7)  $I(5\text{ A}) = 1.05\text{ A}$ ,  $I(2\text{ A}) = 0.21\text{ A}$ ,  $I(2\text{ V}) = 0.042\text{ A}$ ,  $I(5\text{ V}) = -0.526\text{ A}$ ,  $I = 0.776\text{ A}$ ,  $P = 3.61\text{ W}$
- 8) For  $3\ \Omega$ :  $I(10\text{ V}) = 2.41\text{ A}$ ,  $I(10\text{ V}) = -0.864\text{ A}$ ,  $I(5\text{ A}) = -1.38\text{ A}$ ,  $I(5\text{ A}) = 0.516\text{ A}$ ,  $I_{3\Omega} = 0.682\text{ A}$ ,  
 $P_{3\Omega} = 1.4\text{ W}$   
For  $1\ \Omega$ :  $I(10\text{ V}) = 1.03\text{ A}$ ,  $I(10\text{ V}) = -2.16\text{ A}$ ,  $I(5\text{ A}) = 1.55\text{ A}$ ,  $I(5\text{ A}) = -3.71\text{ A}$ ,  $I_{1\Omega} = -3.29\text{ A}$ ,  $P_{1\Omega} = 10.82\text{ W}$
- 9) For  $20\ \Omega$ :  $I(20\text{ V}) = 1\text{ A}$ ,  $I(10\text{ V}) = -0.5\text{ A}$ ,  $I(9\text{ V}) = 0\text{ A}$ ,  $I(50\text{ V}) = -2.5\text{ A}$ ;  $I = 2\text{ A}$ ,  $I_{20\Omega} = -2\text{ A}$ ,  $P_{20\Omega} = 80\text{ W}$   
For  $1\ \Omega$ :  $I(20\text{ V}) = 20\text{ A}$ ,  $I(10\text{ V}) = -10\text{ A}$ ,  $I(9\text{ V}) = -9\text{ A}$ ,  $I(50\text{ V}) = 0\text{ A}$ ;  $I = 1\text{ A}$ ,  $I_{20\Omega} = -2\text{ A}$ ,  $P_{1\Omega} = 1\text{ W}$