




**BENNETT**  
UNIVERSITY  
A TIMES GROUP INITIATIVE

# Series and Parallel Connections


Rama Komaragiri
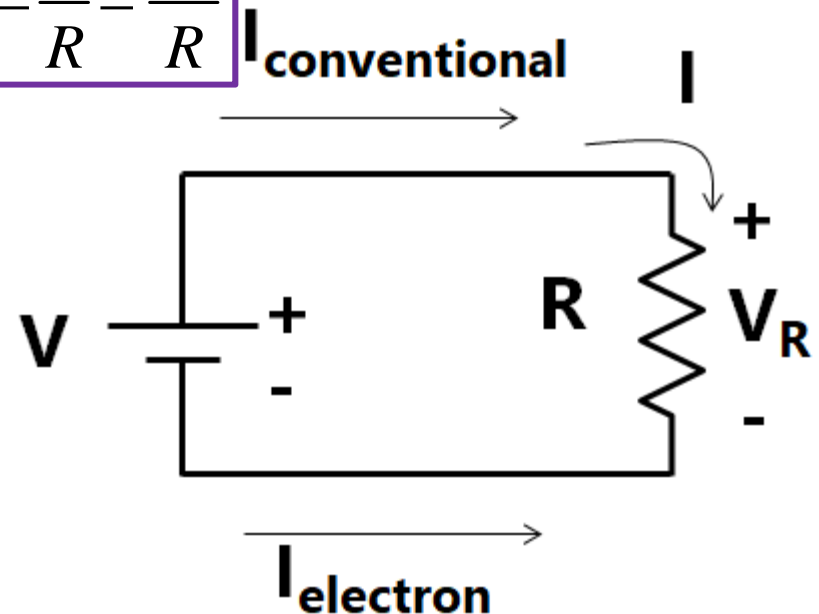
# Direction of Current Flow: Voltage Source

- If the wires is an ideal conductor (having no opposition to current flow), then the potential difference across the resistor  $R$  ( $V_R$ ) is equal to the supply voltage ( $V$ )
- By convention, the direction of conventional current flow and electron current flow are opposite
- Following the conventional current flow,  $I = \frac{V}{R} = \frac{V_R}{R}$
- a rise in the potential across the battery (- to +)
- a drop in the potential across the resistor (+ to -)




# Series Connections

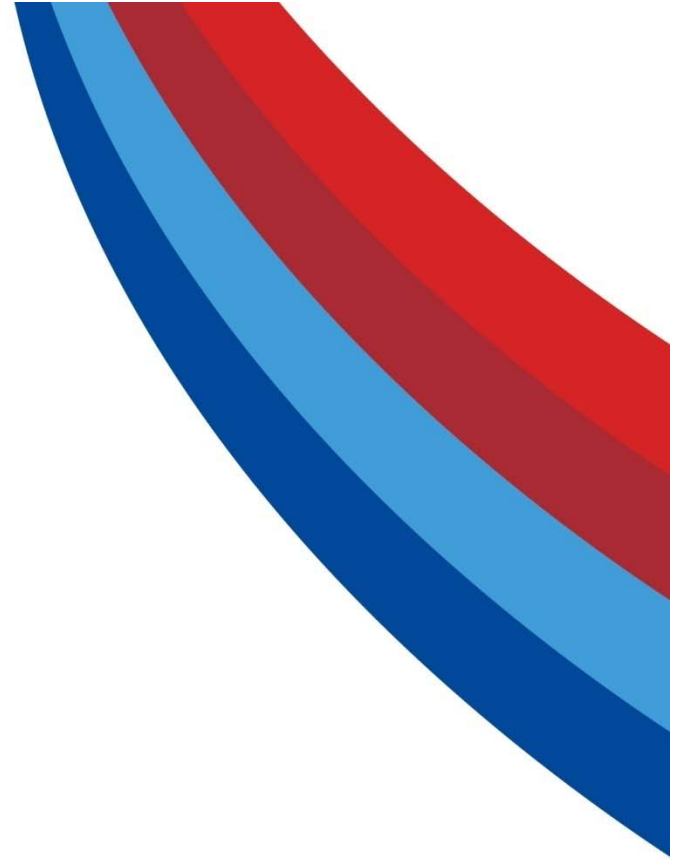



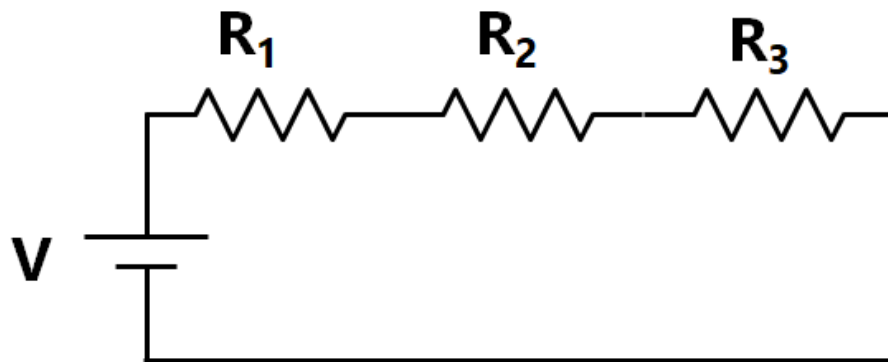
# Series Connections

- Circuit is an arrangement of components (or circuit elements) that results in a continuous flow of charge, or current, through the configuration
- Series Configuration: The current is same in the every point in the circuit



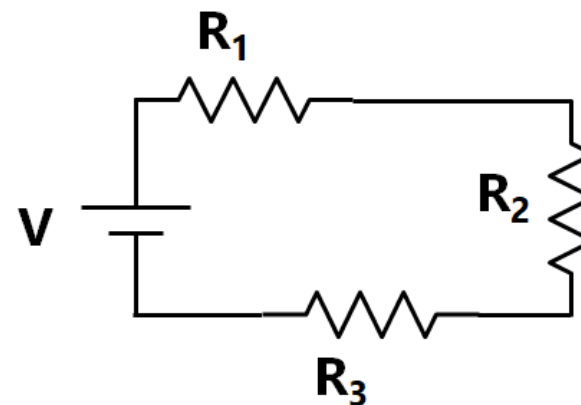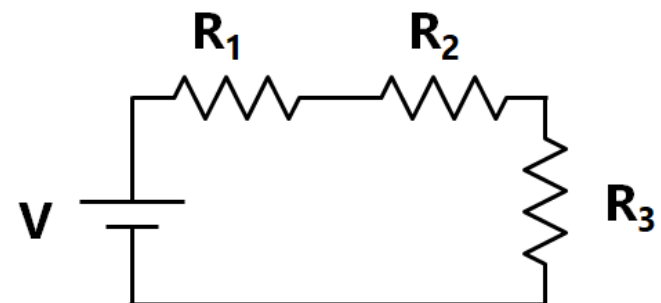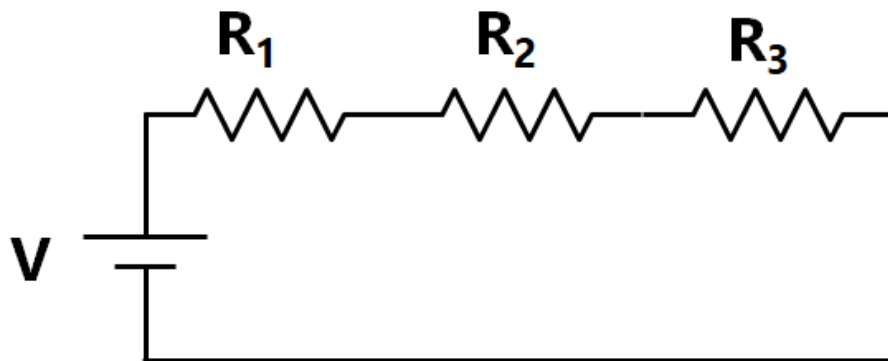
# Resistors in Connected in Series

- Series Configuration: The current is same in the every point in the circuit
  - In a circuit, if two elements are in series, the current must be same
  - If the currents are same in two adjoining circuit branches, the elements may or may not be in series


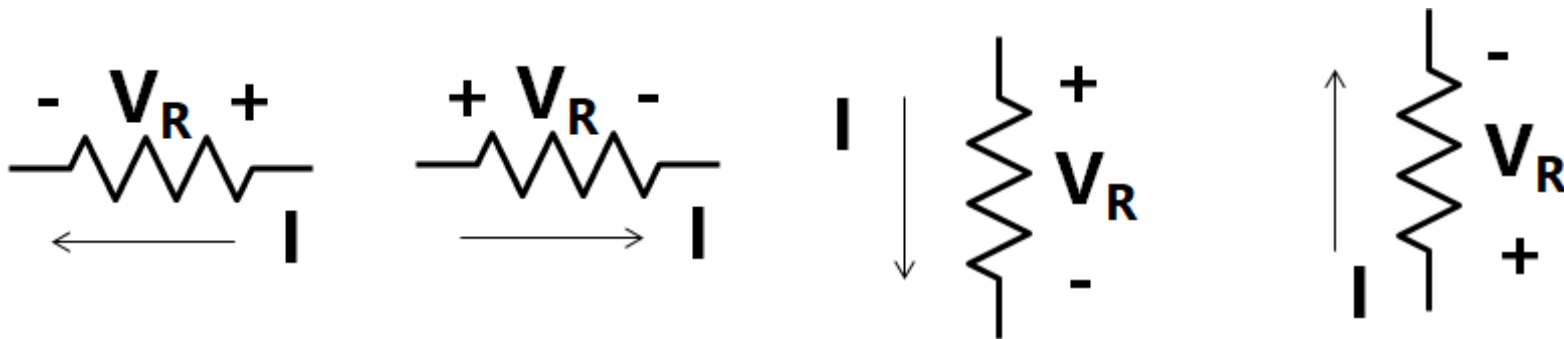
# Direction of Current in a Resistor


- The polarity of the voltage across a resistor is determined by the direction of current
- Current entering a resistor creates a voltage drop with polarity as shown



- **The sign of current flow in a resistor when current flows from positive potential to negative potential is negative**
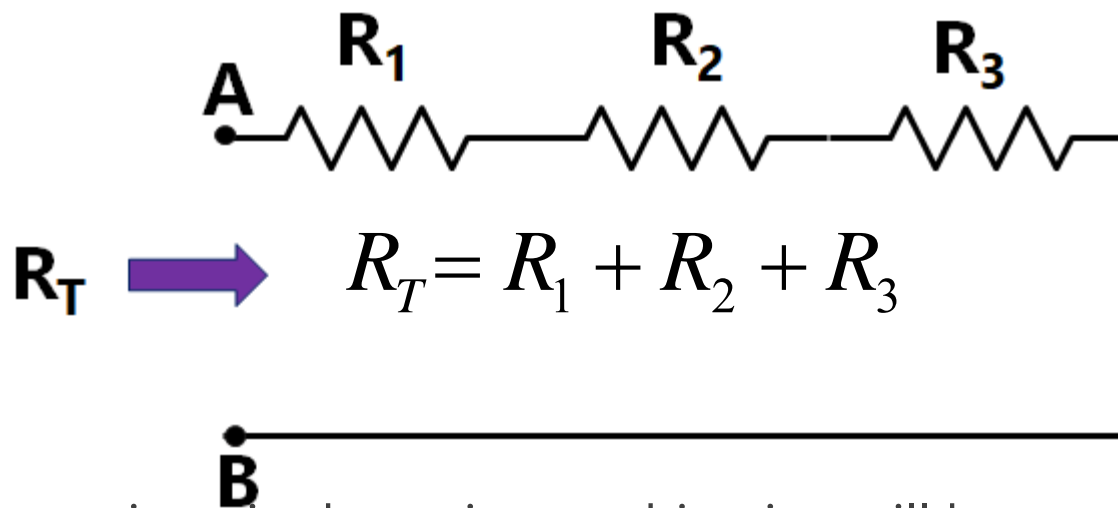
# Resistors in Connected in Series

- The total resistance of a series configuration is the sum of the individual resistances as seen between the terminals "A" and "B"





- The largest resistor in the series combination will have most impact on the total resistance
- More resistors in series combination, the greater the resistance, no matter what the value of the resistor is
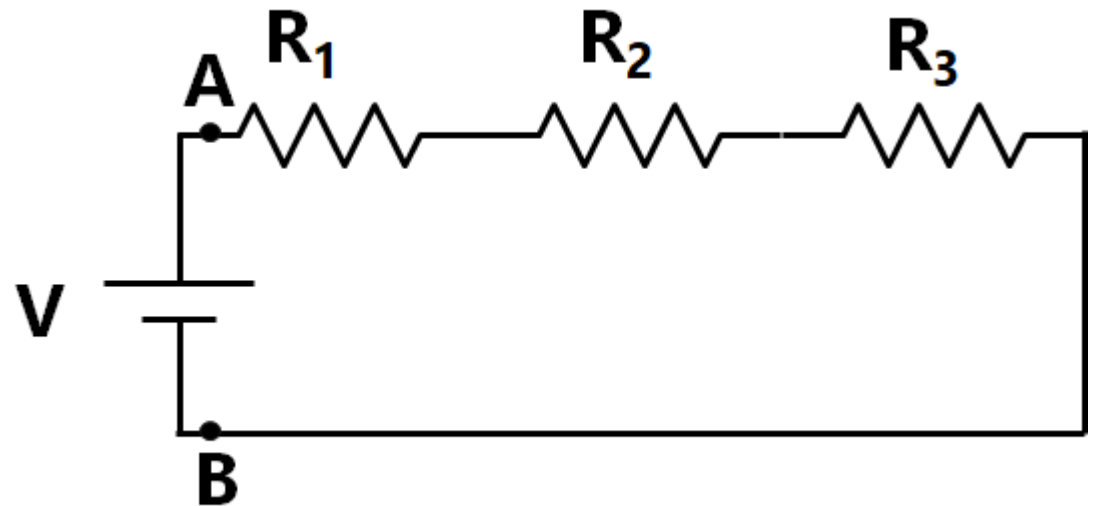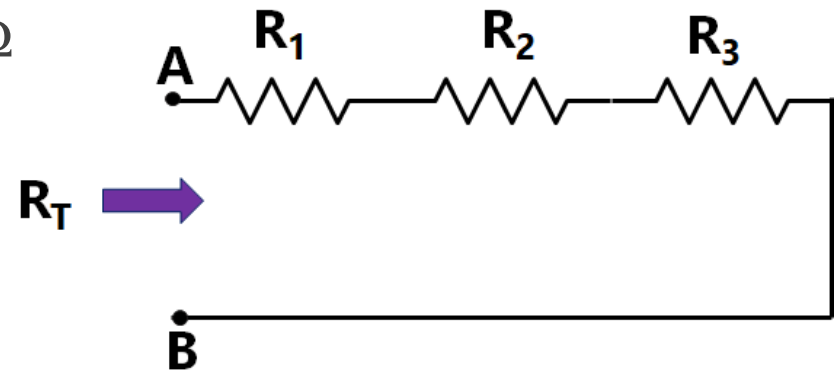
# Resistors in Connected in Series

- Let  $R_1 = 1 \text{ k}\Omega$ ,  $R_2 = 5 \text{ k}\Omega$ ,  $R_3 = 1.5 \text{ k}\Omega$
- The total resistance  $R_T = 7.5 \text{ k}\Omega$ .
- Let  $V = 15 \text{ V}$
- Current  $I$  through the circuit is


$$I = \frac{V}{R_T} = \frac{15V}{7.5k\Omega} = 2 \text{ mA}$$





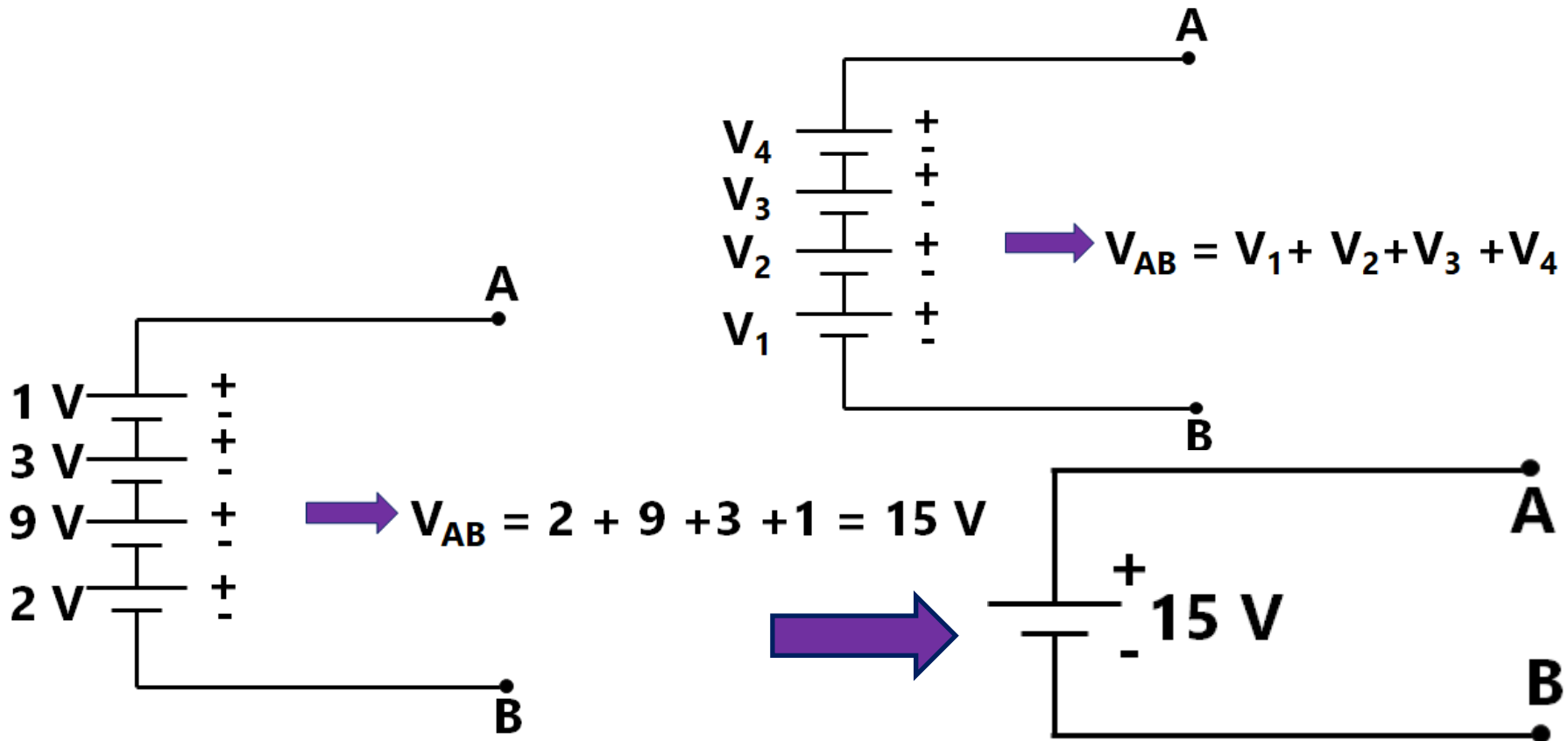
# Voltage Sources Connected in Series

- The net voltage is obtained by summing up the voltages with same polarity and subtracting voltages with opposite polarity




# Voltage Sources Connected in Series

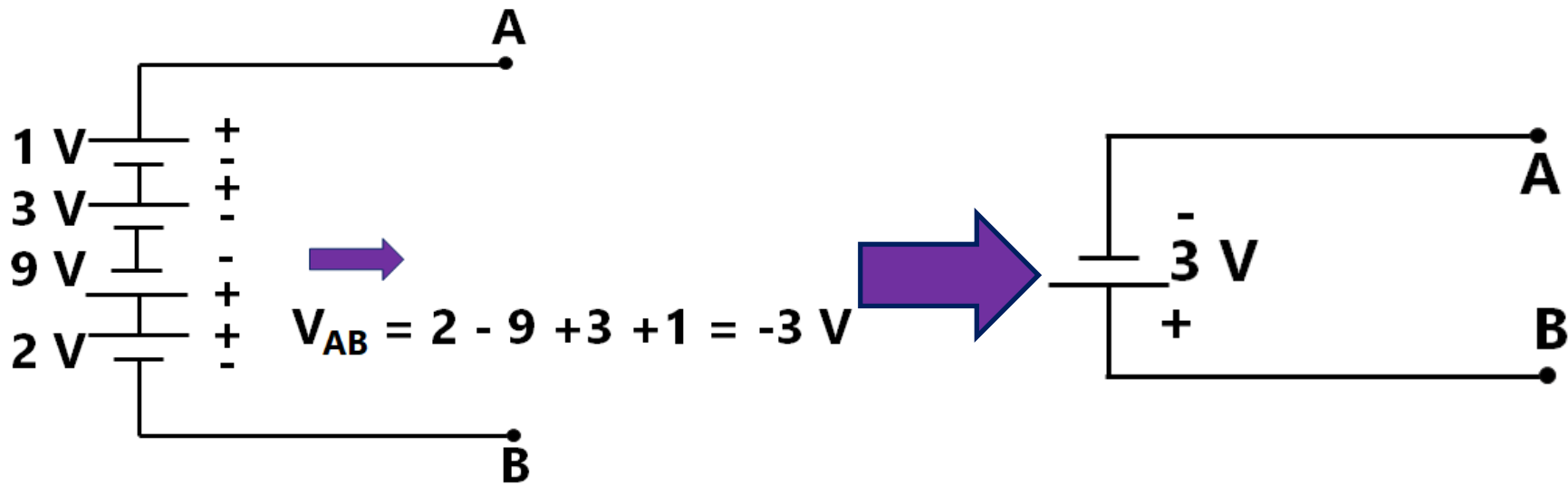
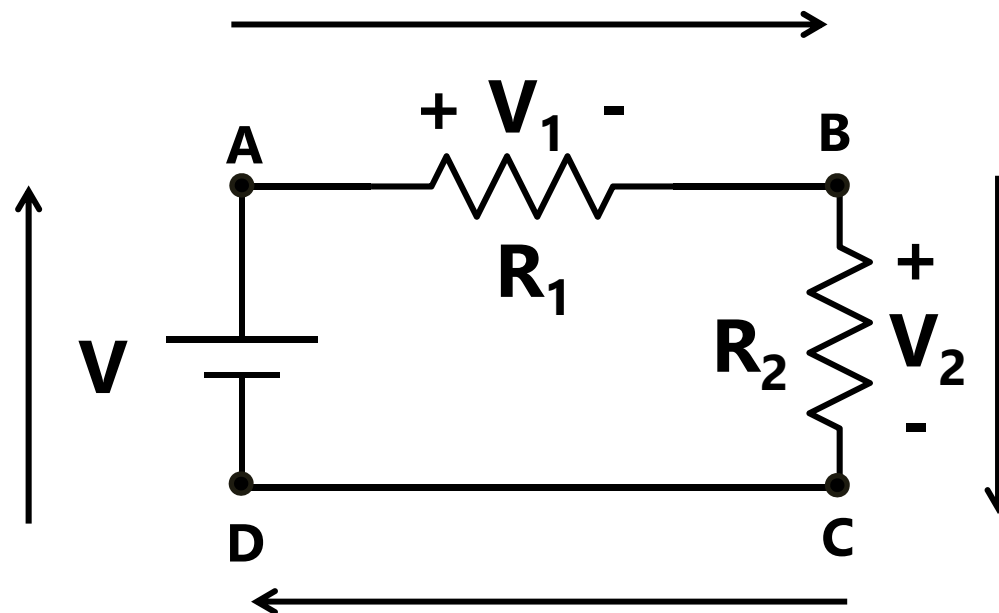
# Kirchhoff's Voltage Law

- A definition of closed path is required by starting at a point and ending at the same point thus forming a closed loop
- **Kirchhoff's Voltage Law (KVL):** The algebraic sum of the potential raises and drops around a closed path (closed loop) is zero




# Kirchhoff's Voltage Law

- Writing out the voltages in sequence by noting the sign convention,
  - $V$ : with positive sign
  - $V_1, V_2$ : with negative sign
- By applying KVL,
  - Loop: "A" → "B" → "C" → "D" → "A"

$$+V - V_1 - V_2 = 0$$



$$V = V_1 + V_2$$

$$\sum_{raises} V = \sum_{drops} V$$

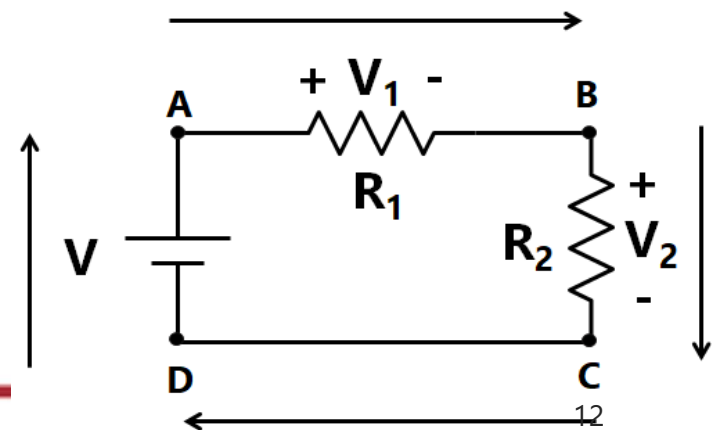
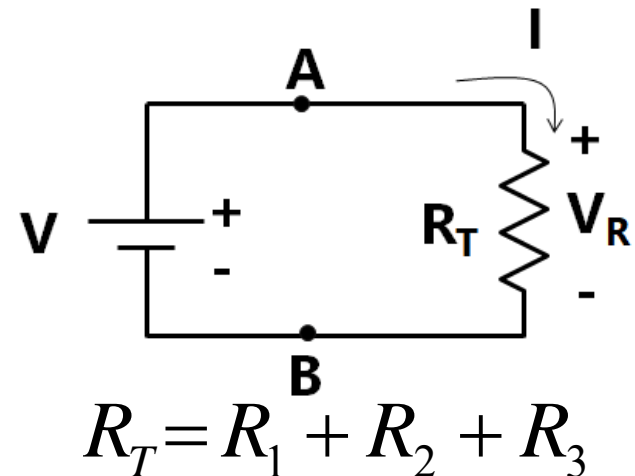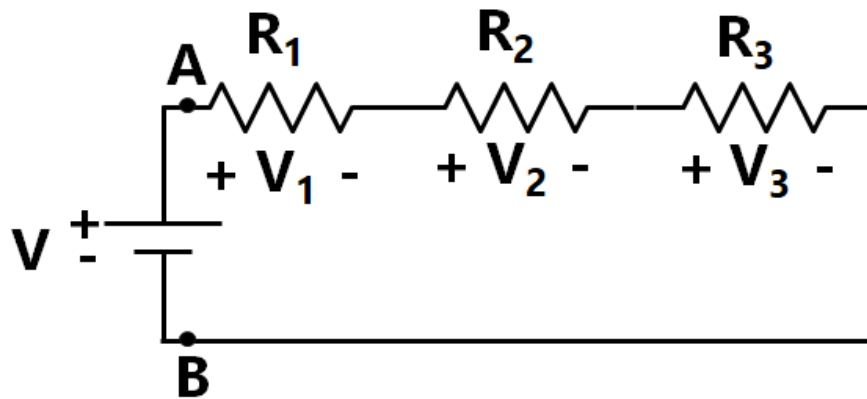
# Resistances Connected in Series-Voltage Divider Rule

- To calculate the voltage drop across the each resistance in a series circuit



- Current through the circuit  $I$  is given by

$$I = \frac{V}{R_T} = \frac{V_R}{R_T}$$

# Resistances Connected in Series-Voltage Divider Rule


- Voltage drop  $V_1$  across resistor  $R_1$  is given by  $V_1 = IR_1$ .
- Similarly,  $V_2 = IR_2$ ,  $V_3 = IR_3$
- $IR_1 + IR_2 + IR_3 = IR_T = V$
- Thus, voltage drop across  $R_1$  is given by

$$V_1 = IR_1 = \frac{V}{R_T} R_1 = \frac{R_1}{R_T} V$$

- Similarly,

$$V_2 = IR_2 = \frac{V}{R_T} R_2 = \frac{R_2}{R_T} V \quad V_3 = IR_3 = \frac{V}{R_T} R_3 = \frac{R_3}{R_T} V$$

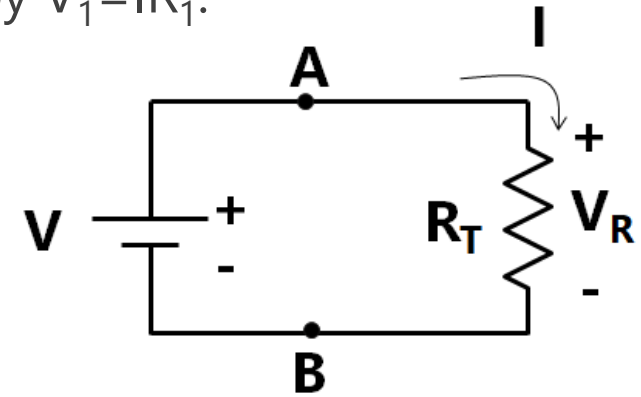- Thus,  $V = IR_1 + IR_2 + IR_3 = \left( \frac{R_1}{R_T} + \frac{R_2}{R_T} + \frac{R_3}{R_T} \right) V$




$$R_T = R_1 + R_2 + R_3$$


**The voltage drop is maximum across the largest resistor in the series combination**
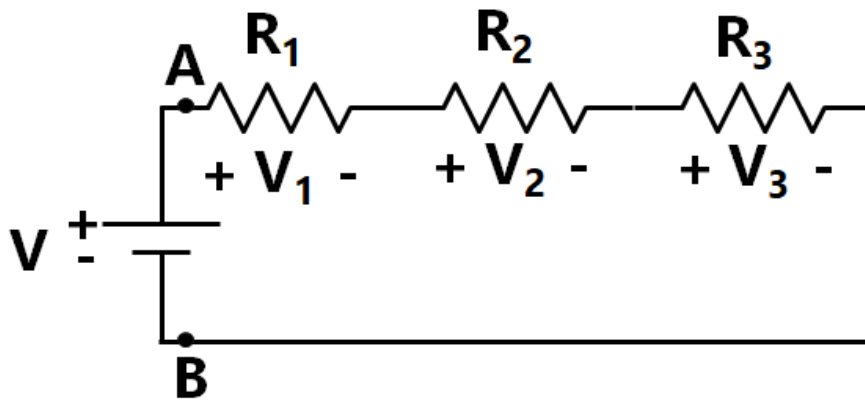
# Resistances Connected in Series

- To calculate the voltage drop across the each resistance in a series circuit


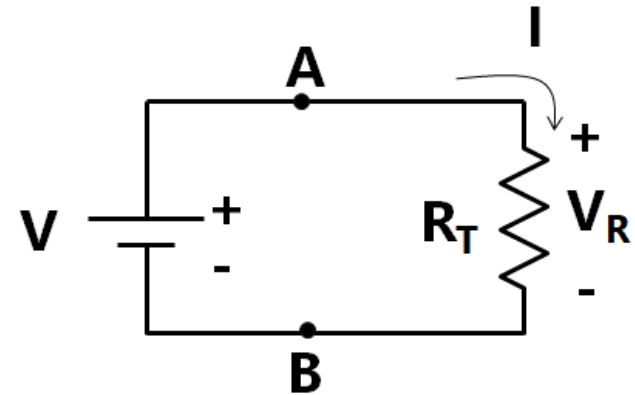
$$R_1 = 1 \text{ k}\Omega, R_2 = 5 \text{ k}\Omega, R_3 = 1.5 \text{ k}\Omega$$




$$I = \frac{V}{R_T} = \frac{15V}{7.5k\Omega} = 2mA$$

$$V_1 = IR_1 = 2V, V_2 = IR_2 = 10V, V_3 = IR_3 = 3V$$

$$R_2 (5k\Omega) > R_3 (1.5k\Omega) > R_1 (1k\Omega)$$

$$V_2 (10V) > V_3 (3V) > V_1 (2V) \quad V_R = V_1 + V_2 + V_3 = 2 + 10 + 3 = 15V = V$$

# Parallel Connections

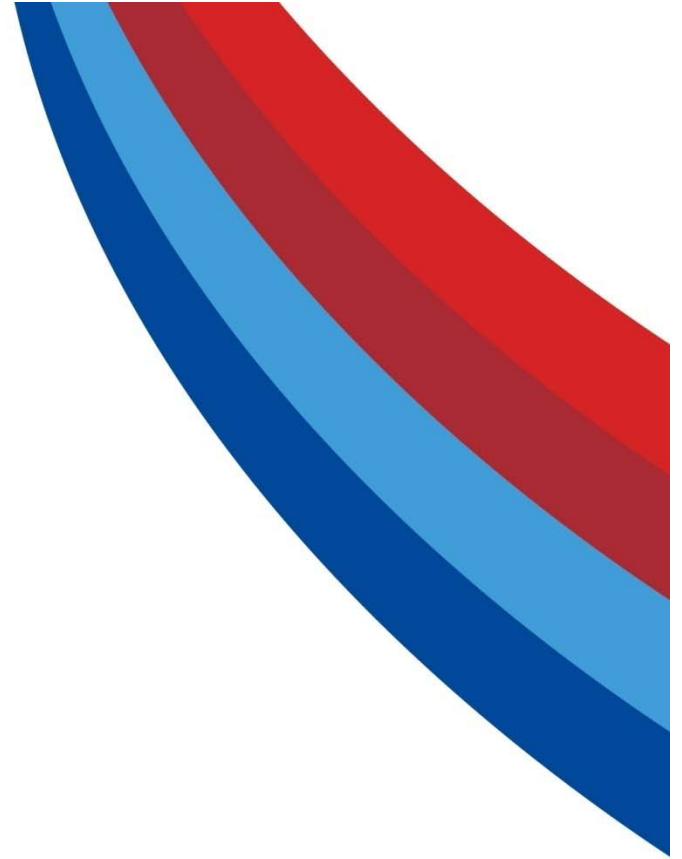




# Parallel Connections


- Two elements or circuits or branches are in **parallel** if they have two **points in common**
- The total current before branching is sum of currents in the individual branches

$$I = I_1 + I_2$$

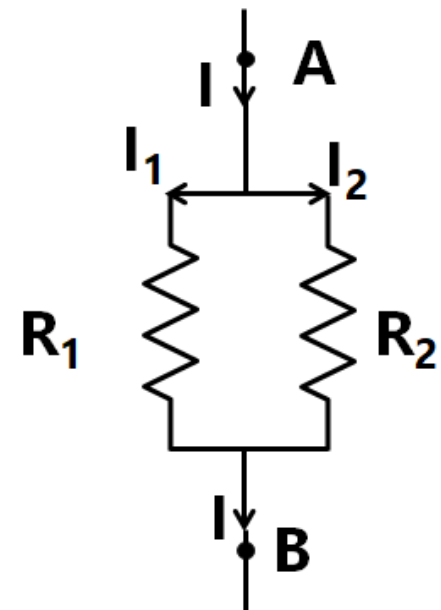
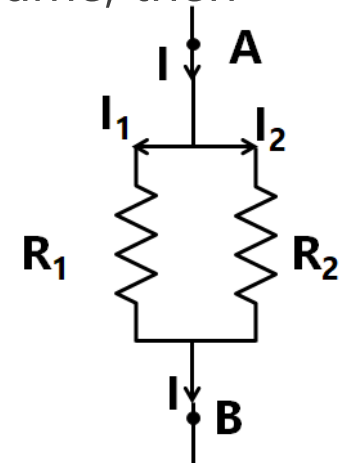
# Parallel Connections

- Two elements or circuits or branches are in **parallel** if they have two **points in common**
- Voltage across parallel elements is always same
- If two elements are in parallel the voltage across them must be same.
- If the voltage across two neighbouring elements is the same, then the two elements may not be in parallel



# Equivalent Resistance of a Parallel Combination

- Let  $I$  be the total current and  $V_{AB}$  be the voltage between points **A** and **B** and  $R_T$  be the equivalent resistance between points **A** and **B**

- The total current  $I$  is given 
$$I = \frac{V_{AB}}{R_T}$$


- The total current  $I = I_1 + I_2 + I_3$

- Current through resistance  $R_1$  is given by

$$I_1 = \frac{V_{AB}}{R_1}$$

- Similarly,
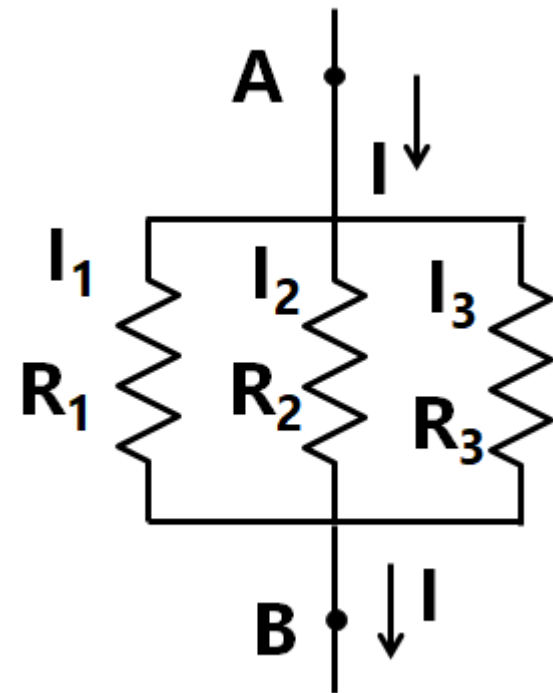
$$I_2 = \frac{V_{AB}}{R_2} \quad I_3 = \frac{V_{AB}}{R_3}$$




# Equivalent Resistance of a Parallel Combination

➤ Thus

$$I = \frac{V_{AB}}{R_T} = I_1 + I_2 + I_3 = \frac{V_{AB}}{R_1} + \frac{V_{AB}}{R_2} + \frac{V_{AB}}{R_3}$$

$$\boxed{\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}}$$

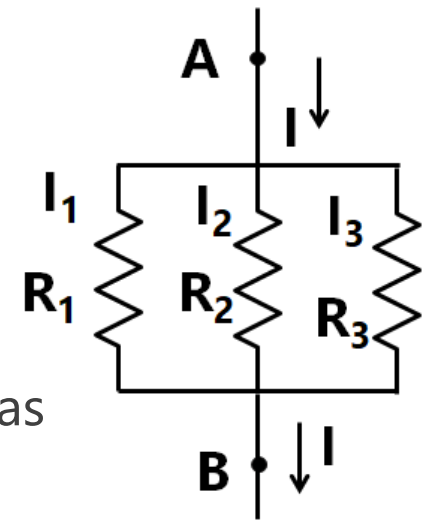➤ The large the value of resistance is, less the effect it has




# Current Division

- Current  $I_1$  through resistance  $R_1$  is given by

$$I_1 = \frac{V_{AB}}{R_1}$$

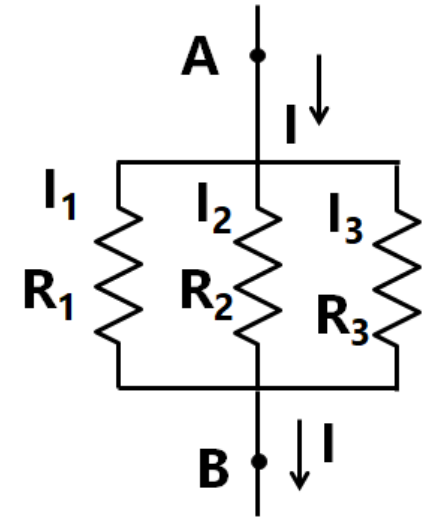- Substituting  $I = \frac{V_{AB}}{R_T} \Rightarrow I_1 = \frac{IR_T}{R_1}$



$$\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \Rightarrow R_T = \frac{R_1 R_2 R_3}{R_2 R_3 + R_3 R_1 + R_1 R_2}$$


- Thus, 
$$I_1 = \frac{R_2 R_3}{R_2 R_3 + R_3 R_1 + R_1 R_2} I$$

# Current Division

$$I_1 = \frac{R_2 R_3}{R_2 R_3 + R_3 R_1 + R_1 R_2} I$$

$$I_2 = \frac{R_3 R_1}{R_2 R_3 + R_3 R_1 + R_1 R_2} I$$
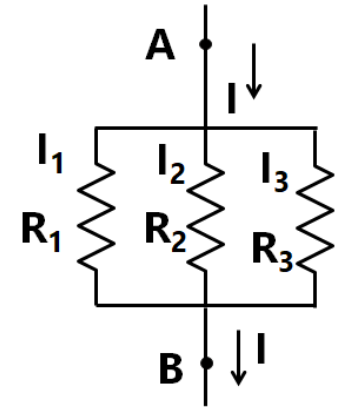
$$I_3 = \frac{R_1 R_2}{R_2 R_3 + R_3 R_1 + R_1 R_2} I$$




- The branch with largest resistance in a parallel combination has maximum current

# Kirchhoff's Current Law

- The algebraic sum of currents entering and leaving a junction or region of a network is zero
- Let  $I_i$  be the currents that enter in to a junction and let  $I_o$  be currents leaving a junction. Then **KCL** states

$$\Sigma I_i = \Sigma I_o$$

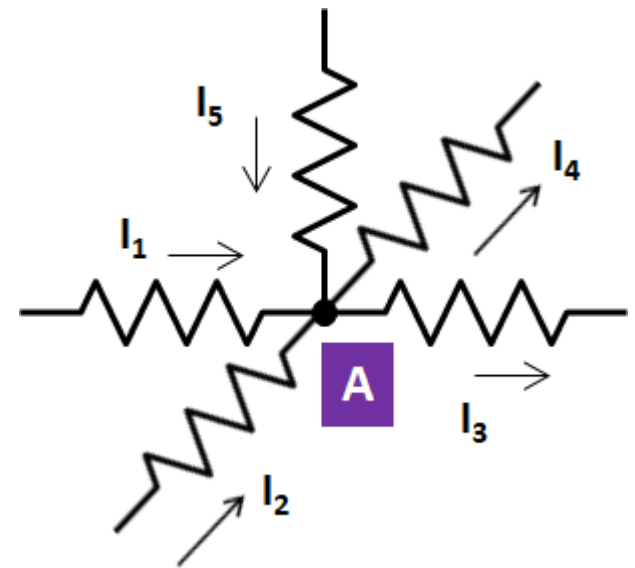- $I_1$ ,  $I_2$  and  $I_5$  are entering junction or node "A"
- $I_3$  and  $I_4$  are leaving junction or node "A"
- Thus, as per KCL,  $I_1 + I_2 + I_5 = I_3 + I_4$



# Ground

- Electrical and electronic systems are generally grounded for reference and safety purposes.
- The symbol for the **ground** connection appears, then its defined potential level is **zero volts**.





Standard symbols for Ground



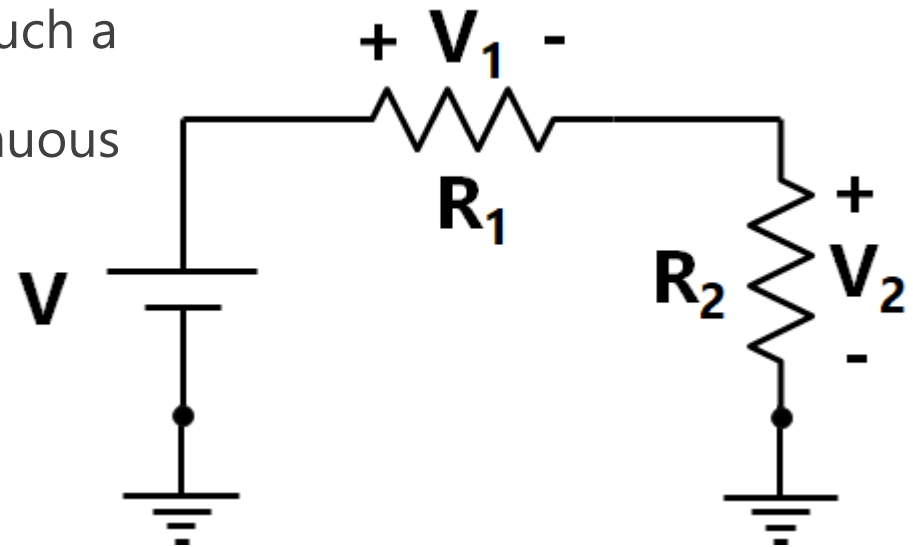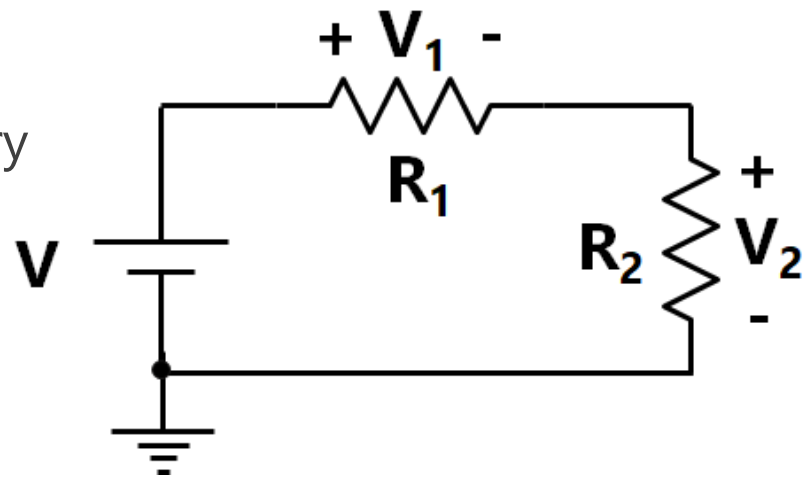
# Circuit Connections With Ground

- Consider the circuit shown below
- the negative terminal of the battery and the bottom of the resistor  $R_2$  are at ground potential
- No connection between the two grounds, it is recognized that such a
- connection exists for the continuous flow of charge




# Circuit Connections With Ground

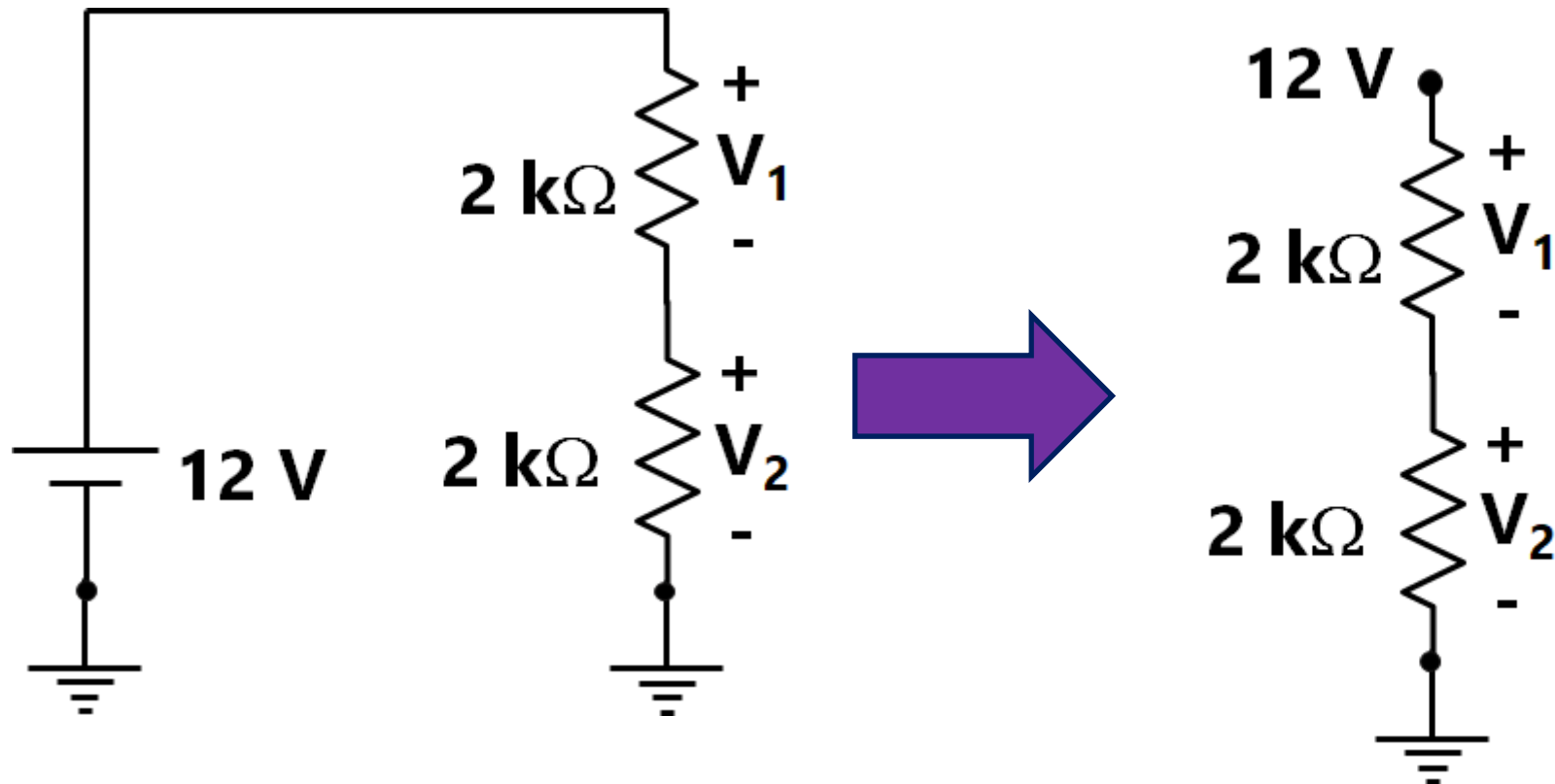
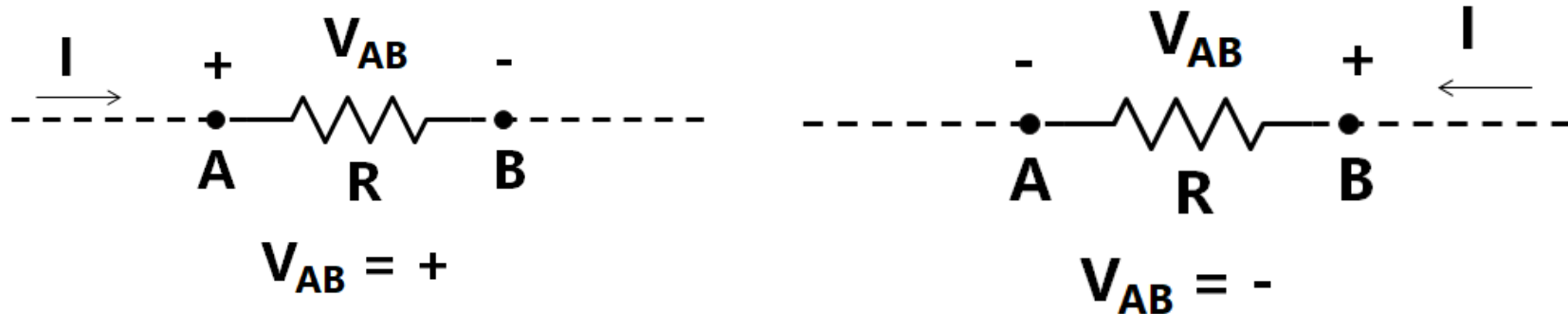
# Double Script Notation

- Voltage is an *across* variable and exists between two points
- Represented using a double-subscript notation that defines the first subscript as the higher potential




$$V_{AB} = V_A - V_B$$

# Open Circuit

- An **open circuit** is simply two isolated terminals not connected by an element of any kind

$$V_{\text{open-circuit}} = V_{AB} = V$$

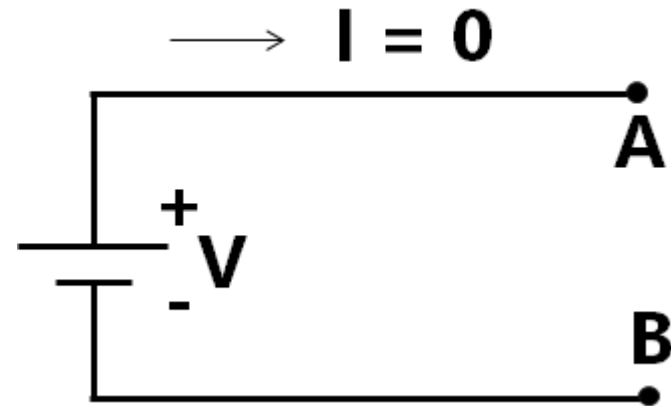

- A path for conduction does not exist.
- The current associated with an open circuit must always be zero.
- The voltage across the open circuit, however, can be any value, as determined by the system it is connected to.

# Short Circuit

- A **short circuit** is a very low resistance, direct connection between two terminals of a network
- The current through the short circuit can be any value, as determined by the system it is connected to
- The voltage across the short circuit will always be zero volts because the resistance of the short circuit is assumed to be zero ohms
- Thus,  $V = IR = I(0) = 0 \text{ V}$ .

