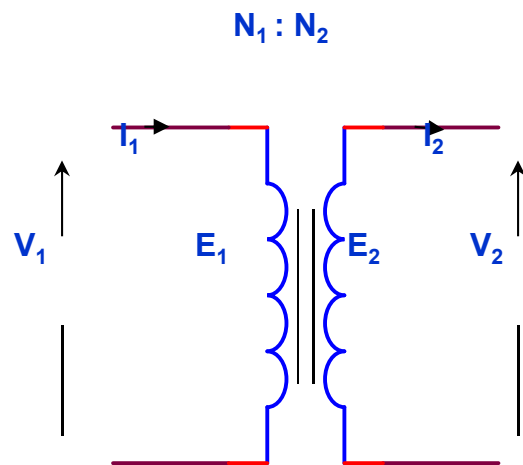


Ideal Transformer

- An ideal transformer is a transformer which has no losses, i.e. its winding has no ohmic resistance, no magnetic leakage, and therefore no $I^2 R$ and core losses.
- However, it is impossible to realize such a transformer in practice.
- Yet, the approximate characteristic of ideal transformer will be used to characterize the practical transformer.



V_1 – Primary Voltage

V_2 – Secondary Voltage

E_1 – Primary induced Voltage

E_2 – secondary induced Voltage

$N_1:N_2$ – Transformer ratio

Transformer Equation

- Faraday's Law states that,
 - If the flux passes through a coil of wire, a voltage will be induced in the turns of wire. This voltage is directly proportional to the rate of change in the flux with respect of time.

$$V_{ind} = \mathcal{E}_{ind} = -\frac{d\Phi(t)}{dt}$$

If we have N turns of wire,

$$V_{ind} = \mathcal{E}_{ind} = -N \frac{d\Phi(t)}{dt}$$

Transformer Equation

- For an **ac sources**,

- Let $V(t) = V_m \sin \omega t$

- $i(t) = i_m \sin \omega t$

Since the flux is a sinusoidal function;

Then:

$$\Phi(t) = \Phi_m \sin \omega t$$

Therefore:

$$V_{ind} = Emf_{ind} = -N \frac{d\Phi_m \sin \omega t}{dt}$$

$$= -N\omega\Phi_m \cos \omega t$$

$$V_{ind} = Emf_{ind(max)} = N\omega\Phi_m = 2\pi f N\Phi_m$$

Thus:

$$Emf_{ind(rms)} = \frac{N\omega\Phi_m}{\sqrt{2}} = \frac{2\pi f N\Phi_m}{\sqrt{2}} = 4.44 f N\Phi_m$$

Transformer Equation

- For an ideal transformer

$$\begin{aligned} E_1 &= 4.44 f N_1 \Phi_m \\ E_2 &= 4.44 f N_2 \Phi_m \end{aligned} \dots\dots\dots (i)$$

- In the equilibrium condition, both the input power will be equaled to the output power, and this condition is said to ideal condition of a transformer.
- From the ideal transformer circuit, note that,

$$\begin{aligned} \text{Input power} &= \text{output power} \\ V_1 I_1 \cos \theta &= V_2 I_2 \cos \theta \\ \therefore \frac{V_1}{V_2} &= \frac{I_2}{I_1} \end{aligned}$$

- Hence, substitute in (i)

$$E_1 = V_1 \text{ and } E_2 = V_2$$

Transformer Equation

$$\text{Therefore, } \frac{E_1}{E_2} = \frac{N_1}{N_2} = \frac{I_2}{I_1} = a$$

Where, 'a' is the Voltage Transformation Ratio; which will determine whether the transformer is going to be step-up or step-down

For $a > 1 \longrightarrow E_1 > E_2 \longrightarrow$

For $a < 1 \longrightarrow E_1 < E_2 \longrightarrow$

Transformer Rating

- Transformer rating is normally written in terms of Apparent Power.
- Apparent power is actually the product of its rated current and rated voltage.

$$VA = V_1 I_1 = V_2 I_2$$

- Where,
 - I_1 and I_2 = rated current on primary and secondary winding.
 - V_1 and V_2 = rated voltage on primary and secondary winding.
 - Rated currents are the full load currents in transformer

Transformer Losses

- Generally, there are two types of losses;
 - i. Iron losses :- occur in core parameters
 - ii. Copper losses :- occur in winding resistance

i. Iron Losses

$$P_{iron} = P_c = (I_c)^2 R_c = P_{open\ circuit}$$

ii Copper Losses

$$P_{copper} = P_{cu} = (I_1)^2 R_1 + (I_2)^2 R_2 = P_{short\ circuit}$$

or if referred, $P_{cu} = (I_1)^2 R_{01} = (I_2)^2 R_{02}$

Transformer Efficiency

- To check the performance of the device, by comparing the output with respect to the input.
- The higher the efficiency, the better the system.

$$\begin{aligned}\text{Efficiency, } \eta &= \frac{\text{Output Power}}{\text{Input Power}} \times 100\% \\ &= \frac{P_{out}}{P_{out} + P_{losses}} \times 100\% \\ &= \frac{V_2 I_2 \cos \theta}{V_2 I_2 \cos \theta + P_c + P_{cu}} \times 100\%\end{aligned}$$

Where $P_{cu} = P_{sc}$
 $P_c = P_{oc}$

$$\begin{aligned}\eta_{(full\ load)} &= \frac{VA \cos \theta}{VA \cos \theta + P_c + P_{cu}} \times 100\% \\ \eta_{(load\ n)} &= \frac{nVA \cos \theta}{nVA \cos \theta + P_c + n^2 P_{cu}} \times 100\%\end{aligned}$$

Where, if $\frac{1}{2}$ load, hence $n = \frac{1}{2}$,
 $\frac{1}{4}$ load, $n = \frac{1}{4}$,
90% of full load, $n = 0.9$

Voltage Regulation

- The purpose of voltage regulation is basically to determine the percentage of voltage drop between no load and full load.

Voltage Regulation (Basic Definition)

- In this method, all parameter are being referred to primary or secondary side.
- Can be represented in either
 - ❖ Down – voltage Regulation

$$V.R = \frac{V_{NL} - V_{FL}}{V_{NL}} \times 100\%$$


- ❖ Up – Voltage Regulation

$$V.R = \frac{V_{NL} - V_{FL}}{V_{FL}} \times 100\%$$


Motors

AC Motor::

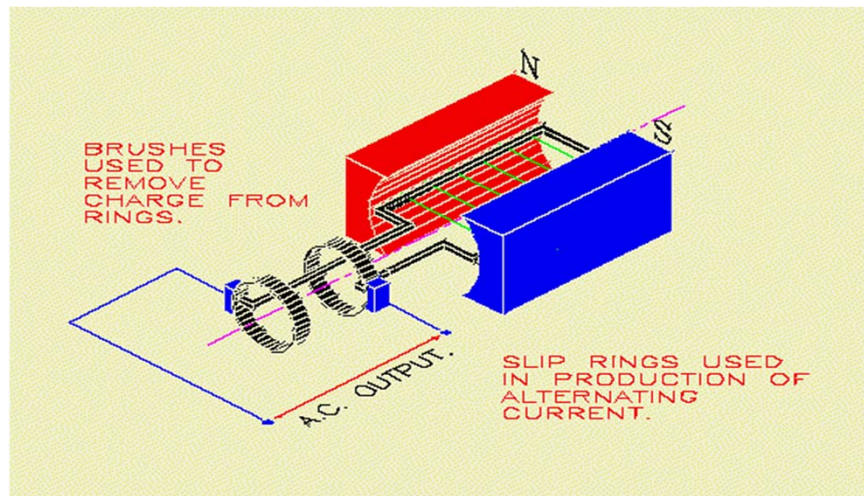- An **AC motor** is an electric motor driven by an alternating current (AC).




Magnet supported from above

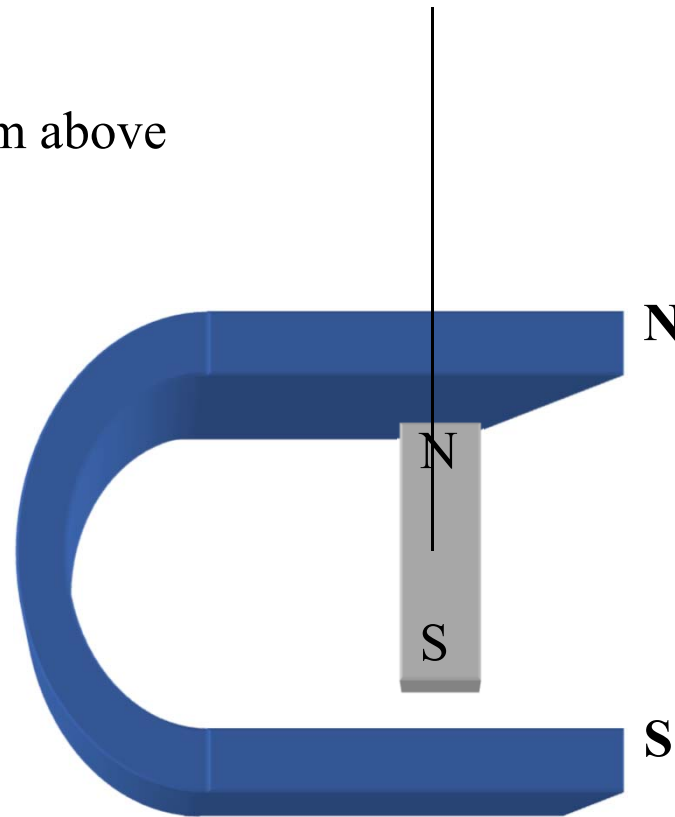


Since unlike poles repel each other, the magnet will rotate


Stationary Magnet

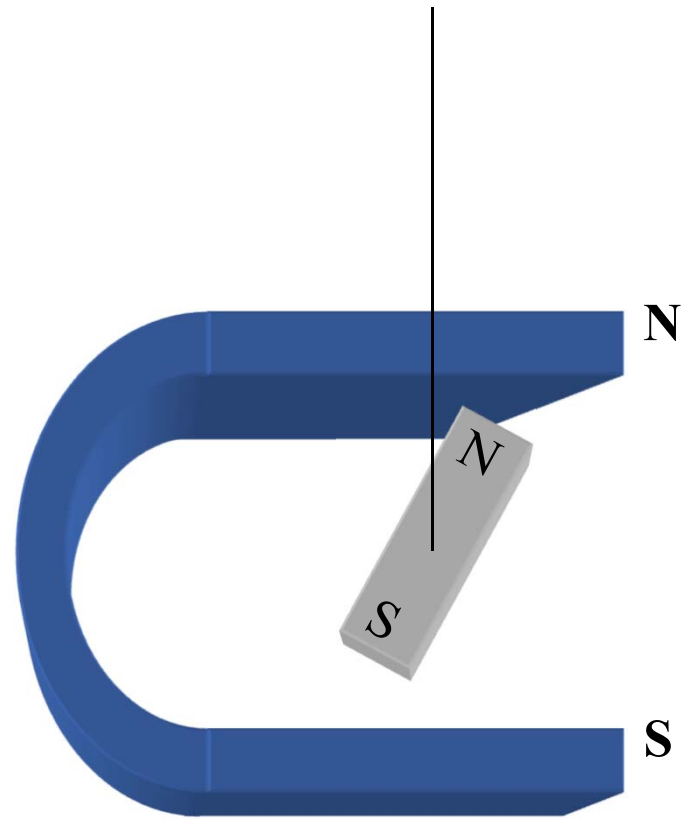


Stationary Magnet

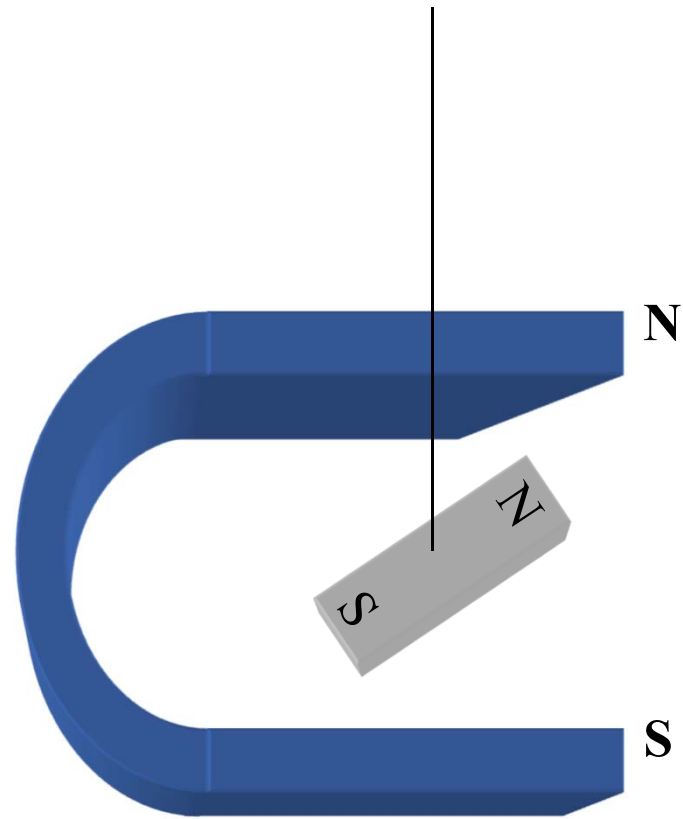


Stationary Magnet

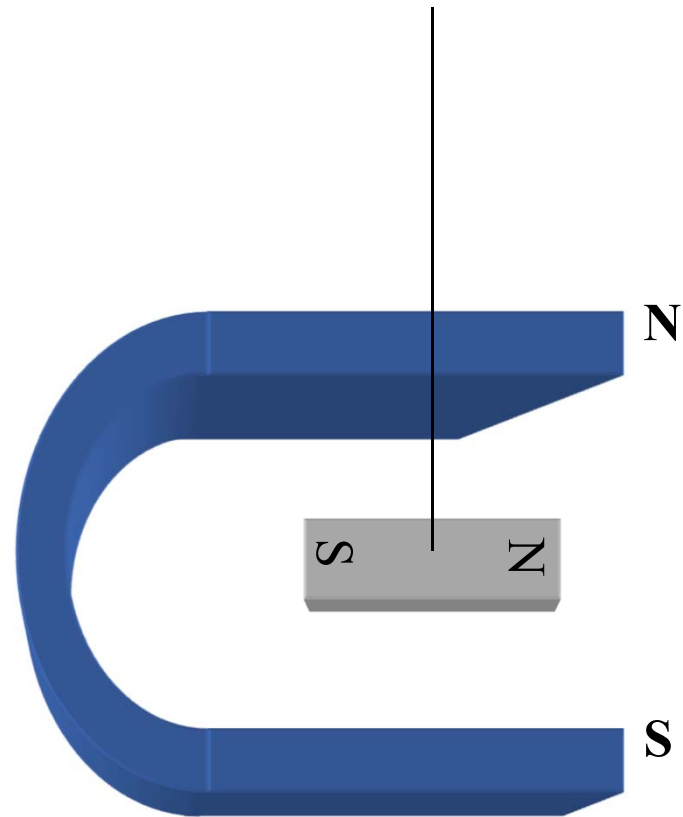


Stationary Magnet

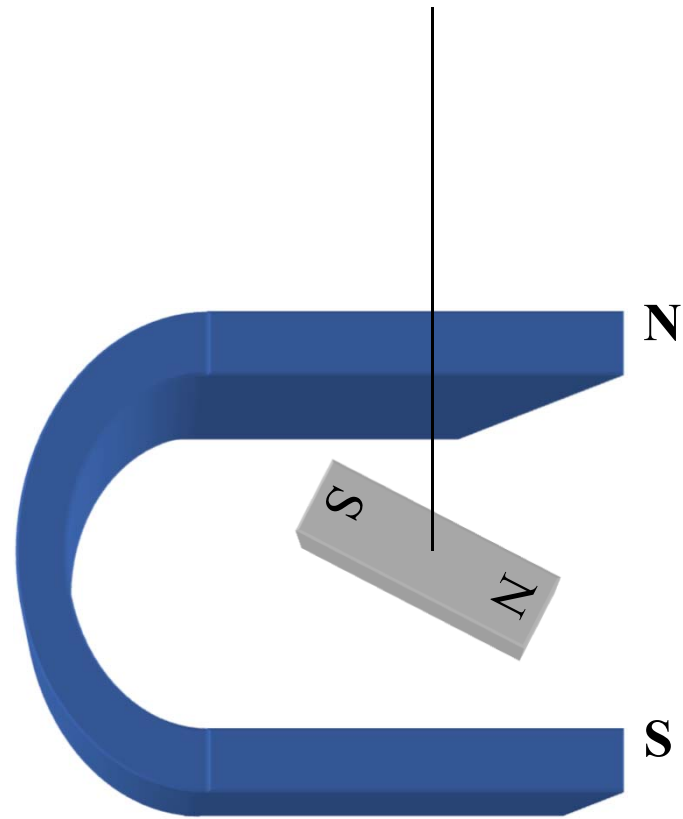

Stationary Magnet

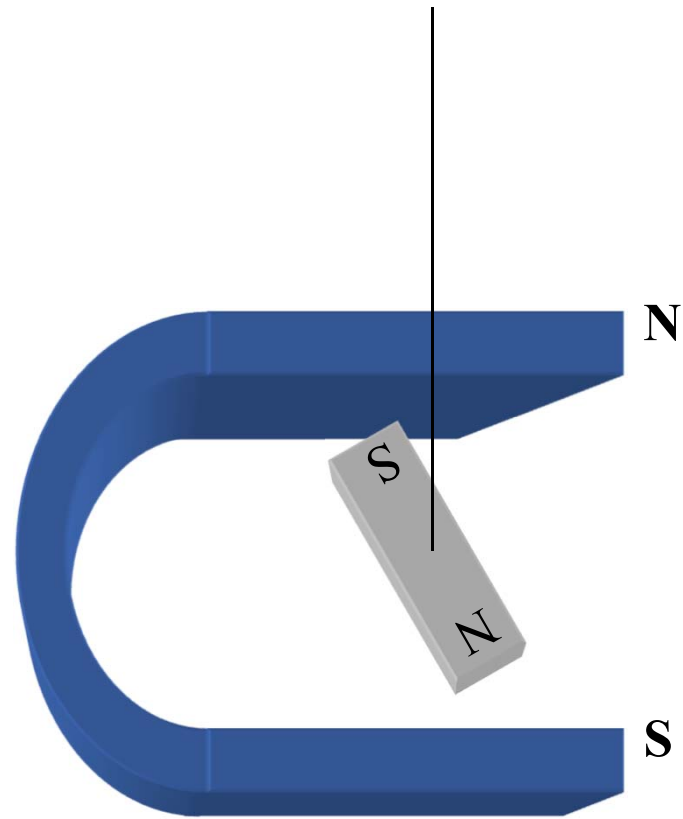


Stationary Magnet

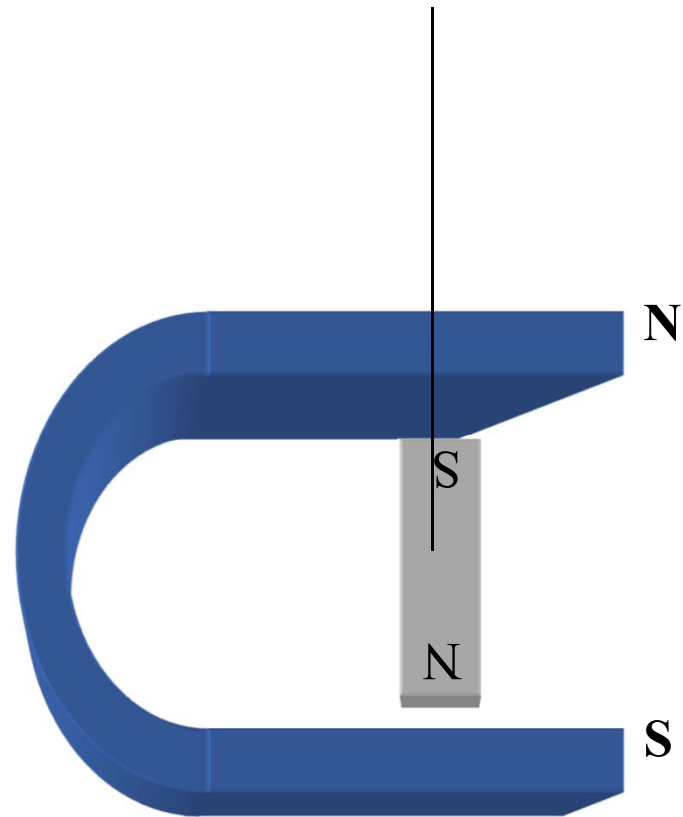

When the unlike poles are lined up with each other, rotation will stop

Stationary Magnet

Exploded View of Stepper Motor

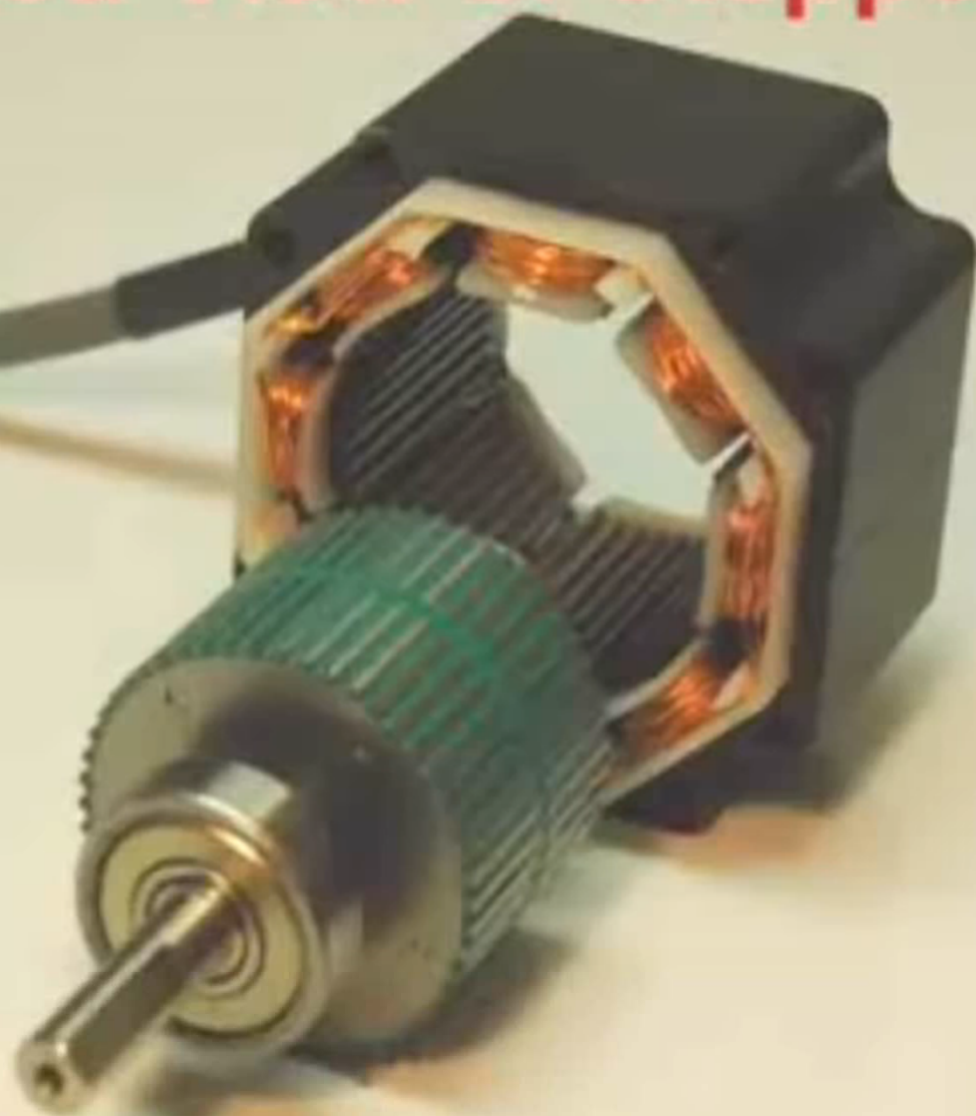

Inventor
DATE

Date: 9/1/2011



TEXAS
INSTRUMENTS

Slide 40

Stepper Motor

- $SPR = NR \times N$
- Where: SPR = number of steps per revolution
- NR = total number of rotor teeth (total for both yokes)
 - In the previous example, $NR = 50 + 48 = 98$
- N = number of motor phases
 - In the above example, the number of phases are two
- $SPR = 98 \times 2 = 198$
- In one revolution, there are 360°
- Angle of rotation for one revolution

$$\theta = \frac{360^\circ}{SPR}$$

$$\theta = \frac{360^\circ}{198} = 1.8^\circ$$